



Editorial

THINGS are moving fairly rapidly in the television world, and all over the world according to reports from overseas.

The American FCC proposals concerning bracket standards have carried the color controversy a little nearer a conclusion but do not necessarily imply color television in the immediate future. It may, in fact, project color services still further ahead.

The decision has opened the deadlock which has existed in that country for some time, but I am quite sure it has not closed the subject of color television. Nor do I imagine that anyone in the USA feels that the bracket standards will be the final answer. Experience may show it to be the best and simplest for some little time, but I think we can watch what happens in the color world, safe in the knowledge that some really fast work will be accomplished.

In Australia, recent parliamentary debate extracted from the Government a pretty clear statement of its attitude to television. In brief, the policy is that present conditions do not warrant spending large sums of money on a complete television network, but do not prohibit at least one station being built as a pilot model. "Experimental" isn't really the right word, because the station will, in fact, be one of the most modern anywhere, and will be used more for experience than for experiment.

It is hard to quarrel with the reluctance of the Government to spend on television at the present time. I often wonder just how many realise what a torrent of labor and finance will be set in motion when the time comes for a full-scale television set-up.

Frankly I don't think the industry as a whole is jubilant over the need to spend money on television. It is, of course, most anxious not to miss out on it, realising the inevitability of video transmissions. But it is I think a little afraid of just where it will all end, and just how to go about making the most of a market without sinking too much too soon or too late.

One thing seems fairly certain, however, and that is that the Government is not likely to expand its television programme until many other problems involving finance are solved. The 25 per cent sales tax hasn't helped, for it adds another £25 to every £100 television set, and points pretty clearly to the classification of radio as a luxury.

John Moyle

INDEX

Page	Page
No Sea Sickness on This Ship - - - 3	The Junior Experimenter - - - 47
Report On Color - - - 4	A Battery Charger - - - 52
Mobile Radio For Motor Cycles - - - 9	A Course In Television - - - 57
This Liner Cannot Roll - - - 11	Here's Your Answer Tom - - - 62
Batteries Drive Japan's Jeep - - - 13	Let's Buy An Argument - - - 64
Why Do Things Happen - - - 14	Trade Notes - - - 71
Technical Review - - - 17	A Reader Built It - - - 74
Radio In The African Jungle - - - 21	An Aerial Radar Laboratory - - - 79
How It Works—Rotary Excavator - - - 23	Making A Drill Stand - - - 80
News And Views - - - 25	Radio Control Of Models - - - 81
A Simplified Dual-Wave Set - - - 28	Short Wave Notes - - - 90
The Serviceman Who Tells - - - 37	The Ham Bands - - - 93
A Transmitter For 50 MC - - - 40	Answers To Correspondents - - - 101

RADIO AND HOBBIES IN AUSTRALIA

A NATIONAL MAGAZINE
OF RADIO, HOBBIES AND
POPULAR SCIENCE

EDITOR

JOHN MOYLE
S.M.I.R.E. (AUST.)

TECHNICAL EDITOR

NEVILLE WILLIAMS
A.M.I.R.E. (AUST.)

TECHNICAL STAFF

RAYMOND HOWE
MAURICE FINDLAY
PHILIP WATSON

VOL. 12 No. 8

SUBSCRIPTION RATES

C'wealth & New Guinea	N.Z.	Overseas British	Foreign
1 year 12/-	13/-	15/-	18/8
6 mths. 6/-	6/6	7/3	7/9

Published on the first Friday of each month by Associated Newspapers Ltd., 60-70 Elizabeth St., Sydney.

Phone BO333

OUR COVER PICTURE

This fine model of the RAF latest twin jet fighter epitomises the speed and grace of modern aircraft. It was the highlight of a recent RAF exhibition.

Model PA: Dynamo-
meter - type Power
Analyser.

Model VTM: Vacuum Tube
(probe) Multimeter.

Hearing Aid.

Palec Elec-
tronic photo-
flash models 60-
1,000 joules.

Palec exposure
meter.

Model SG1 Signal
Generator.

Model M30: Multi-
meter.

Model VCT2: Valve
and Circuit Tester.

Make No Mistake!

Errors cost you time, money,
reputation. Men of judgment
make no mistake. They use
'Palec' instruments—the best
guarantee of accuracy and
quality.



Palec oven tem-
perature gauge.



Moving coil panel
instruments.



Moving iron panel
instruments.



Sector-type Pyro-
meters.

REMEMBER

Palec products are
AUSTRALIAN
made, and backed
by
AUSTRALIAN
factory service.



Paton Electrical

PTY. LTD.



Manufacturers of all Types of Radio & Electrical Test Equipment & Meters.

90 VICTORIA STREET, ASHFIELD, SYDNEY.

Tels.: UA 1923-1960-1982. Telegrams: "Palec."

★ PALEC ARE THE SOLE AUSTRALASIAN AGENTS FOR THE WORLD-FAMOUS "MEGATRON" BARRIER-LAYER PHOTOCELLS—STOCKS ON HAND—ENQUIRY INVITED

NO SEASICKNESS ON THIS SHIP

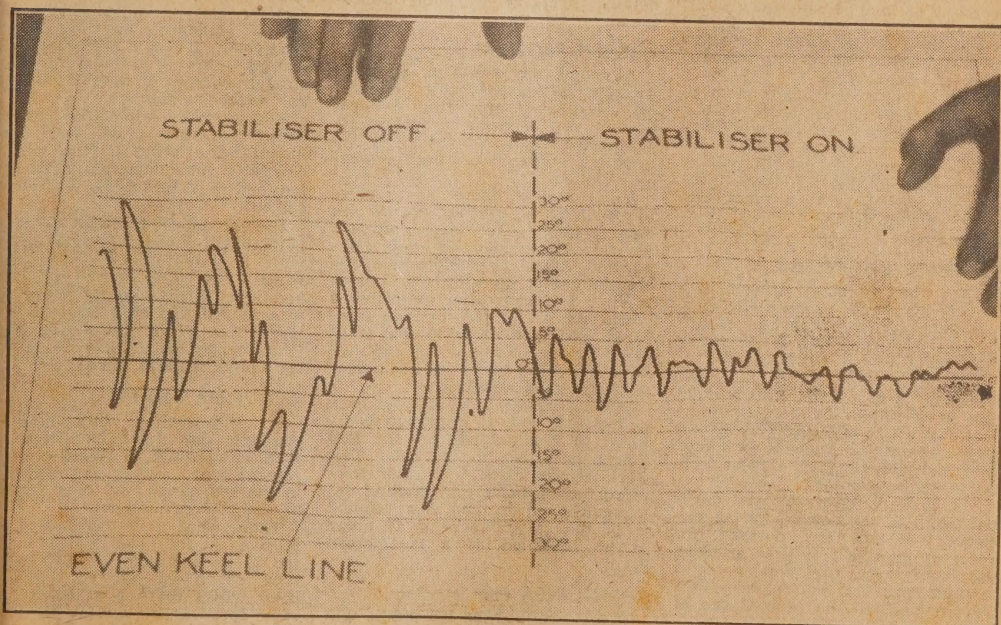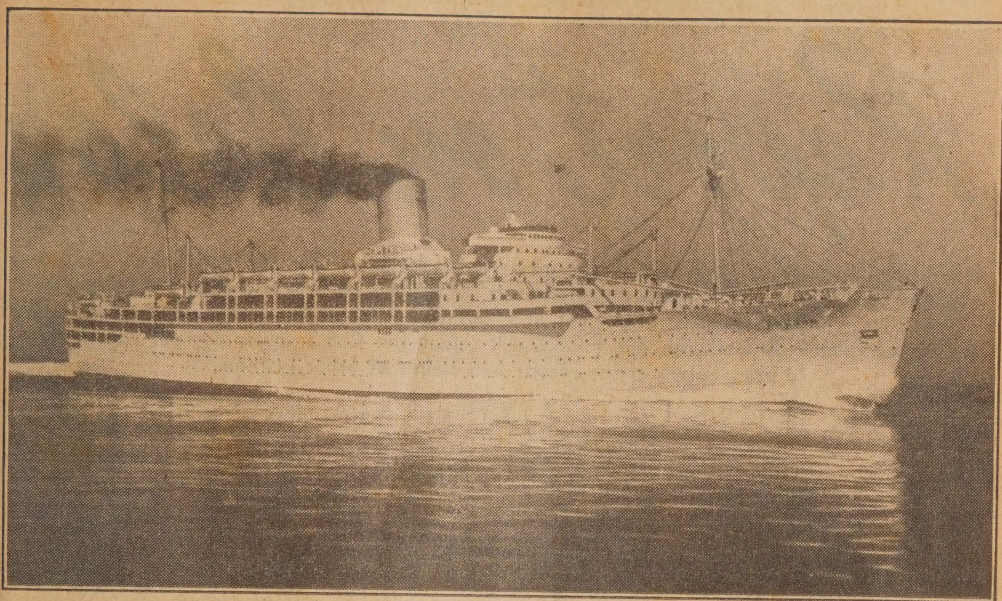

The use of an ingenious stabilising device makes "roll" and sea sickness almost impossible with the 24,000-ton luxury liner RMS Chusan, shown above. The graph in the lower picture illustrates how effectively the stabilising fins iron out the roll, and keep the liner on an even keel. See story on page 11.

The Radio Scene

Report on Color

In an effort to reach some finality in the matter of color television, the American F.C.C. has made a statement to U.S. radio manufacturers. In essence, it says that they must henceforth supply receivers adaptable to a new set of standards. Unless the trade adopts this guard against obsolescence forthwith, the F.C.C. will select the C.B.S. color system as standard, irrespective of the results and claims of other systems.

THE main points exercising the mind of the F.C.C. right now are obsolescence and compatibility—the ability of ordinary receivers to produce a monochrome version of possible color programmes.

The F.C.C. has been trying to reach a decision on this, one way or another, for months, but technical developments have followed in such quick succession that no finality has been reached.

Meanwhile thousands of television receivers are being made every week, and sufficient of them were in the hands of the US public to allow several million viewers to see the Louis-Charles fight.

Even now, before any system of color can be made available, tens of thousands more receivers will have been built and sold. And the F.C.C. knows that new set owners will be up in arms if they are denied the right to see at least a black and white version of the eventual color programmes.

SEPARATE RECEIVERS

They won't be happy either if they have to instal two separate receivers, one for color, the other for monochrome, each receiving a completely different group of stations.

The question is asked: "If color television is still in its infancy—and that is certainly the case—why go into it at all at this stage? Why not wait and see, as England is doing? And, last but not least, is color television really wanted?"

The proponents of this last question point to the cinema for an example. It has been possible, for years at increased cost, to produce any number of first quality color features but, in actual fact, they have not ousted the general run of black and white films.

Against this it is contended that the cases are not similar. Experts point out that, even allowing for mediocre efforts, a lot of editing and

planning goes into the production of a film and, generally speaking, the dramatic interest is sustained. If it isn't, out come the scissors!

With television, a good deal of the programme material comes from sporting and outdoor events, and there may well be lengthy periods when nothing much is happening. During such periods, interest will lag immediately unless color is there to portray the grass, the sky, the colorful costumes, and all the other details necessary to build atmosphere.

URGENT PROBLEM

Although the F.C.C. is probably subjected to a good deal of commercial pressure, it apparently believes in the "pro" arguments sufficiently to regard color television as an urgent problem, requiring immediate solution.

Unfortunately, there is far more to it than merely saying "yes, we will have color." The whole problem of introducing color is more complicated, if that is possible, than the original one of introducing television itself. You have first to evolve a whole new set of transmission standards, add to them additional standards for the color build-up, and then solve the vexed problem of compatibility for good measure.

The earliest color work dates back to the 1930 era, to experiments by Baird in England and by the Bell Telephone Labs, in the US. This work demonstrated that color television was feasible and gradual development since then has brought it to the stage where it is about to be launched as a commercial reality.

THE GUINEA PIG

It appears that the US public will be the "guinea pig" on this occasion, leaving other countries to profit from their experience.

It seems pretty certain now that

in Australia, the PMG will be quite happy for a while to watch US efforts to wrestle with the problem.

Although there are many variant color television work in the US, the centred most around three rival groups which have pursued different lines of approach technically, each achieving a degree of success. The methods employed are quite different, and the F.C.C. has to make up its mind which one is the best.

The Columbia Broadcasting System (C.B.S.) started out with the premise that you had to have a new set of standards anyway, to get good color. It would only complicate matters by trying to make the transmissions conform to the present black and white standards.

Furthermore, when the experiments were put under way, there was little offering in the way of electronic color devices and the system had to be essentially a mechanical one.

Having reached these decisions, Columbia provided their video camera with a simple motor-driven color wheel. The wheel carried red, green and blue filters and its speed was so arranged that each separate film was in front of the optical system just long enough for the camera to scan the complete scene, once.

COLUMBIA SYSTEM

By this method they produce complete red, green and blue pictures in sequence, or rather complete sets of video signals corresponding to the red, green and blue versions of the televised scene.

These were duly transmitted and received in the usual way and then fed to an ordinary "white" picture tube, which was viewed through color wheel rotating at exactly the same speed as the one at the transmitter. The rapid succession of color images were seen by the viewer as a complete tri-color picture.

In essence, this system resembles

one of the Baird rotating disc method which was abandoned many years ago.

On the surface, the C.B.S. system suffered from certain basic limitations, not the least of which was the necessity for using high speed color wheels in front of the viewing tube. If the tube was to be of a useful size, the color wheel would need to be of cartwheel dimensions.

Furthermore, all the problems of maintenance, noise, safety, synchronization and bulk would operate against the C.B.S. system. And these very things had already sped the doom of mechanical black and white television.

However, C.B.S. introduced many refinements, and they were also quick to point out that their system could change over to purely electronic reproduction when this has reached what they consider to be a satisfactory standard.

Quite apart from the method of reproduction, the C.B.S. field sequential scanning system calls for a high picture repetition rate, if flicker is to be avoided.

For black and white reproduction, it is sufficient to fill in the outlines of the scene at a rate of from 50 to 60 frames per second. However, if this same number of frames is to be subdivided between three distinct color images, the repetition rate for each color is limited to 20 or less, which can give rise to severe color flicker.

STROBING

A further effect is that strobing occurs with moving objects. Under bad conditions, the object is split up into colored stripes or patches.


To overcome these effects, C.B.S. found it necessary to raise the frame repetition rate, and, with it, the total band-width occupied by the transmission. As a result, the early C.B.S. experiments pre-supposed that much higher carrier frequencies would have to be set aside, and that the picture signal band-width would be about 16 Mc!

In an effort to avoid this exorbitant demand on "ether space," C.B.S. engineers cut down the number of picture lines, thereby slipping well below the resolution that was theoretically possible from the 525 monochrome standard. Many changes have been made over the period of experiment and it has now been found possible to compress the signal into a channel approximately 6 Mc. wide, which is similar to that required by a black and white station.

But the point is that, out of all this, C.B.S. engineers have been able to turn on demonstrations, and offer arguments, which have made a favorable impression on the F.C.C.

The one big objection to the C.B.S. system from a commercial viewpoint is that the color transmission standards have nothing in common with the monochrome standards already operating, and therefore with those built into the nation's receivers.

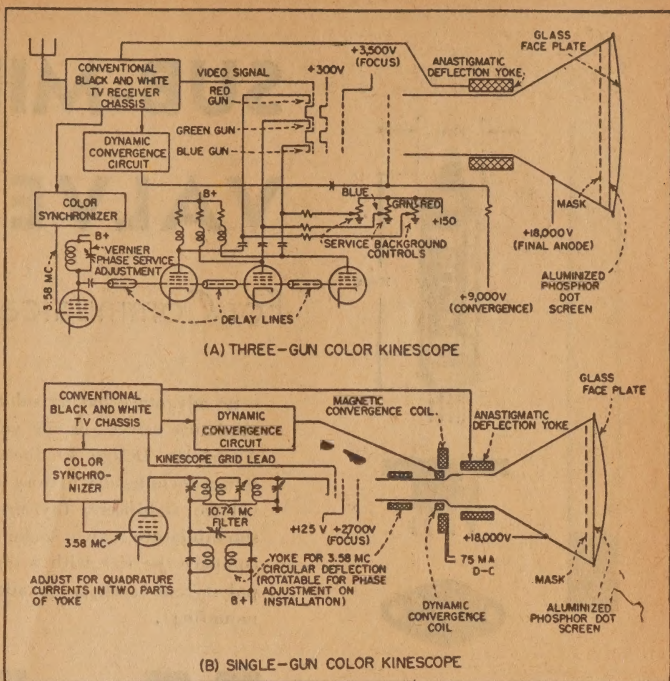Any station which might be permitted to commence transmission on these standards would have to face



This diagram from "Electronics" shows the essential details of the RCA color system using two types of tubes but the same general principle.

the problem of producing costly programmes in the hope that people would begin buying receivers to look at them.

ELECTRONIC APPROACH

Adopting the alternative approach, the two other concerns, CTI and RCA, assumed at the outset that mechanical color scanning systems were doomed, and their efforts were directed primarily to producing an all-electronic system.

They further reasoned that the system should, if humanly possible, be compatible with existing black and white standards, so that the industry would not be faced with change-over problems. Individual stations could switch over to color, as they desired, and their viewers could continue to receive a black and white version of the picture.

It was entirely up to the viewer whether or not he purchased a new color receiver. If he did, the old set could be sold or traded in, because the new one would receive equally well in color or in black and white.

In taking up this stand, the engineers sentenced themselves to an enormous programme of original research, and progress was necessarily slow. However, the promise of all-electronic and compatible television was sufficiently good to make the FCC defer any possible decision in favor of the CBS system.

CTI dodged the problem of frame flicker by evolving a system of line sequential scanning. In other words, their camera produced a chain of

video signals equivalent to alternate lines of red, green and blue. These are built up at the receiver into a complete picture made up from an ever-changing pattern of colored scanning lines.

Unfortunately, the line structure in any one color is necessarily rather coarse, and, under certain optical conditions, a line strobing or line "crawling" effect is produced, similar to that which results from a bad interlace. The rapid pattern of lines, each slightly displaced from the other, can give the effect of horizontal lines crawling across the picture.

CTI's method of color generation at the camera also sets a limit on the definition, but this is not beyond solution. Though the complexity of equipment at the originating station must be considered, it is secondary to design considerations for millions of individual receivers.

FILTERS


RCA carried the scanning procedure to its logical limit with the dot-sequential system.

The scene to be televised is broken up into its color elements by a "dichroic" mirror system and fed to separate camera tubes. These generate continuous video signals representing the primary colors, which are fed to an electronic sampler (or switch).

Operating at an extremely high rate, this sampler extracts from each channel in turn instantaneous pulses, whose amplitude corresponds to the intensity of the particular color at

SUB-MINIATURE VALVES

For Communications and Industry

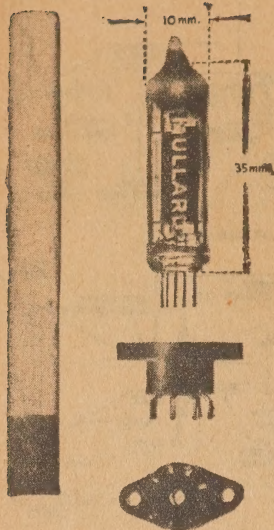

Data on a few of the Mullard sub-miniature valves is listed below. Further details available on application.

Mullard

Thermionic Valves and Electron Tubes

TYPICAL CHARACTERISTICS

Type	Description	Length (mm)	Filament or Heater (V)	(mA)	V _a (V)	V _{g2} (V)	V _{g1} (V)	I _a (mA)	g _m (ma/V)	r _a (K Ω)	P _{out} (W)
DF72	Sharp cut-off R.F. Pentode	41.2	1.25	25	67.5	67.5	0	1.7	1.0	650	—
DF73	Variable-mu R.F. Pentode	41.2	1.25	25	67.5	67.5	0	1.7	0.8	450	—
DAF70	Single Diode A.F. Pentode	41.2	1.25	25	67.5	67.5	0	0.9	0.45	200	—
DL75	A.F. Output Pentode	41.2	1.25	25	90	90	-3	1.3	0.67	500	0.047
EF70	High Slope R.F. Pentode with Short q3 base	38	6.3	200	100	100	-2	3.0	2.3	100	—
EF72	High Slope R.F. Pentode	38	6.3	150	100	100	-1.4	7.0	5.0	200	—
EF73	High Slope non-R.F. Pentode	38	6.3	200	100	100	-2.0	7.5	5.0	250	—
EC70	R.F. Triode for use as Oscillator up to 500 Mc/s	38	6.3	150	100	—	-2.0	13	5.5	3.6	0.75 500 Mc/s
*EA76	Single Diode	25.4	6.3	150	150 (r.m.s.)	—	—	g (max)	—	—	—
70B1	Voltage Stabiliser	50.7	V burning = 70V., Current range = 5-15mA., A.C. resistance = 300 Ω .								

* 5 mm diameter bulb. Leads disposed on pitch circle of 2.3 mm diameter.



INDUSTRIAL POWER VALVES • THYRATRONS • INDUSTRIAL RECTIFIERS • PHOTO-CELLS • FLASH TUBES • ACCELEROMETERS • CATHODE RAY TUBES • STABILISERS AND REFERENCE LEVEL TUBES • COLD CATHODE TUBES • ELECTROMETERS, ETC.

MULLARD-AUSTRALIA PTY. LTD. Head Office: 35-43 Clarence St., Sydney. Representatives in Aust. for Mullard Electronic Products Ltd., London

MRS-50

the instant of sampling. In other words, the pulses correspond to a succession of red, green and blue dots right along each line.

The individual pulse trains are then fed to low-pass filters, which tend to round them out into a sinoidal wave form having the fundamental pulse frequency and a peak amplitude controlled by the pulse amplitude. These wave trains are passed out to the transmitter and thence to the receiver.

Here the sampling process is reversed and the local sampler, operating in step with the transmitter, extracts from the carrier envelope pulses which closely approximate the original pulse and color values. The picture is thus built up again from an enormous number of color dots, which shift their position each frame to give an overlap effect.

FINER DETAIL

But what of the high frequency components which were removed from the video signals by the low-pass filters? These higher frequencies, representing the fine detail of the picture are combined to form what is virtually a monochrome detail pattern and fed to the transmitter in the normal way as the outer sidebands.

At the receiving end, these outer sidebands are used to impose a monochrome detail pattern over the color pattern. The ultimate result is somewhat similar to a printing process which imposes black lines and shading over the three basic color inks.

For the system, R.C.A. has coined the term "mixed high" transmission.

All this is very involved, in terms of color receiver design. However, a black and white receiver is largely unaware of the machinations with dots and sidebands. It accepts the video carrier on its face value and proceeds to reproduce an ordinary black and white picture. Hence the compatibility.

It appeared, not so long ago that R.C.A. had the game pretty well "taped" but apparently their progress or the final result is not in line with F.C.C. expectations. They are obviously not prepared to sit by and watch experiments much longer while the American public continues to buy standard receivers.

BRACKET STANDARDS

In an attempt to buy time, the F.C.C. has now circularised manufacturers and asked whether they are prepared to release new television receivers incorporating what they have called "bracket" standards. In the main, these new receivers would have a switch which would change the line frequency from 15,750 to 29,160 per second and the field frequency from 60 to 144 per second, the latter figures in each case being in line with the standards proposed by C.B.S.

This would mean that, for the time being, such receivers would be used with the switch set for the present standards. Indeed, should the F.C.C.

system, the alternative provision would never be required.

However, if the decision went in favor of the C.B.S. frame sequential system, the switch would simply be flipped over the other way and the receiver would operate immediately to produce a monochrome version of the C.B.S. color picture. A single adaptor would then serve to provide for color reception.

By this proposal, the F.C.C. obviously hopes that at least some purchasers will be saved the experience of having their sets become partially obsolete overnight. They probably hope, too, to build up an immediate and potential monochrome audience for possible C.B.S. color transmissions.

Unless the industry indicates its willingness to fall in with this plan—and the deadline has already expired—the F.C.C. has said that it will immediately terminate the period of initial research and give the green light to Columbia and its standards. This would mean that television manufacturers could, if they wished, go ahead with new combination receivers based on the frame sequential system.

ELECTRONIC PICTURES

Apparently R.C.A. and other companies are not overmuch concerned by this development, since production of receivers to the "bracket" standards will give them the extra time required for further research.

Whichever way it goes, R.C.A. and the other big tube manufacturers will have their hands full, because it is almost certain that electronic television will win out, irrespective of the standards involved.

Up to date, to produce an electronic color picture, it has been necessary to use three separate picture tubes, their output being combined and viewed via a di-chromatic mirror system. There are obvious difficulties in keeping the three images in perfect register since, in addition to ordinary optical difficulties, the scanning currents must maintain the three pictures to exactly the same proportions at all times.

The optical difficulties were removed by producing a tube having a screen made from countless pyramidal structures, each face covered with a phosphor giving a characteristic red, green or blue glow. Cathode-ray beams from three separate guns, impinging on these distinct faces, built up the complete picture. Problems of electrical registration and trapezium distortion still remained, however.

RCA licked these by producing its three-gun tube, as recently mentioned in these columns. Three gun-structures are mounted side by side to produce three separate beams, simultaneously focused and deflected by coils over the neck of the tube.

PICTURE SCREENS

The beams impinge, from slightly different angles on a plate just be-

hind the fluorescent screen and covered with a complex pattern of fine holes. The fluorescent screen is made up from countless triangular patterns of colored phosphor, so arranged that each color dot is affected by the beam which approaches it from a particular angle through the screen.

The beams, separately modulated, go on their merry way, each exciting its own color dots to a greater or lesser degree and thereby building up the complete color picture.

A refinement of this uses a single beam which is rotated magnetically at a high speed, so that it appears to come from three different directions at the precise intervals in time, thus doing the work of the three separate beams.

MASKING PLATE

The job of piercing a masking plate with tens of thousands of precisely positioned holes and then placing behind them a maze of triangular phosphor dot patterns is one which staggers the imagination. And this has to be done, not for the half dozen experimental tubes produced to date, but for the millions of picture tubes which will ultimately be required, and that at a moderate purchase price!

Be that as it may, the tube manufacturers are apparently quite happy to go ahead on that basis and produce the three color picture tubes the industry will need.

And it will need a lot of other tubes beside, for the addition of color in any form calls for more circuits, more adjustments, more tubes and more things to go wrong.

We hope this more or less technical recital has not proved wearisome, but to appreciate the color position, it is really necessary to have some idea, however general, of the main technical points involved.

One thing is fairly obvious from the FCC decision. It is impossible yet to clarify the path to eventual color. The industry has, in fact, been told to try again. But in case CBS should win, at least those sets made under "bracket" standards won't have to be thrown out. If RCA should win, then all sets including bracket sets, can be used. For this reason, it is possible that the FCC secretly hopes RCA will win, but hasn't overmuch confidence that it can do so, at least on its present lines.

AUSTRALIAN PLANS

How does all this affect our Australian plans? At the moment, not at all. We won't be faced with the necessity for such a decision until we are ready to manufacture sets and transmitters for a permanent service. Nor will the outcome one way or the other affect the wisdom of erecting a couple of experimental stations to "get the feel" of television and carry out vital field research.

It underlines once again the need for this experimental approach, and the disastrous results which could follow the acceptance of any standards offering at present as a basis for a permanent system.

Filling a long felt want—

Slade's Radio Pty. Ltd.



MODEL 508

makes available to
Radio Dealers and
Home Constructors a full range of
Console Radiograms and
Combinette Cabinets.


*Made from best quality
Maple and Italian Walnut-
veneers, finished with a
brilliant piano finish.*

Model 508 is suitable for all types of
Record Changers.

Model 509 is suitable for Single Motors.
Dial fits on front of Cabinet Lid being lifted only
for record playing.

Model 510 is a Combinette type Cabinet
large enough to take a 5 Valve D/W Set with a
Single Motor.

EXPERT PACKING FOR OUT OF TOWN DELIVERIES.

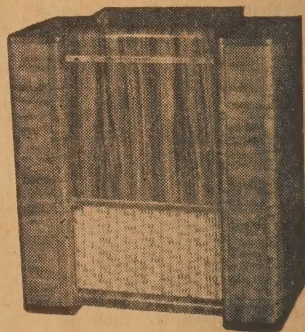

Model 509

*Let Slade's Radio or their Suburban Dealers show you how
cheaply you can convert your old Radio Set into a modern
Radiogram.*

**DAILY DEMONSTRATIONS OF FREQUENCY
MODULATION AT OUR FACTORY**

SLADE'S RADIO PTY. LTD.,

Lang Street, Croydon, N.S.W.—Tel. UJ5381-5382.

ESTABLISHED ————— 30 ————— YEARS.

MOBILE RADIO FOR MOTOR CYCLES

A Frequency Modulated, crystal controlled equipment operating on a spot frequency within the 68.0-100.0 Mc/s. band consisting of a 6 volt, 10 watt R.F. output transmitter-receiver, has been introduced by The Plessey Company, of England, especially designed for use on motor cycles.

A SELECTIVE calling system is available whereby one, or all, of ninety units, each consisting of one or more vehicles, may be called from the control station. This system can be supplied either to "lock-out" all stations not being called, or to allow these stations to interrupt communication between the fixed and a mobile station should it be necessary. Notification of an incoming call is given by a bell or buzzer and a lamp.

Installation is neat and unobtrusive, the receiver with selective calling, transmitter and power unit being combined within two waterproof cases mounted on either side of the rear wheel. Every effort has been made both to distribute the weight evenly and to keep the centre of gravity low.

POWER LOW

Power consumption on "standby" is claimed to be as low as 18 watts, service being about 20 miles, dependent on terrain and installation conditions, when operating in conjunction with a 20-watt control transmitter.

This 27 valve equipment is crystal controlled throughout, and therefore requires no adjustment in operation. Sensitivity is 1 microvolt carrier input for 10 dB quieting. Spurious


responses are at least 60 dB down on wanted signal. Fully tropicalised in accordance with RCS 1000, all com-

ponents are suitable for use within the temperature range -40°C to plus 71°C with humidity as stated for K110.


It is stated that use of a low multiplication factor obtainable with the recently developed Plessey modulation technique virtually eliminates the radiation of spurious frequencies from the transmitter. Frequency deviation is plus/minus 15 Kc/s.

What does the earth look like from Mars? Actually, clouds and haze in our atmosphere constantly obscure most of the earth's surface. Some color would appear from time to time; and our polar ice gleams brighter than other areas when the sun strikes it. Proportionately, the earth's surface is smoother than that of a pingpong ball, although we have peaks, such as Mt. Everest, measuring up to 11½ miles high.

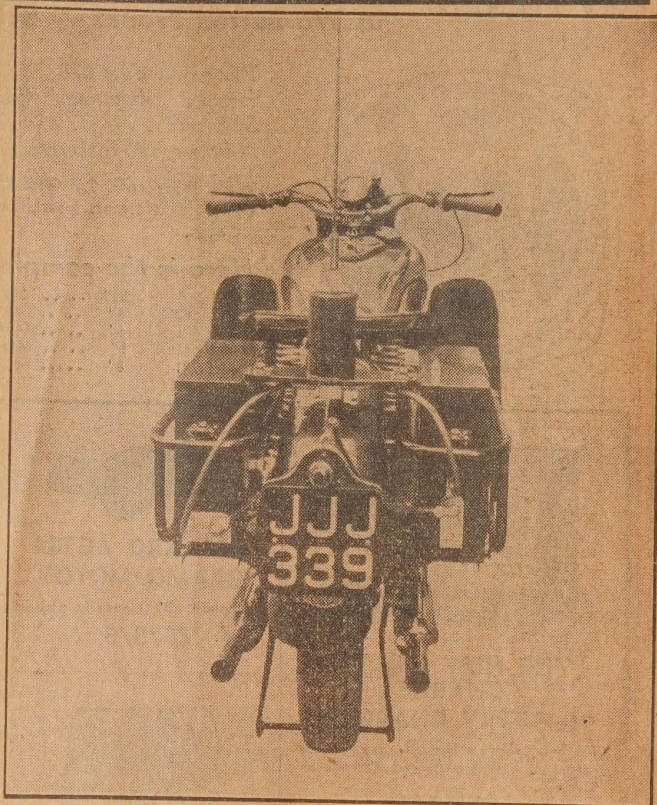Here are the units which make up the complete motor cycle equipment.




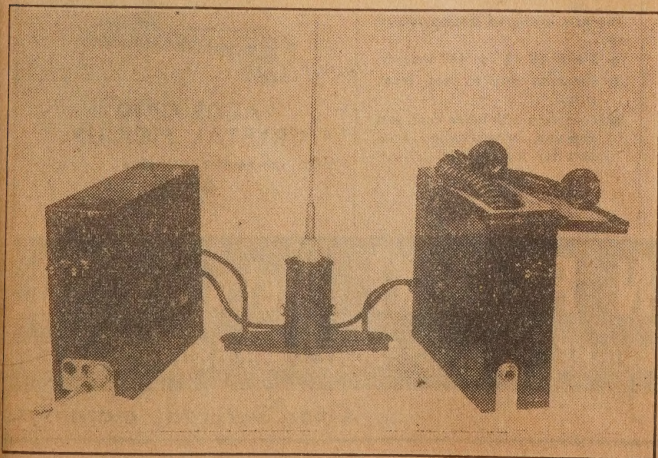The equipment is carried in two cases mounted one on each side of the cycle. The aerial unit is carried on the luggage rack.



A NEW MODEL "MAGNAVOX" SPEAKER IS HERE

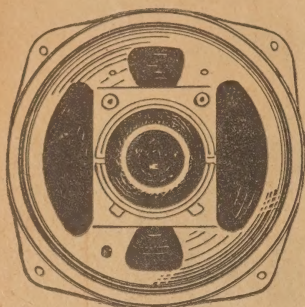It has recently joined the big "Magnavox" range at Warburton Franki — Sole Victorian Distributors.




This new model 525, 5 $\frac{1}{4}$ " size, is the latest addition to the famous "Magnavox" Centre Pole series of Permagentic Speakers and it incorporates all the renowned "Magnavox" features:—

- All voice coils 2.7 OHMS.
- All transformers interchangeable.
- Permanent cone alignment.
- Damaged cones easily and speedily replaced.

Here is the complete "Magnavox" range:—


Model 525	5 $\frac{1}{4}$ "	33/8	Model 10P2	10"	49/3
Model 6P2	6"	40/-	Model 10P1	10"	53/3
Model 6P1	6"	43/-	Model 12P2	12"	52/11
Model 8P2	8"	41/11	Model 12P1	12"	59/1
Model 8P1	8"	46/1	14/60 Filter Chokes		8/11

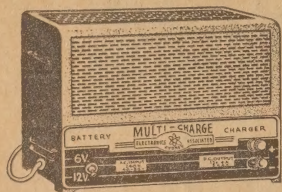

THE NEW MULTI-CHARGE BATTERY CHARGER

The only selenium type charger with an output of both 6 volts and 12 volts at 4 AMPS.

£8/19/6

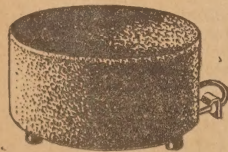

"MYTI" DISPLAY TURNTABLES

8" carries 112lb. £11/5/-

12" carries 175lb. £15/8/-


TRADE ENQUIRIES WELCOMED.



COLLARO AC504 GRAMO MOTOR

Complete with magnetic pick-up

£5/8/6

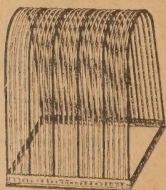

RECORDEX

The new improved Gramo record rack.

- Holds 25 10" or 12" records.
- Engraved easy to read index strip.
- Complete with index card and gummed identification numbers for the records

25/-



GOLDRING REPLACEMENT HEADS FOR GARRARD UNITS

Converting even old Garrard Changers (RC4) to high fidelity reproduction. Available as follows: G1. Using miniature sapphire or steel needles. Output .3 volt. Frequency range [30-8000 cycles]. Needle pressure 1 oz. • 55/9

G2. Using standard size sapphire or steel needles 45/3



ACOS GP10 CRYSTAL PICK-UP

With unbreakable cartridge

48/6

WARBURTON FRANKI (MELB.) LTD.

380 BOURKE ST., MELBOURNE, C1. . . . PHONE : MU 6355 (8 LINES)

Trade also supplied.

Open Saturday mornings.

THIS LINER JUST CANNOT ROLL

THE rolling of a ship which takes place as the ocean swell sweeps under the hull means that one side is lifted as the water level rises, only to be depressed a little later during the passage under the hull of the trough between each "wave."


If some method could be devised which prevented this rise and fall of the ship, it obviously would not rock. Treatment of the ship itself seems indicated because so far no one has thought of a method by which waves can be ironed out flat in the immediate vicinity of the ship.

Most people are familiar with the method by which an aircraft is made to bank either way when the ailerons on the wings are raised and lowered. By providing a pair of "underwater wings" with a variable angle of incidence, this angle being automatically adjusted according to the amount of roll to be corrected, a Scottish firm has succeeded in keeping a ship on an even keel.

DENNY-BROWN SYSTEM

While steaming at 19 knots off the Isle of Wight, the new 24,000-ton P. & O. liner RMS Chusan was forcibly made to heel over many degrees to port and starboard. She was then brought back to an even keel by the "Denny-Brown" system of stabilising fins, fitted for the first time to a luxury passenger liner.

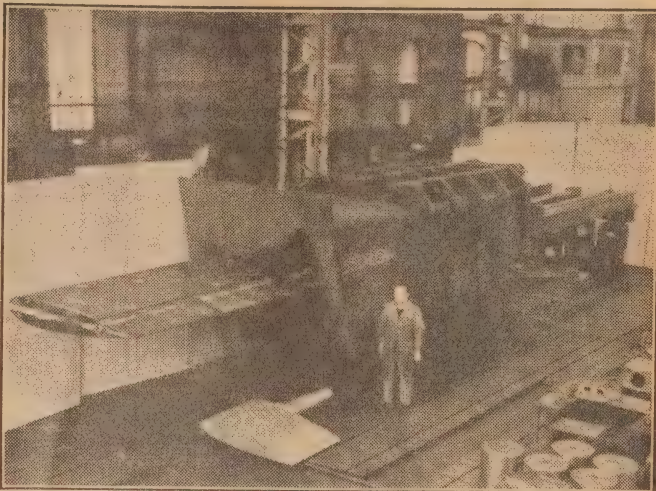The intention was to demonstrate the working of the "Denny-Brown" stabiliser by the manipulation of fins on each side. The stabiliser has been adopted successfully for cross-Channel ships and has been fitted in many destroyers of the Royal Navy. It was perfected during the war and installed in over 100 naval



This picture shows the stabiliser fin for the port side of the Chusan before installation.

The stability of ships at sea has always been a major problem to designers and ship-owners alike, as the millions of sufferers from sea sickness are able to testify. This new device promises to eliminate roll even under severe conditions, as demonstrated by the trials described here.

craft, none of which, however, exceeded 3600 tons.

The stabiliser consists of two fins fitted at bilge level which are retractable when not in use. The principle on which it operates is that two rectangular fins lie approximately horizontal in the same horizontal plane, each fin mounted on a shaft so arranged that it is hydrodynamically balanced. In operation, the fins

tilt about the gyro position and are controlled so that their angular movement is equal and opposite.


The forward movement of the ship causes an upward force of water on one fin and a downward force on the other, thus combining to reduce any roll produced by wave action. The control is automatic and is operated by two small gyroscopes, one measuring the angle of the roll and the other its velocity.

On trials carried out, Chusan was made to roll—by reversing the stabilisers—and left the vertical by 17 degrees on either side, yet this roll was killed in six seconds. Complete success of the stabiliser opens up new possibilities of stability for ocean-going liners in the roughest seas and gives new hope to world travellers who suffer from seasickness.

HIGH frequency radio warning equipment patented recently can give the engineer of a speeding train a continuous indication of whether another train is on the track ahead, and how far away it is.


The equipment is designed to supplement the usual safety system on US railroads.

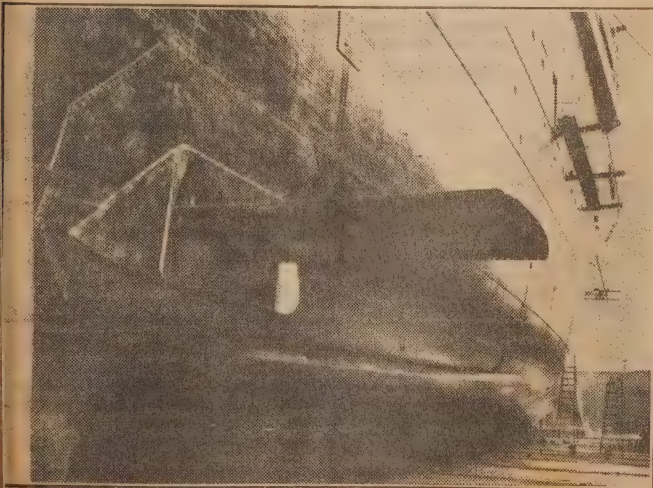The starboard fin, which measures 12ft. in length and more than 6ft. in width. Fins are retractable.




It's New... It's News!..

The AEGIS Windowmount Aerial.

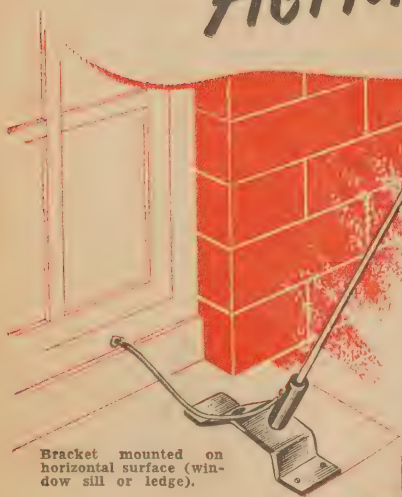

Bracket mounted on horizontal surface (window sill or ledge).

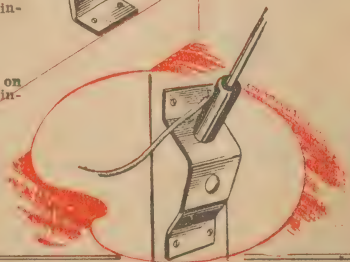Bracket mounted on vertical surface (window frame or wall).



Here it is . . . the lowest priced practical aerial on the market! An innovation that will be welcomed by hobbyists and Radio enthusiasts alike! . . . ideal for flats and private homes, the "Windowmount" aerial is neat and compact, being adjustable to any fitting. The efficiency standard is such as to make all other type aerials obsolete!

LIST PRICE

30/-

CONTENTS OF PACK

One Mounting Bracket.
Three Section of Aluminium
Aerial Rod with Insulator.
Four Fixing Screws.
25ft. Insulating Lead-in Wire.

Obtainable from
Distributors in all States

AEGIS

MANUFACTURING CO. PTY. LTD

208 Little Lonsdale Street, Melbourne, Victoria.

BATTERIES DRIVE JAPAN'S JEEP


THE battery idea probably had a number of disadvantages which prevented it from making much headway against petrol driven cars. But in Japan, at least, it appears to be making a comeback in one of those fantastic ways, which are so crazy that only the Japanese, who doesn't know it can't be done, makes it work.

The cars are built by the Tokio Electric Automobile Company, according to reports, and will run 125 miles without a battery charge. As it would be bad practice to flatten batteries anyhow, between charges, it's pretty certain that when the car is finally parked for the night, the owner plugs the charger into the appropriate socket, and tops them up during the night.

The car comes in two models. Whether it is the Japs' love of small things, or whether it costs too much to make big cars, at any rate the larger of the two Tamas is about the same size as the jeep, or a little smaller. As the illustration shows, however, it is a sedan job, and would probably look pretty smart bowling along at a top speed of 33 miles per hour.

There are, however, still more amazing things about this car. It is entirely hand-made. The body is made of wood as a framework, after the style of the 1920's, after which the metal body panels are hand-fitted. There is no heavy machinery — each car is actually "custom built." This is made possible, because in Japan, labor is still obtainable at a cheap rate.

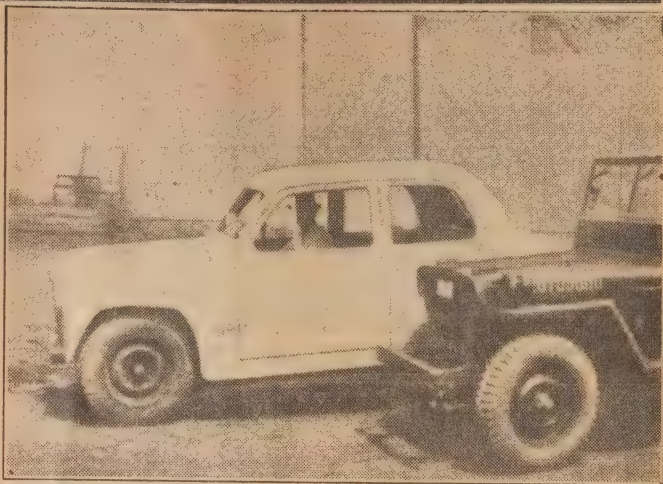Once the body is assembled, it is mounted on a wooden dolly, and rolled round from department to department, until the final assembly



The Tama Senior is shown here alongside an American jeep demonstrating that it is actually smaller in size. A second model is even smaller.

It is not so long ago since a strange motor car was seen regularly in the streets of Sydney, if indeed it is not still in use. Its progress was smooth, silent, and stately. The reason—it was driven by an array of batteries, and filled up from a mains plug each night instead of at a petrol pump.

is complete. The worker, who makes each part, also installs it. The factory makes everything except the wheels and the electric motor. The upholstery is also done by another firm.

Painting is done by hand, and the pigment for the paint is actually ground at the factory.

The greatest flexibility is possible

in this manufacturing method, for there is little difficulty about making modifications or changing a model. Everyone just agrees to hammer out a part in a different way, or to fit a panel with a different curve, and there you are! Tooling up is a thing of the past, or is it the future?


Naturally, the factory hasn't a huge output — about 30-40 cars per month. And the price isn't really low — about £800 for the larger model. It makes one wonder, however, just what the price would be if a modern factory got to work on a similar car. In the meantime, the patient Jap turns it out by hand.

ELECTRONIC FERTILITY DETECTOR TESTS EGGS

ELECTRONICS may soon tell poultry-farmers which eggs are fertile, thus eliminating the present trial-and-error method of incubation. All that is needed, according to Karl Norris, of the US Department of Agriculture, is an instrument to measure minute differences in response to electric current. Fertile eggs respond differently from non-fertile eggs. Modern electronics may soon produce a practical device for measuring the few millionths-volt difference that shows fertility, Norris says.



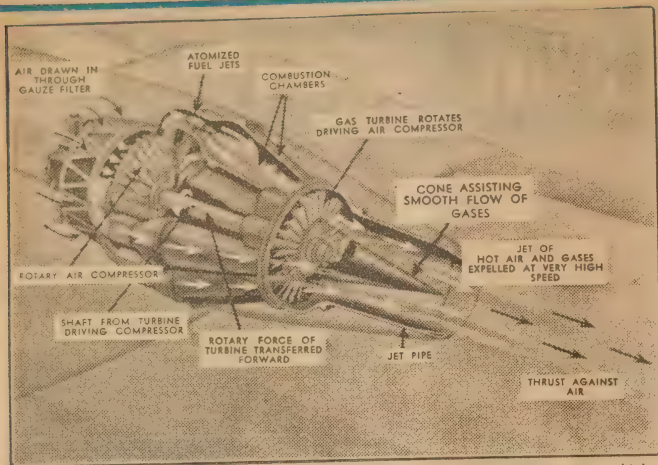The batteries which drive the car are shown in the picture at the left, housed under the bonnet. At the right is seen the grinding of pigment to make the paint.



The jet engine, big news in today's aviation, depends on a simple principle which is not always understood.

WHY DO THINGS HAPPEN?

Despite the complexity of man's machines they depend in the main on quite elementary rules of physics. This article discusses simple examples which illustrate the operation of these rules.

ONE of the reasons why science is unpalatable to many people is the difficulty which they find in understanding the language in which many of the scientific laws are framed. To attempt to imagine, or form a mental picture of, the results of a law is difficult. Thus the job is given up, and what could be a most interesting subject is lost to an otherwise earnest investigator.

All of us remember the way in which, at school, we mechanically carried out the physical experiments as laid out in the text-books.

Unless one had a "flair" for the subject, our experiments were considered somewhat in the same light as a meal consisting wholly of spinach garnished with castor oil.

MIXTURES AND SMELLS

The most interesting matters were, of course, those which led to something concrete, such as mixing up some sort of explosive with which to frighten the life out of the teacher or an unsuspecting schoolmate.

Our chemical experiments became matters of great interest when we found out how to make the most abominable smells with iron sulphide and hydrochloric acid. These things had prospects.

Then, of course, we found that we could, with a little phenolphthalein mixed with water, cause this colorless liquid to turn red—then colorless again by adding equally colorless solutions of soda or vinegar, as the case may be. This was magic,

and possibly gave the answer to many of the tricks performed on the stage by the great conjurers. Beyond this many of us considered chemistry and physics as subjects to avoid.

In this age of science, however, there are many who now wish they had taken a little more interest in the subjects. The newspapers, day after day, reveal more and more amazing scientific excursions, and we now feel that a little knowledge of the laws of science would enable us to understand the whys and wherefores of the matter.

SIMPLE EXPERIMENTS

Fortunately, there are some simple experiments which any enthusiast can perform which will demonstrate the principles involved and sometimes help to remove some misunderstandings.

For our first example we will select Newton's third law of motion. What could sound more uninteresting than the bald statement that "to every action there is an opposite and equal reaction"?

Yet here is the law upon which the science of jet propulsion is based.

by Calvin
Walters

Have you ever jumped out of a rowing-boat on to the shore? You have probably noticed that, when you jump, the boat sails off in the opposite direction. Indeed, most people who have rowed boats have had the alarming experience of having one foot on the shore and one in the boat and being left in a precarious and incongruous position, doing the "splits," with deep wet water beneath.

This is an example of Newton's law. In order to jump forward you also pushed backward with the same force.

REACTION

Another example is the recoil of a gun or the unrecommended method of forcing tomato sauce out of a bottle by bashing the end of the bottle.

In order to witness the force of reaction, you can obtain a bottle two-thirds full of acidulated water. This can be done by putting some

vinegar with the water—about a ounce of vinegar will do.

Put the bottle on a pair of household scales, drop into it a small quantity of alkali, such as baking soda, wrapped up in absorbent paper and cork the bottle.

As the soda contacts the vinegar carbon dioxide gas will form and gradually fill the space in the bottle. Watch closely until the pressure of gas shoots the cork from the bottle. When this happens, the scale will be depressed by the reaction on the bottle.

Some people have the idea that a jet plane or rocket is propelled by the force of the jet pressing on the air. This is a common fallacy.

If this were so, rockets could not be propelled past the earth's atmosphere, where there is no air to push against.

REACTION MOTOR

What happens is that, obeying the law of reaction, the hot gases emanating from the nozzles at the rear tremendous force must also push forward on the front of the machine thus propelling it forward. This is nothing new about jet propulsion. Hero of Alexandria, who flourished about 100 to 150 years BC, thought up the idea and made a novel engine which he called an aeolipile.

This gadget took the form of a hollow ball, from which tubes, at backwards, protrude at opposite diameters. The whole affair was pivoted at the centre and when wa-

was heated in the ball the steam coming from the tubes caused the assembly to revolve. Today the counterpart of this device exists in the revolving garden lawn sprinkler.

A simple jet engine can be made by taking a talcum powder tin which has one of those screw-on tops. Tighten the lid and punch a small hole in the bottom near the edge. Put some water in the tin first. Bend up some wire and wind it round the tin so as to make four legs. Stand this boiler in a light aluminium soap dish floating in the bath. Put a piece of lighted candle under the boiler and when the water boils and steam issues from the hole in the tin the "boat" will sail along in the opposite direction to the steam.

THE SWERVING BALL

Steam cannot issue from the hole unless it presses on the front end of the tin. Opposite and equal reaction. By the way, don't have the water boiling too fiercely and see that dad supervises the experiment, so that the tin won't blow up. Just have the boat going long enough to see what's happening. If you want to make a better outfit you will have to fit a safety valve.

Over 200 years ago a smart fellow named Daniel Bernoulli discovered forces which are responsible for quite a few well-known effects, such as the curved flight of a tennis, golf, or ping pong ball which has been "sliced." The action of a paint spray, garden spray, and all such devices, also depends upon these forces, but most important perhaps is the fact that the aeroplane gets its lift because of these self-same forces.

The clever Bernoulli formulated a law which is rather difficult to understand when read as written in the text-books. It says, in effect, that when the velocity of a fluid (air is included in this) is increased, the pressure inside the fluid is decreased.

QUESTION OF PRESSURE


There doesn't appear very much in this at first sight. It is hard to believe that the pressure on the inside of a hurricane is less than that outside.

There are two kinds of pressure to consider. First, there is "dynamic" pressure and secondly static pressure.

The first is the pressure developed when the fluid collides with something and the second is the pressure of one particle against another inside the fluid. It can be demonstrated that


dynamic pressure rises with increase of velocity and static pressure falls in proportion.

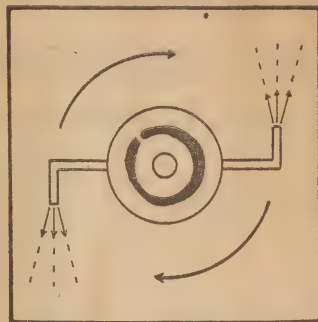If you suspend two balls, about 1½ inches apart, by fairly long cords and blow between them you would expect the balls to fly apart, but they don't. They come together. You create a region of low pressure between the balls by blowing through the gap



The common garden sprinkler shown simplified above operates on the jet principle.

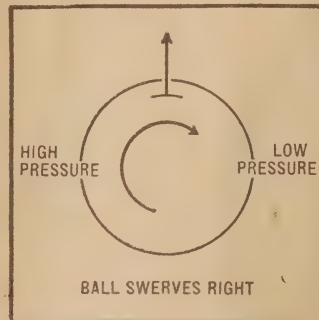and the normal air pressure on the outer sides of the balls pushes them together.



This diagram illustrates the "swerve" of a tennis ball.


The same thing is responsible for the action of a toy balloon when placed in a strong current of air.

Fix up your vacuum cleaner so that it blows instead of sucks.

You can do this by connecting it up as if you were intending to use the sprayer attachment. Turn the

vacuum cleaner on and place a toy balloon in the draught of air.

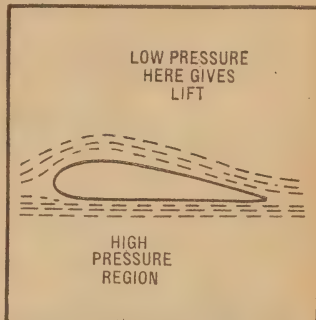The balloon will stay suspended in mid-air. Why? Because every time it tries to get out the high pressure outside the air stream pushes it back into this higher speed low pressure air. Of course, the air stream will have to be directed upwards at an angle, otherwise the force of gravity



It is the low pressure above the aircraft wing which causes it to lift.

will overcome the velocity of the draught of air and pull the balloon down.

When a tennis ball is "chopped" or a golf ball is "sliced," it is given a spinning motion. This spin carries the air around with it so that on one side of the ball this air is moving in the same direction as the current of air caused by the forward rush of the ball. On the other side the air carried round with the ball is moving against this forward air current. The result of all this is that on one side of the ball the total air velocity is faster than on the other side and the ball curves toward the side which has the fastest moving air flowing past it.

In the case of the familiar spray the draught of air being forced across the upper end of a narrow tube produces a region of low pressure across the tube. As this is lower than the pressure of air inside the container and therefore at the lower end of the tube, the higher atmospheric pressure forces the fluid up the tube and it is caught in the draught of air at the top and carried along with it to the unsuspecting mosquitoes.


TOP LIFT

These forces discovered by Bernoulli give most of the lift to an aeroplane. A lot of people think that it is the air flowing under the wing of an aeroplane which gives it the lift. This is quite wrong.

Most of the lift is caused by the air flowing over the TOP which causes this most desirable attribute. Want to prove it? Right. Take a piece of paper about two inches wide and, say, 10 inches long, and hold it between your thumb and forefinger, so that the paper hangs down in a curve over the back of your hand.

Have the palm of your hand facing toward you then blow across your thumb and along the top of the paper. What happens? Did you blow the

(Continued on Page 95)


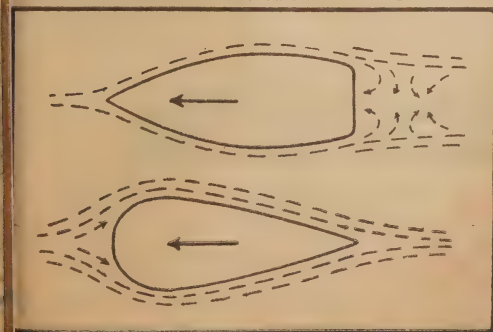


GOODMAN'S LOUDSPEAKERS

As used by AUDIO ENGINEERS PTY. LTD.
In High Quality Reproducing Systems

Make your choice from the following:

AXIOM 80	10W Output 17 to 20000 cycles
AXIOM 150	15W Output 40 to 15000 Cycles
AXIOM 22	20W Output 40 to 15000 Cycles

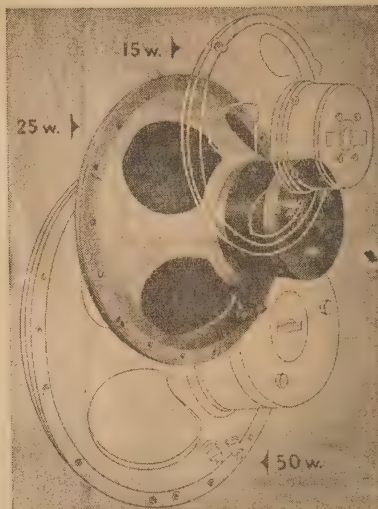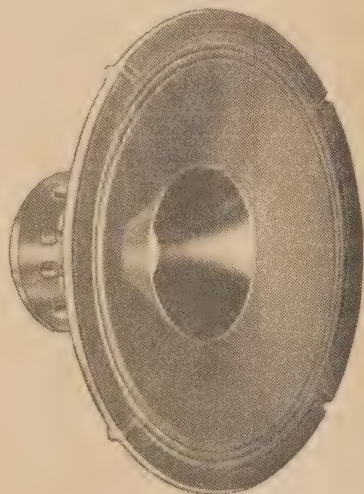

PRICE LIST

AXIOM	80	£27	5	0
"	150	£17	12	0
"	22	£30	8	0
AUDIOM	50	£9	13	0
"	60	£14	3	0
"	70	£25	3	0
"	80	£45	0	0
"	90	£60	15	0
plus minus 1DB 10 to 20000 CPS			£8	4	0
Goodmans H6 Output Transformer 30W					



WANTED! . . . the services of an experienced Technician for design of general Audio Equipment. Vacancies also exist for juniors for general work such as wiring, assembly, installation of all classes of sound systems and Audio Amplifiers. This is your opportunity to learn this fascinating work. Good prospects for the right type of person. Call and have a chat with Mr. R. C. Fitzsimmons or Mr. D. K. Fletcher.

Audio Engineers Pty. Ltd.

422-424 KENT STREET, SYDNEY.

Phones: MA9537 — MA9538

OPEN ON SATURDAY MORNINGS, 9.30—12 NOON.

Victorian Factory Representative: John L. HARROWER, 71 Little Lonsdale St., Melbourne.

Phone Central 8519



Technical Review

OPTAR — A NEW SYSTEM OF OPTICAL RANGING

An ingenious combination of optical and electronic principles, which has earned the name "Optar," was described recently before the American IRE by H. E. Kallman. It has already produced a prototype electronic guide for the blind.

To understand the principle of optar, it is necessary to refer first to the basic optical illustration of figure 2. This depicts a convex lens which produces images whose size and distance from the lens is proportional to the size and distance of the original object. It is, in fact, possible to gauge the size and distance of the object by determining the size and position of the image behind the lens.

The method suggested for determining the image position involves placing a comb-like interrupting vane in the region of focus (see figure 3) and moving it so that it interrupts the light field. The interrupted light falls on a sensitive multiplier phototube, which tends to produce an a-c component, dependent on the interaction of the moving combs and the distribution of light over the field.

OBJECT IMAGE

In a perfectly flat light field, there would be no change in light intensity and no modulation. However the introduction of an object into the field increases the tendency to produce output, the tendency being most marked when the position of the comb coincides with the image of the object in question.

Thus, by moving the comb longitudinally, the point of maximum output gives the image position and therefore the distance from the lens of the object. The measure is primarily one of distance and the dimensions of the object can be gauged by swinging the Optar device through the requisite arc.

For the precise measurement of distance, two combs can be used, slightly displaced from one another and arranged to give a complementary output. Two positions of maximum output are obtained with a null point between them, the null being the significant measurement.

The device for the blind has a disc mounted on a diminutive motor and so arranged that the edge of the disc

lies in the optical field. Around the edge of the disc are marked a number of radial lines arranged in groups and made progressively finer so that they tend to produce about eight separate audio frequencies as the disc spins through the optical field.

The disc is also distorted in such a way that the different line groups spin through the field at progressively different distances from the lens. As a result of this, images at differing distances cause one or other of the frequencies to predominate in a small earphone.

It is claimed that a blind person could soon learn to gauge the distance and movement of objects from

(Continued on Page 51)

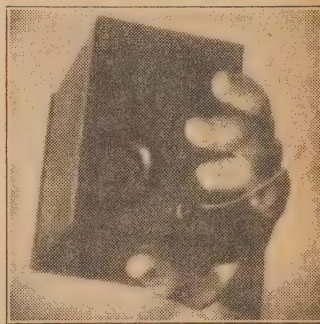


Figure 1. An external view of the device for guiding the blind.

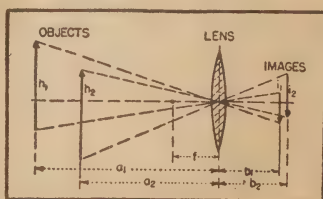


Figure 2. A familiar optical illustration. Optar locates an object by measuring the position of its image.

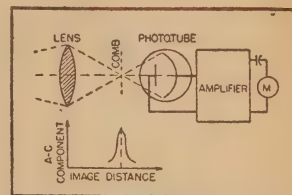


Figure 3. The fundamental Optar system showing how the a-c component peaks when the comb corresponds with the image position.

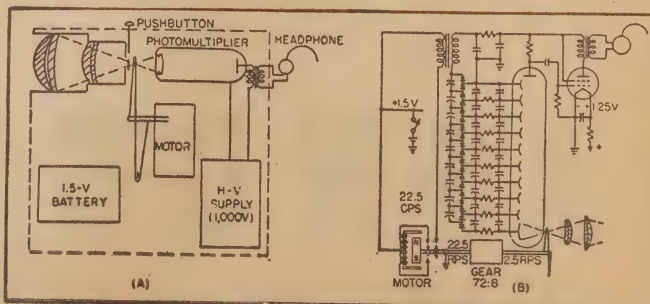


Figure 4. The mechanical arrangement of the blind-guide and, on the right the electrical circuit. All this operates from one torch cell.

here is the

KINGSLEY *KU3-5* ★

***Dual
Wave***

★ **KU3-3**
(6J8GA)

KU3-4
(6BE6)



55/-

***Tuning
Unit***

KU3-5
(X61M-ECH33)

KU3-6
(6AN7)

Procurable from all leading Radio Houses

You Require for the
5 Valve A.C. D'W Receiver

Detailed in this issue

Your I.F. Transformers are
KIF5 & KIF6

KINGSLEY

THE GREAT NAME IN AUSTRALIAN RADIO

3 CORNELL PLACE, CARLTON, VIC. 3154

BUZZER BECOMES 10,000 m.c. GENERATOR

Combination of an ordinary 800-cycle buzzer with a tunable cavity provided research workers with a microwave oscillator tunable over the range 3000 to 11,000 Mc. Output is as much as 200 microvolts across a 200-ohm load.

ONE of the problems of work in this extreme region is that of obtaining convenient signal sources. Accurate single-frequency oscillators can be produced but these have serious limitations for testing receivers covering a wide range of frequencies.

A simple tube-less oscillator has helped solve this difficulty. The initial energy comes from a simple 800-cycle buzzer of the door-bell type which is used to excite an adjustable cavity resonator. The output is therefore modulated at 800 cycles, while the frequency stability is purely a function of the cavity construction.

SCALING

To produce the original instrument, the usual scaling procedure was used in reverse in that a large scale, low frequency model was built up to discover the significance of problems which might be associated with tuning, coupling, output control, &c.

This large-scale prototype, measuring some 22in x 15in overall was made up by the local tinsmith and quickly earned the nickname of "ashcan." It operated in the region 120 to 440 Mc., where there was no shortage of suitable gear for taking performance measurements. Despite the use of ordinary galvanised steel, the "Q" of the cavity was found to be good.

Positions were found for the coupling loops and the nature of the oscillation studied over the "scaled up" band it was proposed to cover. Then engineers were able to establish that a closed cavity would be preferable and also to discover the positions slits intended to suppress spurious modes of oscillation.

CURRENT DRAIN


With such problems solved, the final microwave instrument was produced and its performance was found to correspond very closely with expectations. Current drain from the self-contained batteries is from 50 to 150 milliamps, giving at least 300 hours of operation, with no problems of heat-up time, maintenance, &c.

The simplicity of the scheme is evident from the schematic circuit. The buzzer, energised from a 3-volt battery produces sharp pulses of current, which are coupled into the cavity through the coupling loop. The cavity is sharply resonant at one particular frequency, as determined by the plunger position.


Harmonic components in the buzzer output excite the cavity at its reson-

ant frequency, so that it produces constant oscillations which are picked up by the coupling loop and fed out through a piston-type attenuator.

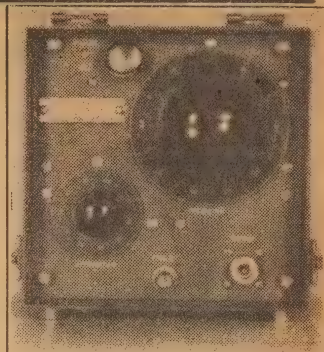
The buzzer produced pulses comprising a 5-amp breaking current through the contacts, with a 200 volt peak across the coil. It was necessary to select a type which gave a suitable operating frequency but with a clean make-and-break action. Some buzzers were found to exhibit "bounce" in the contacts, producing a virtual wave train rather than a single steep wave front.



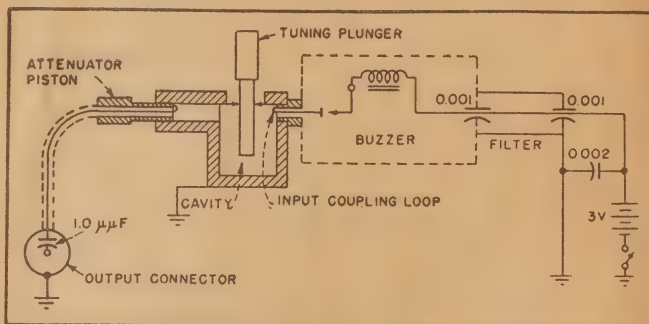Front view of the instrument showing the dial at the top right and the attenuator on the lower left of the panel.



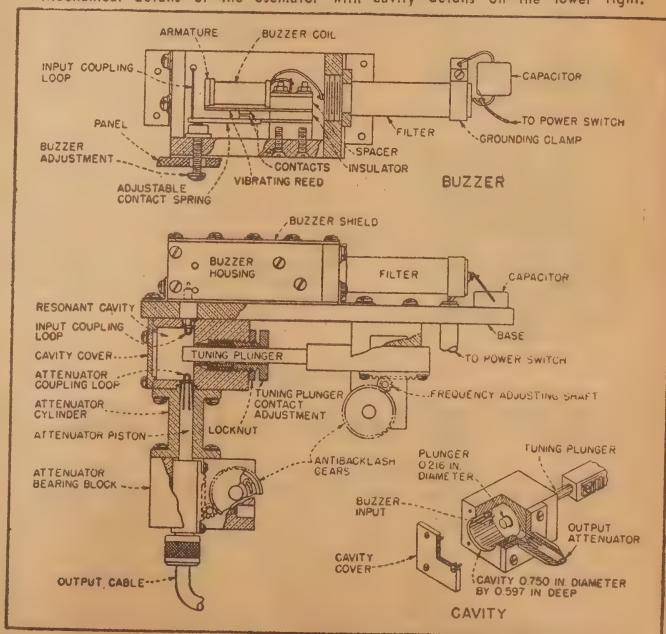Mechanical details of the oscillator with cavity details on the lower right.




An equivalent electrical circuit for the buzzer-oscillator.

SOLVE YOUR PROBLEMS WITH TAYLOR TEST EQUIPMENT

MODEL 47A-P

MUTUAL CONDUCTANCE VALVE AND MULTITESTER

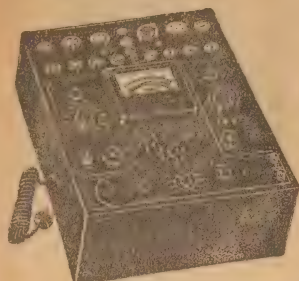

Fitted with large direct reading meter with illuminated dial and OVERLOAD PROTECTION. Tests over 2000 American English and Continental valves including latest types. Filament volts range from 1.1 volts to 117 volts. Filament continuity and element shorts shown directly on meter. The instrument is housed in a solid oak carrying case and supplied with comprehensive instruction manual. Also available as valve tester minus multitester ranges—Model 45 A-S.

MULTITESTER RANGES. 1000 ohms per volt A.C.-D.C.

D.C. Volts	D.C. Current	A.C. Volts	Resistance
0-120 m.V.	0-0.6 mA	0-3	0.5-22.5-1000 ohms.
0-3	0-6 mA	0-15	50-2250-100,000 ohms.
0-15	0-30 mA	0-150	x 500-22,500-1 megohm.
0-150	0-150 mA	0-300	x 5000-225,000-10 Megohms.
0-300	0-1.5 Amps	0-600	x with external battery.
0-600			

PRICE £39/17/6 Plus sales tax.

IMMEDIATE DELIVERY

MODEL 75A

RANGES

20,000 ohms per volt A.C.-D.C.

D.C. Volts	A.C. Volts	A.C.-D.C. Current	Decibels	Resistance
0-0.1	0-1	0-50 uA	-30 to -5	1-50-10,000 ohms
0-2.5	0-2.5	0-5 mA	-22 to +3	1000-50,000-10 Megohms
0-10	0-10	0-50 mA	-10 to +15	*10,000-500,000-100 Megohms
0-50	0-50	0-500 mA	+4 to +29	*With external battery.
0-250	0-250	0-5 Amps	+18 to +43	
0-1000	0-1000		+30 to +55	

This is a robust 20,000 ohms per volt 50 range universal multitester designed for accuracy and stability. Fitted into an attractive case, the meter is provided with instantaneous OVERLOAD PROTECTION. The clear, easy to read scale has a length of 4 inches. An internal buzzer is provided for quick continuity tests. Complete with test leads.



PRICE £19/15/- Plus sales tax.

MODEL 120A POCKET MULTIMETER

RANGES

1000 ohms per volt A.C.-D.C.

D.C. Volts	D.C. mA	A.C. Volts	Resistance
0-0.25	0-1	0-10	0.5-20-2000 ohms
0-10	0-10	0-50	50-2000-200,000 ohms
0-50	0-50	0-250	*500-20,000-2 Megohms
0-250	0-500	0-500	*5000-200,000-20 Megohms
0-500		0-1000	
0-1000		0-2500	*With external battery.
0-2500			

This is an accurate pocket size instrument using a robust, sensitive meter movement fitted with instantaneous OVERLOAD PROTECTION and is housed in a high grade moulded case. All resistors used for voltage and current ranges are adjusted to an accuracy of 1%. Supplied complete with test leads.

PRICE £9/17/6 Plus sales tax.

DIMENSIONS: 4 1/2" x 3 1/2" x 2"

Australian Distributors:

JACOBY MITCHELL & CO. PTY. LTD.

MA5475—MA5058.

Sales and Showrooms 277 Clarence Street, Sydney.

Queensland: CHANDLERS PTY. LTD., Cnr., Albert & Charlotte Sts., Brisbane.

Victoria: J. H. MAGRATH & CO., 208 Little Lonsdale St., Melbourne.

NSW: JOHN MARTIN PTY. LTD., 116 Clarence St., Sydney.

SA: GERALD & GOODMAN LTD., 192-196 Rundle St., Adelaide.

Manufactured by:—TAYLOR ELECTRICAL INSTRUMENTS LTD., GREAT BRITAIN



RADIO IN THE AFRICAN JUNGLE

With so much attention focused on television, it comes as a shock to realise that some countries are still grappling with the problems of introducing sound broadcasting to the population. A recent report from the Director of Information, Northern Rhodesia, outlines the problems of broadcasting in Central Africa.

HIGHLIGHT of the report is the success of the Saucepan Special, a British-built "poor man's radio" designed especially for use in Central Africa. It's acceptance by the native population foreshadows a tremendous advance in their education and outlook.

The big problem of the Rhodesian Information Department, as revealed by the report, is to educate the Central African natives and also to keep them sufficiently well informed to protect them against native agitators. Without radio, the process looked like taking three or four generations, which was far too long a period.

COMMUNITY SETS

On the other hand, broadcasting was plainly futile if the natives lacked receiving facilities and "community" receivers in the ordinary sense were deemed a failure.

The problem, therefore, was to introduce individual receivers to the native homes, remembering that the total monetary income to the majority of such homes barely averaged one pound per month. On the surface, it seemed unlikely that any receiver could be marketed which would be within the purchasing power of such folk.

However, a search was made throughout Britain and the Dominions for a possible source of supply and, ultimately, one large British manufacturer decided to investigate the matter and produced a few pilot prototypes retailing for £5 each.

These were immediately sold to African buyers and a subsequent check showed that they were well received. Accordingly an initial order was placed for 500 more receivers for the African population, 1500 sets for official use and with sufficient future promise to warrant setting up a full production line.

In actual fact, the full initial consignment of 2000 sets was sold privately and there was an immediate and outstanding demand for further stocks.

LOW PRICE

Many factors assisted in creating this demand. Low profit margins for the distributors allowed the receivers to be sold for £6/5/-, including batteries, while a transport company undertook to deliver them over all their motor lines free of cost. Government loans were arranged to assist public servants, while natives often "pooled" their salary to make the purchase. Many could afford to do this because the

small communities are fairly self-sufficient in regard to dwellings and food.

The total population of Northern Rhodesia is a million and a half and, apart from those living in industrial centres, it is spread out in some 20,000 villages, each comprising a dozen or so family huts. Initial target is to see at least one family receiver in each village.

switch and volume control and below it the two-speed tuning control and tuning dial. There is no tone control or other refinement.

"The set stands on black bakelite knobs, the tuning dial is white, the appearance of the receiver is more attractive than one would imagine. It is painted blue since research in the various colonies in Africa revealed the fact that one tribe or



Our artist's impression—the "Saucepan Special" brings Radio Lusaka into an African village.

At the present time some 300 sets per month are being sold and, allowing for ten listeners to each set, the radio audience is growing at the rate of about 3000 listeners per month.

At the present time some 300 sets casting takes place on short-waves and the "Saucepan Special" is therefore a short-wave receiver only. It will tune the normal range of short-wave stations in addition to the popular local African station Radio Lusaka. Technically, the set is described in the report as follows:—

THE RECEIVER

"The Saucepan Radio is a simple but efficient short-wave receiver operated by an external dry battery of 90v. HT and 1½v. LT which gives 300 hours' service.

"The cabinet of the receiver is, in effect, a large aluminium saucepan (without handle) of nine inches diameter with a back plate attached by screws and sealed, and a gauze-covered opening at the front of four inches diameter. Above this opening is the combined on-off

another had some kind of superstition about almost every other color. The back plate is tight fitting and the three holes in it are gauze-covered, so that the set is entirely insect proof. It is also tropically finished throughout.

"The receiver is a formal (though simplified) four-valve superhet type. Its range is from 25 to 90 metres. The aerial and earth wires are attached to the set, and it is important that the earth system should be used with this receiver. Before the sets are distributed a small copper plate is soldered on to the earth wire which should be buried about nine inches in the ground.

"The receiver and the battery, which is about 8 inches by 3 inches by 5½ inches, each weigh just over seven pounds.


SERVICE TROUBLES

"The aerial wire supplied could with advantage be lengthened."

Experience in handling the receivers has shown minor failings in the construction and packing ar-

(Continued on Page 89.)

two of the best ...

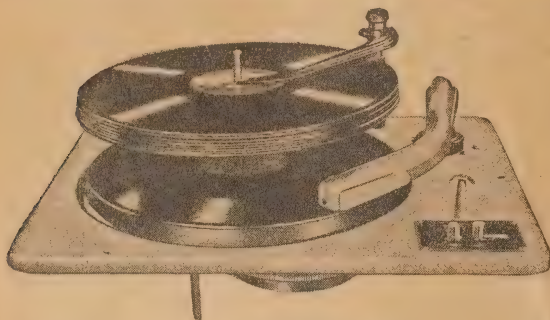

★ *SIMPLICITY is the secret
of COLLARO success.*

RC500 "COLLARO" the world's best record-changer

Check these outstanding COLLARO advantages against any other record-changer.

1. With only three moving parts the COLLARO always remains in adjustment and cannot jam.
2. Plays nine records, either 10" or 12" as selected.
3. Amazingly quick and easy... to load... to play singles... to reject... to unload... to stop,
4. Crystal or high fidelity moving pick-up
5. Incredibly light needle pressure.
6. Twin ball-race pick up mounting.
7. Triple twin-spring mounting of entire unit.

The best on record ...

*Also available in straight and
midjet light-weight types.*



Sole Australian Agents

ELECTRONIC INDUSTRIES IMPORTS Pty. Ltd.

(Division of Electronic Industries Limited)


666-670 Chapel Street,
South Yarra. BJ1227.

52 Bowen St.,
Brisbane. B7161.

147-149 Castlereagh Street,
Sydney. M6031.

90 Grote Street,
Adelaide. Cent. 1780.
EI/2458

HOW IT WORKS-ROTARY EXCAVATOR

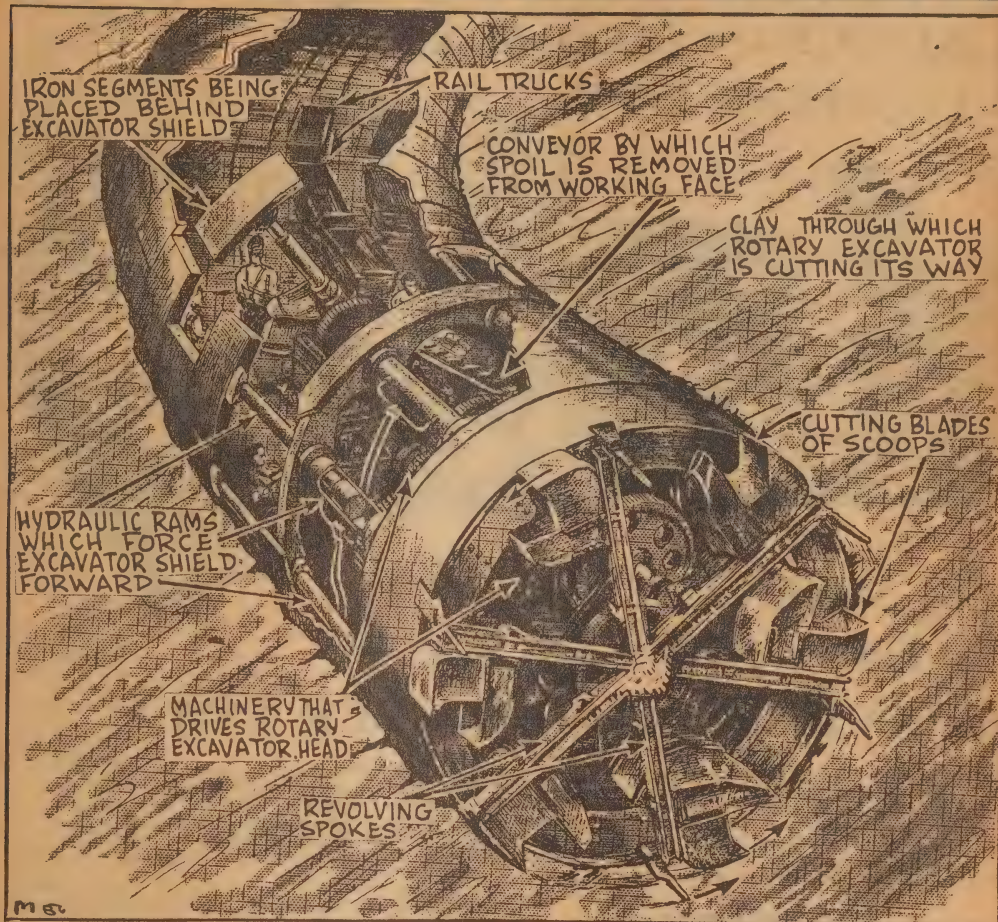

Modern engineering methods have greatly simplified the problems of tunnel-making, and special devices and methods have been developed to deal with the construction problems met with. There are, broadly, three types of tunnels—those driven through hard rock, those driven through mixed soil and rock, and finally those through very soft rock or clay.

IT is a little over a century since the famous engineer Marc Isambard Brunel introduced a shield to expedite tunnel boring. The shield was constructed to the full diameter of the tunnel. It was kept pressed against the working "face" and, in the open compartments into which it was divided, men worked with pick and shovel.

By present standards, Brunel's shield was primitive, cumbersome, and not too safe. From it have been evolved wonderful tunnelling shields, however.

The remarkable rotary excavator, for use in tunnelling through clay, is illustrated here. This excavator bears some similarity to the snow plough as well as to Brunel's tunnelling shield. Rotary excavators

such as this have been used to a considerable extent in tunnelling through London's clay.

Forced forward by powerful hydraulic rams, the electrically-driven rotary excavator head uses mechanical cutters to remove the spoil from the working face.

The spoil is thrown back and fed to the conveyor, which in turn carries it back to the railway trucks that operate within the finished section of the tunnel.

The hydraulic rams that force the excavator forward press against the iron segments of the tunnel already fixed in position behind them.

The direction of forward movement is controlled by regulating the force exerted by the individual rams. Thus the tunnel may be driven

straight forward, or may be curved to left or right, or sloped upward or downward, according to the requirements of the prepared plans. For driving curves, pressure is exerted by the rams on one side only. For downward slopes, the pressure is exerted only by the rams on the upper segment, and for the upward slope by the rams on the lower segment.

Excavation of a tunnel may proceed simultaneously from both ends of the tunnel in order to speed up the work. When the workings meet, they do so exactly because of the accuracy of preliminary calculations.

With a rotary excavator of the type illustrated in this diagram-sketch, tunnelling progress at the rate of 25ft a day is possible.

Q. WHEN DOES A RADIOGRAM BECOME A RECORDOGRAM?



A. WHEN IT'S FITTED WITH A R-12-D RECORDING AND PLAYBACK UNIT!

Convert your Radiogram easily and economically and have all the fun of making and playing your own records. The operation of the R-12-D is so simple a child could use it—a flick of a switch—a foolproof control adjustment and it's ready to record from either a microphone or radio. And the records you make... well, you'll find they're right up to commercial standard for volume and fidelity and can be played back immediately. Recordings can be made at 2 speeds, 33 $\frac{1}{3}$ or 78 r.p.m. and ordinary commercial records are reproduced with crystal clear quality. The R-12-D will provide you with a most fascinating hobby—one you can share, too. The R-12-D is available for either standard groove or microgroove.

MICROGROOVE CUTS COSTS OF DISCS BY 75 PER CENT

Microgroove recordings, which are recorded and reproduced at 33 1-3 r.p.m., have four times the capacity of ordinary standard groove discs. This makes it possible to record 8 three-minute numbers or one complete short work on each Microgroove recording, resulting in a 75 per cent saving on discs.

Apart from longer playing time and saving in space and cost, Microgroove being cut at lower recording levels gives infinitely better reproduction. This is particularly noticeable in increased high frequencies with less distortion.


The extremely low noise level of BRS discs makes them ideally suited for Microgroove use, the noise being still far below that of standard pressings. MICROGROOVE is the last word in sound recording technique.

SAPPHIRE STYLUS SHARPENING SERVICE

Byer Industries have now installed precision sapphire stylus sharpening equipment. You will save pounds by taking advantage of this quick expert service.

EASY TO INSTALL

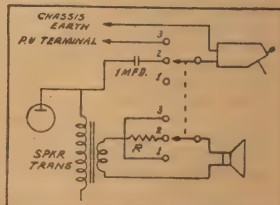The installation of the R-12-D can be easily and cheaply effected. All you need are a few low-cost components and this simple circuit diagram.



Interstate Representatives:—

Wm. J. McLellan & Co. Pty. Ltd.,
55 York St., Sydney, N.S.W.
L. S. Wise & Co.,
14 Pirie St., Adelaide, Cent. 818.

Carlyle & Co. Ltd.,
915 Hay St., Perth, W. 937.
NEW ZEALAND:
Svan Electrical Co. Ltd.,
Wellington, Christchurch,
Auckland, Dunedin.

A. E. Harrold,
123 Charlotte St., Brisbane, B2729.
Giles & Elliott Ltd.,
Wellington.



BYER INDUSTRIES PTY. LTD.

8 Dorcas Street, Sth. Melbourne, Vic.

NEWS AND VIEWS OF THE MONTH

Australia's Radio Stars

THE "radio stars" which have been the subject of so much successful experiment in Australia have again been in the news. Their existence was discussed as one of the features of the recent International Radio Science Congress in Zurich, Switzerland.

Leader of the Australian delegation, Dr. D. F. Martyn, who is chief of the Radio Research Board of the CSIRO in Canberra, said the Australian discovery was one of the most startling disclosures made at the congress.

Australian experts had received these strange signals on television wavelengths, he said.

"We can only presume that they are stars," said Dr. Martyn, "for although we know their exact location from the radio signals, they cannot be seen even with the strongest telescope.

"They are still much of a mystery, and just about all we know is that these radio-sending objects do exist."

Dr. Martyn added that other delegates confirmed this discovery, but it was found that Australian research into these "mystery radio stars" was, by far the most advanced.

There is not the faintest suggestion that these radio signals are being sent by any living beings on the "radio stars."

Air Tides

Another discovery made by Australia was that giant air tides in the upper atmosphere had profound effects on long-distance radio communication. Dr. Martyn said these tides were far more regular than sea tides.

Many of the delegates from more than 20 nations who attended the congress praised Australia's efforts so highly that it was decided to hold the next congress, in 1952, in Sydney and Canberra.

Proof of Australia's advance in these subjects is a recent mission to America by Dr. Martyn, Dr. R. Woolley, Commonwealth Astronomer, and Professor L. G. H. Huxley, of the Physics Department, Adelaide University, to advise the US Air Force on upper stratosphere problems.

These Arguments

"LET'S Buy An Argument," by Neville Williams, has proved one of our most popular features. More and more readers have written in about their ideas, their agreements and their differences. It's a pity we can't print them all.

One or two, however, have been inclined to think his style a little too outspoken, and have been disturbed by his trenchant criticisms.

Let us say here and now that our

editorial policy has always been, and always will be, completely impartial and objective. Neville's idea was to stimulate good-humored discussion with profit to all.

Radio and Hobbies has never printed an ill-natured word. Under no circumstances would it do so. Strong differences of opinion have been expressed from time to time with quite a number of people in the radio world, but never have they been worded or intended to cause offence.

Any reader of our magazine who has any doubt about Neville's intentions can be sure they are completely friendly. Those who interpret them otherwise can only have their own reasons for doing so, or perhaps are inclined to take themselves a little too seriously.

So far, Neville hasn't looked like wilting under the verbal pressure. We can't think our readers have any less endurance!

Light Goes Faster

THE generally accepted figure for the speed of light has been wrong by 11 miles a second, according to the British National Physical Laboratory.

The announcement said that the laboratory's experiments had confirmed the British figure of 186,282 miles a second obtained in 1947.

This figure would displace the previous figure of 186,271 miles a second which the American scientist Albert Abraham Michelson established.

Recent experiments in America and Sweden agreed with the new British figure to within one kilometre (five-eighths of a mile) a second.

"The new British figure will enable more accurate use of radar and will establish new and finer basic calculations in atomic research, astronomy, and radio," the announcement added.

Duty on Radio

THE radio trade was most unpleasantly surprised to find that one of the provisions for the new Federal Budget was the imposition of 25 per cent sales tax on radio sets and components.

It is fairly obvious that if extra taxes are required, they must come from somewhere. At the same time, the Government policy was announced as being in favor of taxing luxuries at the expense of essential commodities.

At any rate, "luxury" is about the only category into which radio sets can fall in the Government's list of items due for extra tax.

The tax is a very stiff one, although the present 8 1/3 per cent reduces the effective increase by this amount.


What seems rather hard to follow is the classification of radio as a luxury. Once upon a time one might have thought so, but today a home without a radio set is dull indeed. Not only because it is denied a wide font of entertainment, but it cannot keep in touch with what is going on. With news and opinion, descriptions of events, police messages, and even Parliamentary debates. It is a necessary contact with the community at large. There is nothing of a luxury about it.

In this issue there is an interesting story of a Government attempt to bring radio sets to the natives of Northern Rhodesia. That story in-

Last Month's Solution



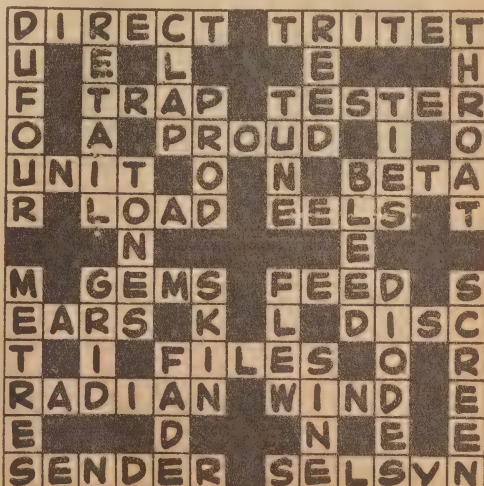We regret to announce that our radio crosswords have been suspended for the time being.




MORGANITE RESISTORS


**TYPES
T and R**

These moderately-priced BRITISH Resistors combine high performance with unusually small size. They are made accurately to their stated resistance values and are consistently stable.

The simple construction of Morganite Resistors provides small, robust, light weight components of high power dissipation and low operating temperatures, and are colour coded to RMA Standard. Stocked in preferred Standard values, viz., 10—12—15—18—etc., values rising in 20 per cent steps (approx.). Morganite Resistors Preferred Value Ranges are standardised in U.S.A. and U.K., and are now available in Australia.

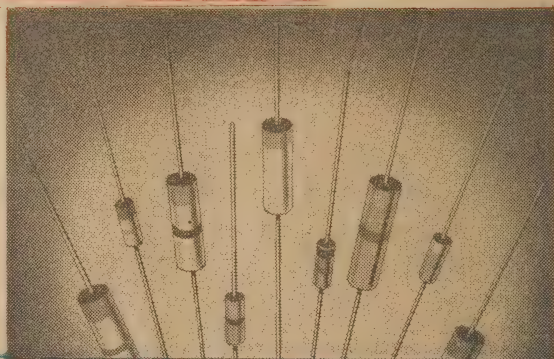

MORGANITE MINIATURE POTENTIOMETERS

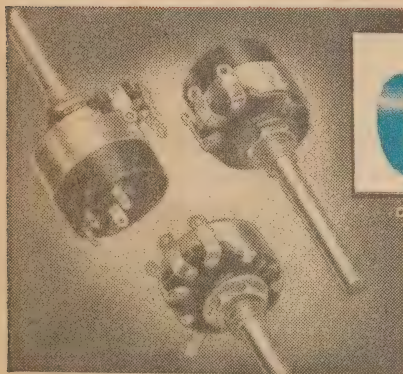

New in design .. British made .. and fully incorporates the traditional Morganite standard of quality.

Radio engineers will appreciate not only the small compact size of the Morganite Potentiometer, but the fact that it is available with a single or double pole switch of proved Morganite reliability.

SPECIFICATIONS

- 1 Overall diameter 1 1/8".
- 2 Double pole or single pole switch operated from shaft.
- 3 Pressure diecast rotor and shaft for accuracy and strength.
- 4 DOUBLE CLENCH TERMINALS eliminate noisy joints.
- 5 Same track design for switch and non-switch type enables interchangeability. Switch type converted to non-switch by interchanging covers.
- 6 The renowned MORGANITE RESISTOR TRACK LOW noise, hard wearing, wide range of standard resistance values and gradings. Rating 1 watt.
- 7 Standard position fixed tapping available.
- 8 Double prong SPRING CONTACTS, in special non-tarnishing metal for resistor sweep, maintains correct pressure for minimum noise without wear.
- 9 The switch withstands the most rigorous operating conditions. Rating: 2 amps, 240 volts.
- 10 Instrument QUALITY at LOW Prices.

THE MORGAN CRUCIBLE CO. (AUSTRALIA) PTY. LTD.

BOURKE ROAD, ALEXANDRIA, N.S.W.

TELEPHONE. MU1371

CABLES & TELEGRAMS "MORGANITE" SYDNEY

cludes the text of some native letters telling of their reactions to the radio sets, and appreciation of the Government which made them available at a low price.

Of course there are quite a few points in which we cannot draw parallels, but if it is radio and isn't considered a luxury for Rhodesian natives it can scarcely be considered so in Australia. Radio sets are dear enough in any case without loading them with a further mark-up.

The extra tax also applies to radio parts, and even to radio cabinets. So that even the home builders will be asked to dig deeper. Fortunately many home builders have a stock of odd parts many of which are quite suitable for use when rebuilding.

The man who will really feel that extra slug is the modest wage earner setting up a home in which we are quite certain he will forgo many things not generally considered luxurious before he can afford to be without a radio set.

Frankly, we could think of many more intelligent methods of making up tax income than slugging the radio industry.

* * *

Fuelling At Speed

ONE of the most intriguing and spectacular things we've seen for some time was a recent newsreel shot of a British jet fighter refuelling in the air.

This isn't a new idea. Well before the war a flying boat used to fill up from an airborne bowser housed in a bomber of almost equal size. But these were comparatively slow craft—slow enough to hook a line one from the other, and haul in a fuel pipe.

Much neater was the fighter's technique of today. The tanker was a larger aircraft of course, and it trailed a hose ending in a cone-like nozzle with the wide end at the rear.

From one wing of the fighter protruded a pipe, looking for all the world like the barrel of a cannon.


Technique was for the fighter to nose up behind the tanker, and manoeuvre this pipe into the end of the funnel. Sealed apparently by the pressure of air on the funnel, fuel then was passed through the pipe at the rate of about 200 gallons in six minutes.

All this went on at 250 mph! It all looked so simple. When the job was done, the fighter just eased back until it disengaged the fuel line, and banked off about its business.

The stunt is more than just that because those fighters use plenty of fuel. They are three times as useful if they can refuel in the air.

The photo-electric cell was once used in a spectacular way at the opening of an American exhibition. The tiny light of the star Arcturus was picked up by the electric eye and the energy utilised to work relays which switched on the whole lighting system in the grounds and pavilions.

Heating-up Time with *SCOPE*

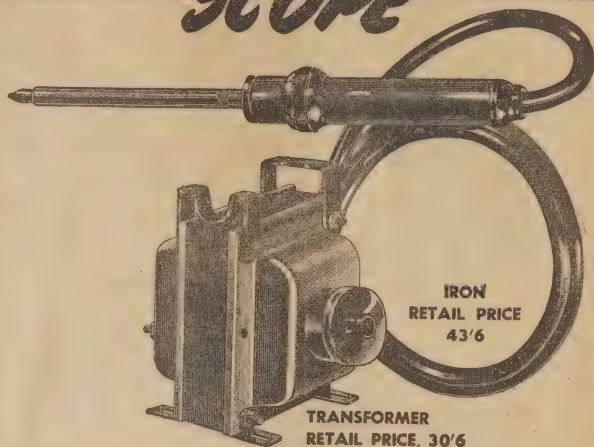

IS 70 TIMES FASTER THAN STANDARD SOLDERING IRONS

The Scope Soldering Iron heats up in the amazing time of 6 seconds—any standard iron takes a minimum of 7 minutes. Scope is, therefore, 70 times faster... and this represents a big saving in power in more ways than one. Firstly, you do not lose the time or power wasted whilst waiting for your iron to heat-up. Secondly, as with ordinary irons, it is not necessary to leave the iron switched on whilst not in immediate use. The Scope Soldering Iron is operated by pushing the switch ring forward with a light thumb pressure and, in 6 seconds, it is ready for use on the biggest jobs. Thus, the Scope Soldering Iron consumes no power when not in actual use. This also prevents

pitting of the bit, and thus avoids frequent cleaning and tinning. Power—approximately 90 watts—dissipated by the Scope Soldering Iron is generated entirely at the bit. Consequently, the transfer of heat is almost 100% efficient. Scope operates from 2.5/6.3 volts A.C. or D.C. and may be coupled to 240 volt A.C. Mains Supply through a suitable transformer. It may also be used from a car battery or 4 volt accumulator. Scope can be used everywhere, anywhere, with the efficiency expected from modern engineered equipment. It is to-day's best soldering iron value. See it, try it—and you, too, will agree.

CHECK THESE FEATURES!

- Operates from 2.5/6.3 volts A.C. or D.C. or from mains with transformer.
- Heats up from cold to ready-for-continuous use in only 6 seconds.
- Has an efficiency equal to that of irons rated up to 150 watts.
- Weighs only 3½ ounces and is 10 inches long.
- Can be used in conjunction with a transformer from A.C. mains or from any suitable car battery.
- Has low operating cost—no current is consumed when not in use; no frequent cleaning and tinning of the bit.
- Extremely suitable for heavy or delicate soldering—heat is applied only where and when it is required.
- Simple to operate—merely press switch ring forward and the iron is hot in six seconds.
- Maintenance is simple—elements and replacement tips are fitted easily and without delay. Replacements are screwed in and cost only a few pence.
- Fully guaranteed for three months from date of purchase. A maintenance service is available at all times.

You should see and test Scope for yourself. If you do this, you will agree it is the soldering iron you should and must have. Ring, write or call for illustrated pamphlet and a demonstration.


Write for illustrated literature

Australian and Overseas Agents:

Wm. J. McLELLAN & CO. PTY. LTD.

Bradbury House, 55 York Street, Sydney. Phone: BX 2508.

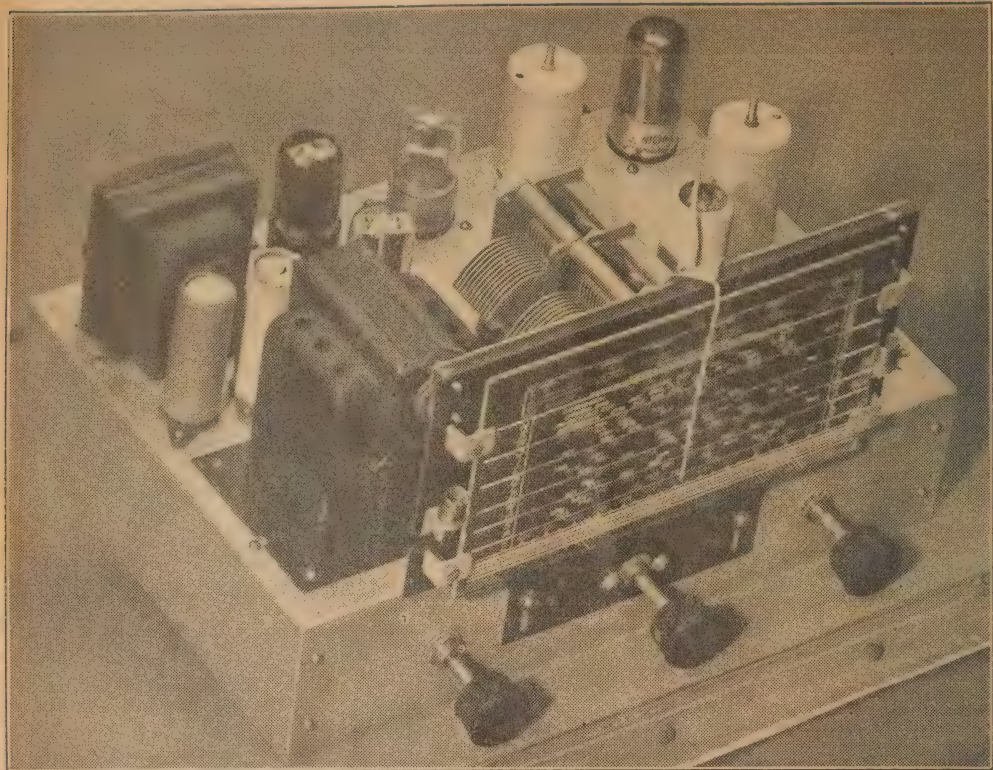MANUFACTURED BY SCOPE LABORATORIES, MELBOURNE, VICTORIA



The controls, left to right, are Volume, Tuning, and Wave Change switch. Otherwise the layout is similar to the broadcast version.

Here is a sensitive and selective dual-wave receiver that you can build and make perform as well as any commercial job, even if you have never built another set in your life. Apart from entertainment on the broadcast band, this set will bring world events and overseas programmes direct from where they happen to your living room via the shortwave bands.

A SIMPLIFIED DUAL WAVE SET

OUR scheme for making set-building easy is now well under way, having brought forward an unprecedented response, not only from readers but from the radio trade in general. Kits for the Simplified Superhet, the Pentagrid Four and the Standard Multimeter are now available at all leading radio supply houses complete to the last solder lug and grid clip.

ANYONE CAN BUILD

With these kits and our complete constructional articles the radio set-building hobby is brought within the reach of everybody.

All you need is an average intelligence and a little practice with the

soldering iron. There is no reason why anyone who has played with a meccano set could not build up any one of the kits described and make it perform as well as did the original in our own laboratory. And you can take our word for it that each of these items performs just as well as the equivalent commercial job.

*by Maurice
Findlay*

The R & H Kit No. 4 is a really good domestic receiver for the average suburban location where a-c power is available. Similarly, the 1950 Pentagrid Four is a standard set for where there are no power mains, while the Standard Multimeter is the first item of test equipment which every experimenter should acquire.

Both receivers are standard broadcast jobs, but many listeners are keen to include shortwave in the household receiver. Programmes from powerful shortwave transmitters all over the world pour into this country every hour of the day and night and a set that can receive them literally brings the world into your living-room.

[illegible]

From the point of view of the constructor a modern dual wave receiver is no more complicated than an ordinary broadcast job.

To switch from broadcast to short-wave it is necessary to change the aerial and oscillator coils, and this is generally accomplished by means of a switch. You can, of course, buy the four coils, trimmers and switch separately and wire them together yourself, but manufacturers have simplified the job by making available a wired and assembled dual wave unit consisting of four coils, a switch and all the required trimmers.

All that is necessary is to connect the appropriate leads into the circuit and the set cannot help but work. Actually, as far as the constructor is concerned, the wiring is simpler than a straight broadcast job.

The complete wired and tested unit costs about the same as would the components separately.

The chassis used for our new set (Kit No. 4) is exactly the same as is used for Kit No. 1. No extra holes are necessary, since the dual wave unit is mounted by a single lock-nut, which also secures the switch shaft. In this case it is convenient to mount the dual wave unit on the right-hand side of the chassis and the volume control on the left.

We suggest that you choose a type of coil unit which is mounted by the control shaft, but if you have any particular preferences there is no reason why another type of coil unit could not be used, provided it will fit. The worst that can happen is that you will have to drill some extra holes in the chassis. Apart from the particular unit you use, it is important to make sure that it is firmly mounted as there is nothing

1 Chassis 13" x 9" x 3".
1 Power transformer 285V per side at
60 mA, 6.3V 2A, 5V 2A.
1 Filter choke 60 mA.
1 Tuning condenser (2 gang, AWA or
Stromberg).
1 Dual-wave dial to suit above.
1 Dual-wave coil unit.
2 I.F. transformers (medium selectivity).
5 Octal valve sockets.
1 4 pin socket.

RESISTORS

1 .005 mfd mica, 2 .00025 mfd mica.
1 100 pf., 1 50 pf.
1 10 meg., 1 2 meg., 2 1 meg., 1 0.5
meg
1 0.5 meg. pot., 1 .25 meg., 3 .05 meg.,
1 .05 meg., 1/2 watt.
1 200 ohm 3 watt wirewound, 1 50
ohm 3 watt wirewound.

SUNDRIES

5 Terminals, 3 knobs, 1 grid clip, 3 1/2"
length resistor panel,
1 5 tag mounting strip, 1 3 tag mount-
ing strip, power flex and plug,
1 4 pin speaker plug, approx. 20 inches
of shielded hook-up wire, length
plastic hook-up wire, nuts and bolts,
solder lugs etc.

more annoying than an unstable receiver.

When mounting or handling the dual wave unit be very careful of the fine connecting wires. The broadcast coil windings are made with multi-strand wire and their efficiency will be spoiled if even one of the fine strands is broken. Therefore, make sure that none of the leads connecting the unit into the set foul the fine wires.

By the way, certain of the coil

Holiday Time

IS PORTABLE TIME

Christmas is just around the corner, the holiday spirit is afoot. Make it a really happy time with a portable radio. Get the added thrill of building your own.

BUILD IT YOURSELF!


It's quite simple, provided you build to a tested and tried circuit and use only the very best components. Electronic Parts kits are compiled to specifications laid down by "Radio & Hobbies" and only the very best quality components are used. **EVERYTHING** necessary to build a first class portable is included with each kit.



CARRY SET

The smartest in small portables. This 4-valver is extremely simple to construct and is most efficient in performance. Note the smart lines of cabinet, size of which is $8\frac{1}{2}$ " high x $4\frac{1}{2}$ " wide x 4" deep. Originally described in "R. & H.", October, 1949.

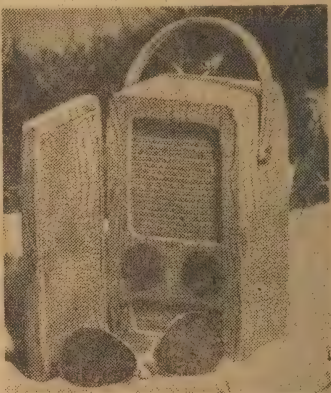Price for Kit complete with Valves, Cabinet and ALL necessary parts, £11/19/0 (Plus Postage).



SENIOR PORTABLE

Originally described in "R. & H." for December, 1948, this 5 valve B/C portable, with R.F. Stage uses either 6" or 7" speaker. A kit of parts for an A.C. power supply is also available. Cabinet size of portable $12\frac{1}{2}$ " x $8\frac{1}{2}$ " x $6\frac{1}{2}$ ".

HANDIE-TALKIE

("R. & H." Oct., 1947, and Dec., 1947). The smallest possible 5 valve portable. Ideal for distance-getting, combined with compactness. A four valve version also available in the same cabinet. Size 7" x $4\frac{1}{2}$ " x 5".



SPRINGTIME PORTABLE

("R. & H." Oct., 1946). A sturdy 5 valve portable with R.F. Stage which will take any amount of hard work. Cabinet size, including hinged lid, 13" x 8 5-8" x $5\frac{1}{2}$ ".

MULTI-TALKIE PORTABLE

("R. & H." July, Aug., 1948). As its name implies, this is a multi unit portable. It is available as a small 4 valve B/C portable and, in addition, an A.C. power unit can be built to enable it to operate from the A.C. mains, or a vibrator unit can be built to enable it to operate from a wet battery. Size of portable cabinet 7" x $4\frac{1}{2}$ " x $5\frac{1}{2}$ ".



Send coupon for free price list of these portable kits, which includes over 50 different varieties of radio kits (battery sets, A.C. sets, car set, grammo-comb, vibrator sets, 32-volt set, etc. etc.)

To ELECTRONIC PARTS PTY. LTD.,
206 Broadway, N.S.W.

Dear Sirs,

Please send me without obligation on my part, price list of your portable kits. (Enclose stamp to cover postage.)

Name

Address


**ELECTRONIC PARTS
PTY. LTD.**

E. S. and A. Bank Build'g,
BROADWAY, SYDNEY, N.S.W.
Phone: MA 1661
Telegrams: ELECPARTS, SYDNEY

**KIT
SET**

SPECIALISTS

UNDER CHASSIS WIRING OF DUAL-WAVE SET

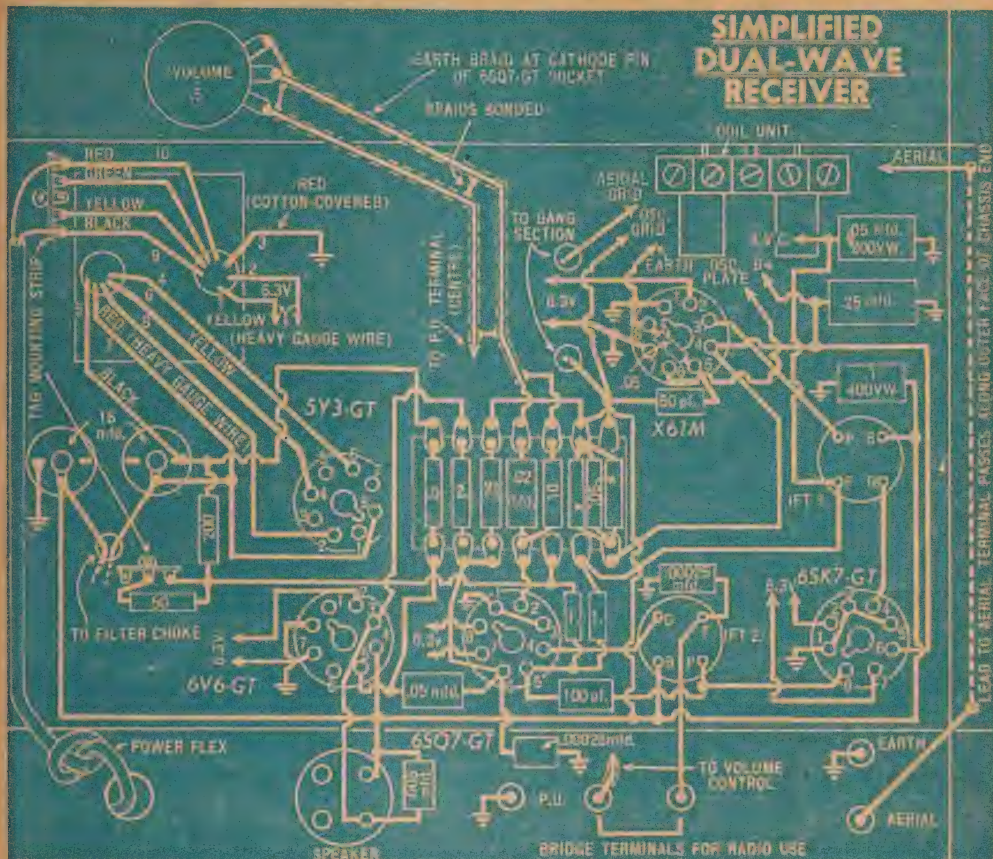

This diagram shows the position of components and methods of wiring. Study it carefully together with the circuit.

units are color coded by means of paint spots on the various connecting leads or switch points, and it is a good idea to make a note of the connections so that, should the coding be removed by the heat of the soldering iron, it will still be possible to identify the connections for the purposes of circuit checking.

Although, up to date, we have been discussing the coil unit, since much of the interest in the set centres around it, in actual practice it is one of the last items to be mounted on the chassis.

ASSEMBLY

When you unwrap your kit from its packing case spread all the components out on the table or your workbench. Make sure that you can identify everything from the parts list and wiring diagram. This should not cause you any undue difficulty, since all condensers have the values marked and you can check resistor values from the standard color code.

The first stage of the assembly is to mount the five octal-valve sockets and the four-pin socket for the speaker. The wiring diagram will guide you as to how to position them.

SOCKETS

Some sockets are provided with a tinplate mounting clip and are bolted to the chassis with two 1-8 in. bolts, while others, known as manufacturers' type, are held to the chassis with a circular spring clip which is crimped to provide the necessary tension. The latter may prove a little troublesome at first, but you will get the knack of it after the first couple of tries.

Your chassis will have a hole on either side of the converter valve which is not used. If cover plates are not provided, you can manufacture a pair from scrap aluminium and bolt them into place. The plates are not necessary from an electrical point of view, of course, but

two empty holes spoil the neat appearance of the finished set.

Sprayed steel chassis cannot be depended upon for good earth connections so that it will be necessary to run a length of tinned copper wire around all the earth points. Therefore, before going any further make sure that there is a solder lug at each earth symbol marked on the diagram.

EARTHING

However, use your judgement in this matter. For instance, there are two earth symbols adjacent to the X61M socket, but one solder lug would be adequate for the purpose. If you are using sockets with tinplate mounting plates, these will make convenient earth points in many cases.

Mount the tuning gang and the two IF transformers and include them in the earth systems by placing a solder lug under one mounting bolt of each. The filter choke is



RECORD PLAYER

★ HIGH FIDELITY
★ DUO-SPEED

GOLDRING PRESENT A RECORD PLAYER which will never become obsolete whatever speed may ultimately be used for DISC RECORDING.

ITS MAIN FEATURES ARE:

- The GOLDRING THREE-WAY PICKUP (No. 150) regarded by many experts as the greatest advance in pickup design.
- A DUO-SPEED MOTOR FOR STANDARD (78 r.p.m.) and LONG PLAYING MICROGROOVE (33 1-3 r.p.m.) records.
- BEST QUALITY LEATHERETTE Covered Case can be closed when playing 12" records.
- Independent on-off switch.
- EASY PLUG-IN TO MAINS.

THE GOLDRING THREE-WAY PICKUP (No. 150)

HIGHEST FIDELITY REPRODUCTION.
Easy change from 78 rpm to 33½ rpm by simply changing color coded stylus and moving weight adjustment.

OUTPUT : 150 mV.
FREQUENCY RANGE : 30—16,000 cps.
STYLUS PRESSURE : 14 grms (78 rpm)
7 grms (33½ rpm)

OPTIMUM LOAD : 50,000 ohms
SAPPHIRE STYLI (supplied with PLAYER)
BLUE : 0.003" for Standard Records
YELLOW : 0.001" for 33½ rpm Records
REPLACEMENT STYLI : 15/- each
Also available GREEN : 0.0025"
ORANGE : 0.0035"

PLEASE NOTE: The unique design of this PICKUP using stylus as ARMATURE does not permit use of other styli or needles.

45 rpm RECORDS when available will be played with same stylus and weight as 33 1/3 rpm record.

THE DUO-SPEED MOTOR

Ideal for playing both standard and long playing records.

Rim driven 4 pole motor of advanced design assures low rumble.

No stray field radiation.


Uniform turntable speed.

Instantaneous speed variation (wow) at absolute minimum.

Self lubricating bearings ensure quiet running and long life. Need no oiling.

Speed change from 78 to 33½ rpm effected in a few seconds by merely reversing main pulley drive.

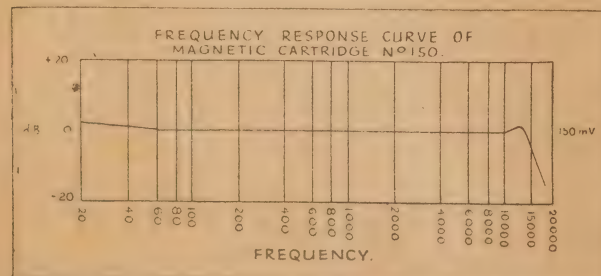10" HEAVY PRESSED STEEL TURNTABLE.
Supplied connected to 200/250 volts but change to 100/125 volts is accomplished easily.




Should records using any other speed become available, adaptors will be supplied at small extra charge.

Availability :
Limited quantities
middle of November..

Price £17/15/- (Incl. 25% Sales Tax)
(Interstate slightly higher)

GOLDRING ENGINEERING (A/SIA) PTY. LTD., 57 H.E. AREA, ST. MARY'S, N.S.W.
Phone: St. Mary's 447. After Business Hours, UW6907.

LAYOUT UNDER CHASSIS

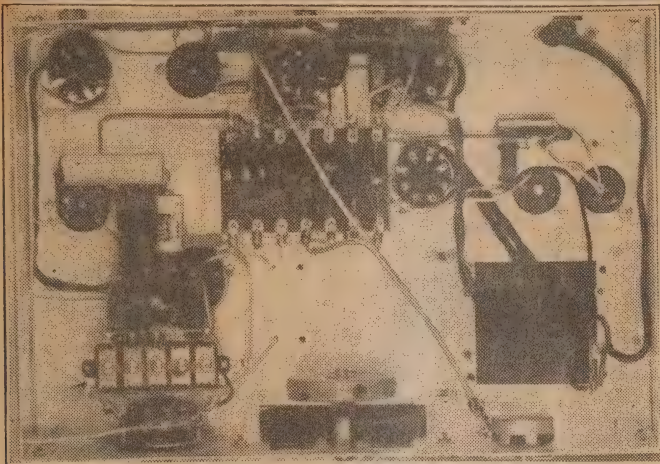

An actual picture of the chassis from beneath.

held in place with four 1/8-in. studs. Tighten the nuts just enough to hold it firmly in place as it is quite easy to strip the threads.

IF TRANSFORMER

The first IF transformer will have a lead protruding through the top of the can which is not required in this set. Snip it off about 1-8 in. above the top of the can. If you are very careful not to break off the retaining lugs you can take the windings out of the can and snip the lead off short.

We have specified the transformer cut-out for a horizontal mounting power transformer, but either type can be used. With the horizontal type tighten the bolts down to the limit to ensure that the laminations will not vibrate.

The vertical mounting transformer which we happened to choose for the prototype set comes complete with a special adaptor plate and it is not necessary to drill any extra holes. The adaptor plate can be seen clearly in the above chassis photograph.

With the vertical mounting power transformer, the leads should be long enough to reach to the rectifier and the filament pins of the 6V6-GT. Twist each pair together for neatness.

It will be necessary to install a tag strip for the primary leads. Connect the unused tappings so that, should you need to change the supply voltage for the set, it will only be necessary to resolder a wire. Don't forget the rubber grommet for the power cord hole and tie a knot in the cord on the inside of the chassis so that accidental strain will not be concentrated on the tag strip.

WIRING

After mounting the 3 1/2 in. length of terminal strip in the centre of the chassis, the five terminals and the volume control, you can proceed

with the major part of the wiring. You will note that the coil unit and the dial are left until later because of the possibility of them being damaged.

As far as the wiring is concerned, concentrate on neatness with the supply leads—filament, high tension, screen and AVC—as an extra inch or two of lead is not of any particular significance.

Short, direct wiring should be the order of the day for all leads carrying signal currents, particularly those in the plate circuit of the mixer and IF amplifier, the grid circuit of the IF amplifier and the detector and AVC diode circuits.

SHIELDING

Two audio leads in the receiver will require shielding. They are the lead from the terminal at the rear of the chassis to the "hot" side of the volume control and the lead from the centre of the volume control back to the .02 mfd. coupling condenser. Note that the shield braid should not be soldered to the cover of the potentiometer, but should be returned to a single earthed point near the cathode of the 6SQ7-GT.

Small components such as resistors and condensers are held in place by means of their own pigtail leads but take care, particularly in the case of the .25 mfd. condenser, that the leads are not so long that the components can flop around.

Incidentally this condenser and the .05 mfd. AVC bypass should not be installed until after the coil unit is in place, since the terminal lugs of the unit make convenient tie points.

Return the earth lead of the dual wave unit to earth with a length of tinned copper wire. You will probably find that it is convenient to make this connection near the X61M socket.

The wire from the aerial grid lug goes direct to the front section of

After stocktaking
"SPECIALS"
 from your favourite
**RADIO-MAIL-ORDER-
 HOUSE**
*(Available for One Month
 only) or until all supplies
 sold.*

VALVES Types,

38, DLS10, GL446A, CV6,	
705A, 7192, EA50, 9004,	
9006, 6H6, 1203A	2/6
954, 955, 1LD5, 6C8	5/-
6AG5, 7C7, 7C5, 12SR7	7/6
9001, 9002, 9003, 6AJ5, 2D21	11/6
6AC7, 12SL7, 1L4	17/6
815, 837, 866A, 913	25/6
35TH (Eimac)	29/6

Midget Kingsley 7000 spkr.	
transf.	5/-
Midget 2/Gang tuning	
condens.	7/6
Midget 150/150/30ma	
P/Transfm.	12/6
Midget 4-valve AC-Batt.	
chassis	5/-

Chrome - plated Instrument	
Probes	12/6
23v - 250v - 60ma Gene-	
motors	21/6

Handpolished Walnut	
Speaker Cases	29/6
Cream Spk. Cases, with	
chrome front	27/6
(Both the above for 3"	
Speakers)	

5 Station Type 240v AC-	
DC Master Inter-	
comm. Unit	£21/15/6
Remote Units for above	
each	£5/18/-

"TELE-TAPE" Magnetic Tape	
Recorders, complete ready for	
operation, 240vAC, Professional	
Model	£149/10/-

For all your RADIO requirements, consult **FN RADIO-TELEVISION CO.** — Australia's Leading Radio-Mail-Order-Firm. ... If it's available in Australia, we can supply it.

FN RADIO-TELEVISION CO.


265 MILITARY ROAD,
 CREMORNE, N.S.W.

XY5063 XY5063
**"SAME DAY MAIL ORDER
 SERVICE"**

OBTAIN EXTRA SENSITIVITY

FREE! IN THE R & H KITSETS

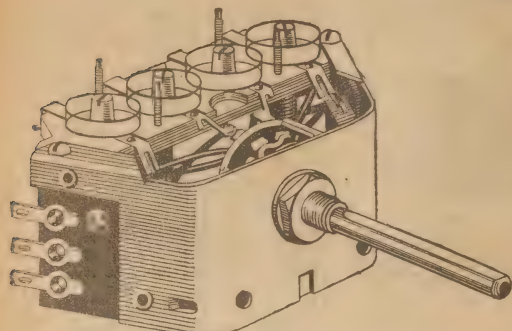BY SPECIFYING "Q PLUS" TYPE ON BRACKET
FROM YOUR FAVOURITE DEALER



THE SINGLE STAGE UNIT

The single stage unit illustrated at left is approximately life size. Available for 16-50m. Only on S.W. band.

FEATURES

- Spherotuned coils on all four bands
- Fits snugly between dial spindle and volume control ETC. ETC.

49'6

RETAIL

Both Units are available in the following types

For 6J8/6K8 .. DW4 or DWR4.

For ECH35/33 .. X61M

DW5 or DWR5

For IR5 DW6 or DWR6

For 6BE6 .. DW7 or DWR7

The DWR Series Being the R.F. Unit

ONLY

95'-

SPECIFICATIONS

B/CAST BAND COVERAGE

550—1630—KCS—"H"

Gang or Dial

SHORT WAVE COVERAGE

13-Y2M or 16-50M


Please specify when ordering

Spherotuned coils on all bands.

Spare contacts for gramo. position

Measures
5½" x 2½"
x 2"

THE R.F. UNIT

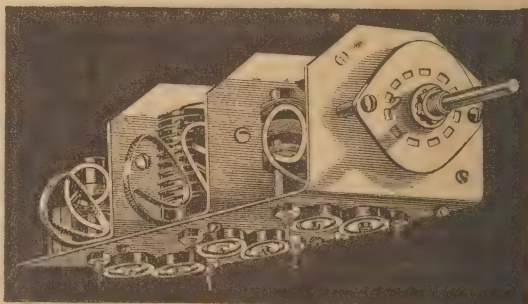

This newly released bracket gave better than 1UV sensitivity on B/C band and slightly less on S/WAVE band.

WHEN USED WITH Q PLUS IF'S

so specify only Q PLUS, please.

MANUFACTURED AND GUARANTEED BY

R. W. STEANE & CO. PTY. LTD., AUBURN, VICTORIA



the gang. Connect the aerial lug to the aerial terminal via the outside of the chassis, and the oscillator plate to pin 6 on the X61M socket by the shortest possible route, at the same time keeping it firmly in place and clear of the coils and fine wires in the unit.

Similarly, keep the oscillator grid clear of the unit and connect to the lug on the corner of the resistor strip near the X61M. The 50 pf. condenser will already be in place. You can now install the lead from the lug to the rear section of the gang, and the only remaining lead is that from the front section of the gang to the X61M top cap (not shown on diagram). Keep this as short as

correct, the first components to check are the two electrolytic condensers and the 1 mfd bypass from high tension to earth. Without a multimeter, the best you can do is to try disconnecting these components one by one until the short disappears.

If everything is in order, you should be able to receive some signals on the broadcast band, at least, although they may be weak and tune rather broadly, since the alignment will not be correct.

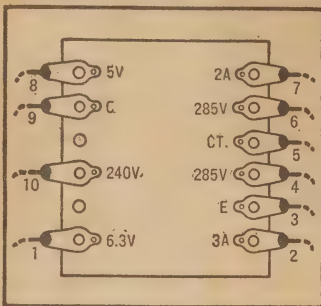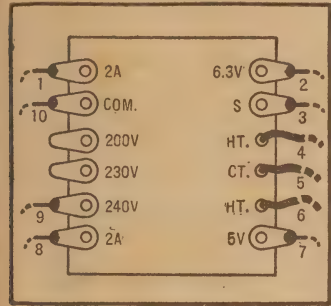If, with an aerial connected, it is not possible to tune in a signal of any sort, you can take it for granted that there is an error somewhere, unless, of course, you are in a poor location and have reason to believe that the



You may wish to use an alternative type of power transformer with a terminal board attached. The layout of two popular types is illustrated above, with their normal markings and the leads numbered to correspond with the wiring diagram on page 31.

possible, at the same time allowing enough slack to make it easy to put the grid cap on.

Bolt the dial in place, but before doing so remove the screw which holds the drum to the frame of the dial. Take great care not to tangle the cord as it is a somewhat ticklish task to sort out a jumbled mass of fine dial cord. See that the drum is in alignment with the two pulleys near the top of the dial, otherwise the cord is likely to come off when the drum is turned.

After thoroughly checking the wiring, plug in all valves except the 5Y3-GT rectifier and switch on the power.

By this time your hands will probably be beginning to shake, but always remember that other people have been through the same experience—and survived!

If the four valves light up normally, and there is no indication of stress from the power transformer you can switch off again and plug in the rectifier and the speaker.

FIRST TESTS

Failure to attend to the latter will damage the output valve so make sure that the speaker plug is 'always' in place before the set is plugged into the power mains.

When you switch on again look between the rectifier plates and filament. If there is a continuous blue glow or flashing inside the rectifier switch off without delay and look for a short between high tension and earth.

If you are sure that the wiring is

trimmers and slugs have been mal-adjusted since leaving the factory.

We will discuss the method of alignment later, but a few remarks will be welcomed by those who have already built Kit No. 1, and would now like to include the dual-wave unit.

MODIFYING KIT No. 1

First, remove the volume and tone controls, replacing the latter in circuit with a 0.5 meg. resistor. Also remove the aerial and oscillator coils and the two trimmers soldered to the gang condenser. Mount the volume control on the opposite side of the chassis and reconnect the shielded leads. They will probably be a little short, and the easiest way may be to install completely new leads.


Transfer the high-tension end of the three .05 meg. resistors to the adjacent vacant lug on the resistor strip, clearing the end lug for the oscillator wiring. Bolt the two metal plates to cover the holes previously occupied by the aerial and oscillator coils and then you can go ahead with the wiring for the coil unit as per the suggestions given earlier in this article, except that you may have to slightly alter the positions of the .25 mfd. and .05 mfd. bypass and the 50 pf. oscillator grid condenser.

The exact alignment procedure you adopt will depend on the type of dual-wave unit you have. However, it is most likely to have air-cored coils and five trimming condensers. We will discuss this type of unit first, and then outline the procedure with iron-

(Continued on Page 99)

N.H.V. KITS

AMPLIFIER CABINETS

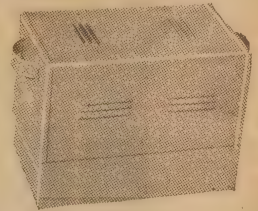


These streamline amplifier foundation units consist of a standard chassis 3" deep with removable top in aluminium. Fitting over the top is a removable cover which has louvres on all sides and handles welded to the ends. Color Grey.

Catalogue No.	W	D	H	Prices plus Sales Tax
AC1	10"	5"	9"	£1 5 6
AC2	12	7	9	£1 12 6
AC3	17	7	9	£1 19 6
AC4	17	10	9	£2 15 0

WITH SLOPING FRONT
CHASSIS 3 1/2" High. Handles Welded to Chassis.

Catalogue No.	W	D	H	Prices plus Sales Tax
AC SF 1059	10	5	7 1/2	£1 12 6
AC SF 1279	12	7	9 1/2	£1 15 6
AC SF 1779	17	7	9 1/2	£2 6 6
AC SF 17109	17	10	9 1/2	£2 19 6

Metal Utility Cabinets

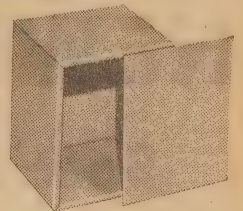

This line of Cabinet is for housing electronic equipment of all types. It has a fixed back and removable front. Color, Grey.


Catalogue No.	D	W	H	Prices plus Sales Tax
MC666	6	6	6	7/6
MC596	5	6	9	8/6
MC7810	7	8	10	12/6
MC6712	6	7	12	12/6
MC81010	8	10	10	15/6
MC81112	8	11	12	19/-
MC7915	7	9	15	19/-

WITH SLOPING FRONT

Catalogue No.	D	W	H	Prices plus Sales Tax
MCSF776	7 1/2	7	6 1/2	10/6
MCSF796	7 1/2	9	6 1/2	12/6
MCSF7116	7 1/2	11	6 1/2	14/6
MCSF8138	8 1/2	13	8	17/6
MCSF101810	10 1/2	18	10	28/6

N.H.V. KITS

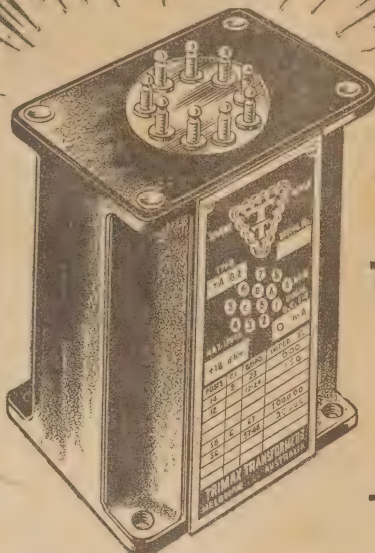97 MARRIOTT ST., REDFERN, N.S.W. MX3764
An Associate of R.H. Oxford & Son Pty. Ltd.



TRIMAX TRANSFORMERS

Every transformer looks to be simply coils of wire on a core . . . but the beauty of Trimax Transformers is more than skin deep! Long experience and high standards of technical ability ensure that the unseen parts of your Trimax Transformer will prove their reliability in every test.

TRIMAX TRANSFORMERS

Cliff and Bunting Pty. Ltd.

CHARLES STREET, NORTH COBURG, MELB., VIC.

QUEENSLAND:
Chandlers Pty. Ltd.

N.S.W.:
Radio Equip. Pty. Ltd.
John Martin Pty. Ltd.

TAS.:
W. & G.
Genders P/L.

SOUTH AUST.
A. G. Healing Ltd.
Gerrard & Goodman Pty. Ltd.
Radio Elect. Wholesalers Ltd.

WEST. AUST.
Nicholson's Ltd.
Atkins (WA) Ltd.
Carlyle & Co. Ltd.

NEWS!



NEWS!

Special MAIL ORDER Dept.

We announce the formation of a special Mail Order Department, and now at last you can obtain your Coil and I.F. Transformer requirements direct from specialists, who are equipped to give you prompt deliveries, and assist you with your technical problems. Ample stocks are available of "VEGA" Super Quality I.F. Transformers and Coils (as used by

leading Receiver Manufacturers), and we commend you to use this service, by selecting your requirements from our Catalogue list of Components.

Help us to help you by placing your order NOW, and include Postal Notes, Money Order or Cheque (plus exchange and postage) to cover cost. Sorry—postage stamps or C.O.D. orders are not acceptable.

MANUFACTURERS, DEALERS, SERVICEMEN—Usual Trade Discounts available to those justly entitled to same.

STANDARD

I.F.T.'s: VIF 5 & 6—455kc—Price 13/9 each.
B/C COILS: VC1 (aer); VC2 (R.F.); VC3 (Osc.)—Price 8/9 each.
S/W COILS: VCH1, 2 & 3 (13—42 Metres)—Price 3/11 each. VCH4, 5 & 6 (16—50 Metres)—Price 3/11 each.

MINI

Giant in performance—dwarf in size—"VEGA" miniature I.F.'s give you the greatest GAIN in radio . . . VIF14 & 15 . . . 13/9 each.

Miniature Coils are also available. Aerial, R.F. Osc. (specify mixer tube) . . . VC19, VC20 and VC21 . . . 8/9 each

KIT

MINI CAR RADIO KIT (matched) . . . Price 57/6 (Aer., R.F., Osc., 2 X I.F.T.'s & "Hash" Coil.)

CRANCH Products & Trading Co.

Telephones: BU 3879
BW 7746

17 BOND STREET, SYDNEY, N.S.W.

Telegrams: "Cranlay"
Sydney

FROM THE SERVICEMAN WHO TELLS

Again this month, the Serviceman's columns are thrown open to his accountant friend, whose object in life, at this moment is to help you keep books straight. Let us know if you find these articles helpful.

LAST month I introduced you to the use of the most "important" of all books of account—the Cash Book. This month we will discuss the use of the most "revealing" book of account—the Ledger.

I have assumed thus far that all your transactions were cash transactions. That is, that you paid immediately by cheque for all goods &c, you received, and that all your customers gave you spot cash for any articles you sold them or work you did for them.

If you could persuade all your business associates to continue dealing with you in this way your trading transactions and the recording of same would be very simple. You would have no worry over outstanding accounts.

However, whilst such a state of affairs is very desirable, modern business methods demand that you enter into transactions other than for cash ie, "Credit transactions."

CREDIT ACCOUNTS

This means that, as your business gets under way, you will be entering into contracts with people for the purchase and sale of goods and services, the payment for which will be made at a later date.

Before you give "credit" to anyone, make sure of their ability to pay. You can do this by asking for references from other firms from whom they have bought on credit. This reference is usually obtained verbally by ringing the firms concerned. If a large amount is involved it may be wise to obtain a written reference and even necessary to check with the bank with which they deal.

We will discuss this question of credit more fully in a later article. Let us for the present confine our attention to the use and keeping of the ledger.

The main advantage of the ledger lies in the fact that it provides a running record (or history) of each item of account.

THE LEDGER

You will recall that last month, we took out a statement of Affairs which showed us the month's income and the expenses incurred in earning that income. You could manage quite well by taking out a similar statement each month throughout the year, but would find it rather cumbersome to have to go through twelve statements to find out the amount of say your purchases for the year.

How much easier it would be to go to one page and there see set out in chronological order your purchases for the twelve months. And that is just what the ledger does

give you — a complete historical record of each item.

This is so because each purchase is recorded in the Purchases account, each amount spent on advertising is collected in the Advertising Account, a record of all amounts spent on lighting find their way into the Power and Light Account and so on.

Here we have the application of our Double Entry Bookkeeping system which is simple, self-checking and ideally suited for you, the radio serviceman.

To refresh your memory, I reiterate that the significance of the word "Double Entry" is that, every time you make a transaction, you record two entries in the books. Up to date in our bookkeeping we have made only one entry. We shall now proceed to make the second or "double" entry.

DOUBLE ENTRY

This is done by "Posting" from the Cash Book into the Ledger. "Posting" merely means transferring from one book to another. It is governed by the first rule you learnt viz. "Debit whatever is received."

Concerning the book itself it is worthwhile spending five or six shillings on a well-bound book preferably with an alphabetical index in the front. If you cannot get one with an index leave the first one or two pages and make up your own index. An index may seem superfluous when you are first starting out, but as your business grows it will save you a lot of time turning over pages looking for the right account.

Allow a separate page for each account. In the case of Purchases and Sales, it may be a good idea to leave two pages. Next write up your index. Having done this you are now ready to commence Posting. Figure 1 shows you a typical layout of a ledger. The ruling is like a small cash book. The debit and credit sides are on the one

sequently was debited. Who gave the money? You did and so you have to be credited.

An account is opened in the ledger "Capital Account" or if you prefer "R. Jones Capital Account." In this case R. Jones would be yourself.

On the credit side of that Capital Account we make an entry dated October 1. By cash indicating that it came from the Cash Book, and the amount of £200 which is the same as shown in the Cash Book.

The next posting is a sales item. Here you can see the advantage of having a separate column for sales in the Cash Book. There are a number of transactions during the month which affect the sales account, and which would have to be posted individually. Instead only one posting of the total sales for the month is required.

To post this item you post the total of the sales column, £82.

The bank received the money for the sales and it is debited, therefore the Sales Account must be credited. The date, October 30 is entered because this posting represents all the sales for the month. The detail is "By Cash" and the amount £82. You will see the entry in the Sales Account of the specimen ledger (Figure 1.).

Next we come to service. Here again only one posting is necessary. The amount of £18 is entered on the Credit side of Service Account. The particulars are By Cash and the date is again October 30.

EXPENDITURE

This completes the posting of the debit side of the Cash Book, and if you check over your entries you will see that you have entered a total of £300 on the credit side of your ledger. So far your Double Entry is correct.

We now turn to the Expenditure or Credit side of the Cash Book. We see that the first item is Purchases, and that it has a separate column. Therefore, we can post the total purchases for the month in one entry.

As far as Purchases are concerned Cash was credited because Cash was given up for the Purchases. What account received the value? It was the goods that were purchases for resale and thus Purchases account is debited.

The entry appears on the left hand or debit side of Purchases account as follows:—Oct. 30. By Cash £100.

Salary is the next item to be posted and this is transferred to Salaries or Drawings Account in exactly the same way. Strictly speaking, the salary you draw for yourself represents money taken from the business and should be debited to Drawings account, but for simplicity I have retained the word Salaries. If, as

by
C. H. Pearce
AICA

page, and usually there is only one money ruling for each. You will find this quite sufficient. In Figure 1 all the accounts appear on one page for convenience, but they will of course be on separate pages in your ledger.

We shall commence posting from the "Receipts" side of the Cash Book. The first item is Capital. The bank received this amount of £200 and con-

IRC

The INDUSTRIES STANDARD

MADE IN AUSTRALIA
**BACKED BY WORLD-WIDE TECHNICAL
ORGANISATIONS**



INSULATED *Metallized*

TYPE BT RESISTORS

THE WORLD'S STANDARD RESISTORS

Their ingenious construction, with the time-tried *Metallized* filament, insures lower operating temperatures with proportionately high wattage dissipation in a small, sturdy lightweight fully insulated unit with an **EXCEPTIONALLY LOW NOISE LEVEL**.

Guaranteed accuracy of plus-minus 10%. Proof against moisture—even salt water immersion. 1000 volts insulation to ground.

Available in all standard values, Types BT₁, BT₁ and BT₂, they suit the exacting requirements of the local market.



Metallized

VOLUME CONTROLS

PERMANENTLY QUIET


TYPE CS with the time-tested *Metallized* element.

The old bugbear of noise is **PERMANENTLY** eliminated by these IRC **EXCLUSIVE** features:—

● **SILENT SPIRAL CONNECTOR**, which provides continuous electrical connection between centre terminal and volume adjustment arm, eliminating metal to metal contact—the common cause of noise.

● **5-FINGER KNEE ACTION CONTACTS** that ride over the resistance element independently of each other.

Thus, in IRC Controls you have **DOUBLE** assurance of smooth action that is quiet—and **STAYS** quiet. There's **NO SLIDE, NO FRICTION, NO NOISE**. Size—they are only 1½" diameter. Brass spindles. No die casting is used in manufacture, therefore there is no distortion or creeping with the passing of time. Insulated shaft, ½-watt rating. D.P.S.T. or S.P.S.T. switches for mains of low voltage operation.

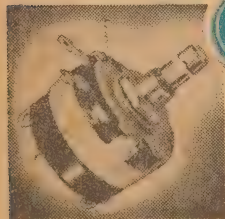

SOLE AGENTS FOR AUSTRALIA:

Wm. J. McLELLAN & CO. PTY. LTD.

Bradbury House, 55 York Street, Sydney Phone: BX 2508

your business grows, you should employ other people, then their wages would be debited to a Wages or Salaries Account. The salary you take out of the business would be debited to Drawings Account.

Now we come to the Sundries column. Here we have a number of items which have to be posted separately. The first is Furniture and Fittings, £30. Cash was given up for these fittings and so cash was credited. We again ask ourselves what account received the value. The answer is Fittings, therefore the Furniture and Fittings account is debited. Turn to Figure 1 and trace the entry through.

Also on October 2 Cash (£30) was expended on test instruments. In this case the account which is debited is called Plant Account.

Next to be posted is Rent, £5, then Advertising £3, Telephone £5 and Lighting £2. When all these accounts have been debited our postings from the Credit side of the Cash Book are complete. Check them over, they should total £195.

FOLIOS

For the sake of accuracy it is always wise to have a key to your posting. Alongside the money column in your books of account you will notice a narrow column about $\frac{1}{2}$ " wide. This is known as the "Folio" column. "Folio" is merely the bookkeeper's way of saying page number. In this folio column you write the number of the page in the book from which you have posted. When you are posting from a book you will write in the folio column the page number of the book to which you are posting.

In the case of the Capital item you will find no fundamental meaning Ledger Page 197 cannot be a column, which means that you have posted that amount to Page 1 in the Ledger.

At the foot of the Sales and Service column you will write the appropriate ledger numbers, indicating that you have made postings to these pages. The same will apply to the credit side of the Cash Book, and the same system will apply to the Ledger.

In the Ledger you will show the page number of the Cash Book from which you have made the postings. For example, in Capital Account in

LEDGER PAGES

Page 1

CAPITAL ACCOUNT

	£ s. d.
Oct. 1.	
By Cash . .	200 0 0

Page 2

SALES ACCOUNT

	£ s. d.
Oct. 30.	
By Cash . . .	82 0 0

Page 3

SERVICE ACCOUNT

	£ s. d.
Oct. 30.	
By Cash . . .	18 0 0

Page 4

PURCHASES ACCOUNT

	£ s. d.
Oct. 30.	
To Cash . .	100 0 0

Page 5

FURNITURE AND FITTINGS ACCOUNT

	£ s. d.
Oct. 2.	
To Cash . . .	30 0 0

Page 7

PLANT ACCOUNT

	£ s. d.
Oct. 2.	
To Cash . . .	30 0 0

Page 8

RENT ACCOUNT

	£ s. d.
Oct. 2.	
To Cash . . .	5 0 0

Page 9

ADVERTISING ACCOUNT

	£ s. d.
Oct. 10.	
To Cash . . .	3 0 0

Page 10

TELEPHONE ACCOUNT

	£ s. d.
Oct. 14.	
To Cash . . .	5 0 0

Page 11

POWER AND LIGHT ACCOUNT

	£ s. d.
Oct. 25.	
To Cash . . .	2 0 0

they appear to job down to 3 valves easily

CASH OR DRAWINGS ACCOUNT

	£ s. d.
Oct. 30.	
To Cash . . .	20 0 0

FIG. 1.

the folio column on the credit side you will write C1, meaning Cash Book, Page 1. This indicates that that is the page from which you have taken the posting.

A wise rule to follow when posting is to insert the folio number immediately after each item is posted. In this way, should you have to answer the telephone or be subject to some interruption, you can, upon returning to your books, see at a glance up to what point you have posted.

TRIAL BALANCE

You will recall I stated last month that your records can be self-checking and that should an error occur it can be located without delay. This is achieved by the preparation of a Trial Balance, which is merely a list of the balances on the accounts in your ledger.

If you look at Figure 2 you will see that to make up a Trial Balance it is necessary only to write down the name of account and put down its balance according to whether it be "Dr" or "Cr." Add up both sides

and if they total the same you have proved the arithmetical accuracy of your books. Figure 2 includes the balance of every account in our ledger, plus the balance brought forward in the Cash Book, viz. £105. Our debits and our credits total £300, therefore we know that our Double Entry bookkeeping is correct.

By reading through this article carefully you should understand thoroughly how to post from one book to another. You will have also realised the great advantage of having a ledger—the book which tells you the "story" of your Sales, Purchases, Expenses, in fact, every account for which you have entered into a transaction.

(Continued on Page 51)

TRIAL BALANCE

ACCOUNT	Dr. £ s. d.	Cr. £ s. d.
Capital		200 0 0
Sales		82 0 0
Service		18 0 0
Purchases	100 0 0	
Salaries		
(or Drawings)	20 0 0	
Furniture and Fittings	30 0 0	
Plant	30 0 0	
Rent	5 0 0	
Advertising	3 0 0	
Telephone	5 0 0	
Power and Light	2 0 0	
Bank	105 0 0	
	300 0 0	300 0 0

FIG. 2.

A photograph of a large, rectangular, metallic object, possibly a piece of machinery or a component, with various bolts, nuts, and a small circular opening visible. A small blue star sticker is placed on the right side of the image.

... **THE WORLD'S STANDARDS** ...
... with the time-tried Metal ...
... temperatures with pro ...

And then, of course, around the summer period there are those tantalizing days when interstate and New Zealand stations suddenly appear out of the blue at "local station" strength and all bedlam breaks loose. Yes, there is plenty on the 50 mc band, and no amateur who has spent a period working there will ever forget the fun he extracted from it.

USING THE 807

The transmitter to be described actually grew from the push-pull 807 design described in the 1950 Short Wave Handbook. It uses virtually the same circuit and parts, with only small modifications to layout and circuit values. It will run perfectly well with 100 watts of input and can be modulated for phone.

It has good efficiency, and the output is quite comparable with that obtained on other bands.

Some amateurs we know have had difficulties with the use of 807's on

by
John Moyle

CIRCUIT DIAGRAM OF THE 50MC TRANSMITTER



The circuit is neither complex nor elaborate. Careful adjustment only is needed for good results. The cathode coil has 7 turns on a 1 inch former. Oscillator plate coil has 6 turns of 16 gauge 1/4 inch diameter spaced 1/4 in. Doubler plate coil has 5 turns 1/2 inch spaced 1/4 in. Final tank coil has 6 turns of 14 gauge wire spaced 1/4 inches.

the higher frequencies and, in fact, on almost any band if it comes to that. There is, however, no fundamental reason why the 807 cannot be used on 50 mc. It has full ratings at that frequency, and although its internal wiring makes it less stable than on 14 mc, for instance, there is no reason why it should prove anything but satisfactory if one goes the right way about it.

However, let us consider the transmitter in general, and the 807's can be discussed later.

INITIAL 6V6's

In the interests of simplicity and economy it is desired to use as few valves as possible. For this reason the transmitter commences with a crystal on approximately 8.3 mc and in two stages multiplies this up to 50 mc. To be accurate, 8.333 mc produces 50 mc and 9 mc produces 54 mc. Because most of the available crystals (generally from Disposals sources) lie between 8.3 and 8.6 mc most stations are found at this end of the band. The order of multiplication is, of course, six times,


This is accomplished by using some form of oscillator-multiplier tripling in the first stage, followed by a doubler to drive the amplifier. Experiments made over some considerable time lead us to believe that the Tritet circuit is about the best of all as an oscillator-multiplier and will produce more than enough output to drive a doubler to 50 mc.

The valves used in these stages are 6V6s because, despite their maximum

full frequency rating of only 11 mc, they appear to do a better multiplying job down to 50 mc than any other valves easily obtainable. Moreover,

they are virtually impossible to "blow up" under reasonable overloads.

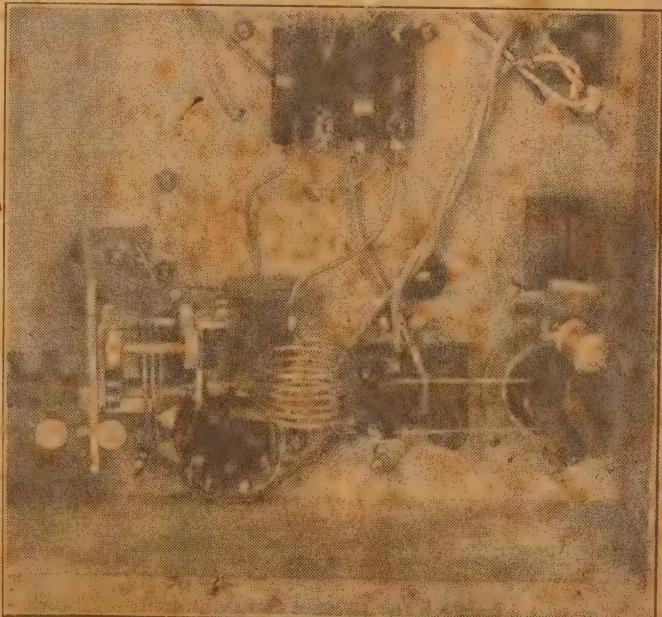The reason for tripling in the oscillator is that it is not hard to obtain



Under the chassis at the oscillator end. Coil is on 25 mc. in the triode plate circuit. The crystal socket is at right, oscillator at centre, and doubler at left.

UCC

ELECTROLYTIC CAPACITORS

INFORMATION BULLETIN



Type 51-130. Pigtail Type—universally used in any position where capacitors can be supported on tinned copper pig-tails. Capacitor body is insulated.



Type 51-134. Flanged Clamp—used where above chassis mounting is required and capacitor is earthed. Capacitor body is not insulated.



Type 51-126. Insulated Flange—used for above chassis mounting and where capacitor is insulated for bias supplies. Capacitor body insulated.



Type 51-101. Twist Lug—used for above chassis mounting by inserting lugs through slots and twisting to hold in position.

SPECIFICATIONS

1. Capacity Tolerance: — 10% + 40%.
2. Power Factor: 15% max.
3. Max. Operating Leakage: 0.1 mA/mfd.
4. Max. Operating Temp: 145° F.
5. Electrolyte: Semi-dry.
6. Container: Hermetically Sealed Aluminium.

UNITED CAPACITOR CO. PTY. LIMITED

433 PUNCHBOWL ROAD, ENFIELD, NEW SOUTH WALES.
POSTAL: Box 19 Enfield.

PHONE: LF3511

Associated with Tecnico Limited of Australia and Telegraph Condenser Co. Ltd. British Insulated Cables Ltd. and United Insulator Co. Ltd. of England.

65/HP2

NOW! FACTORY KITS at FACTORY PRICES!


CROWN MAKES SPECIAL OFFER TO GENUINE AMATEURS



Crown Iron cored short wave Aerial, R.F. and oscillator, 13-42 metres.



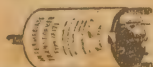Crown P12 Standard 5-plate, 455 k.c. paddar condenser.



Crown 455 k.c. I.F. transformers.

Fully aware of the important contribution that amateur experimentation has made to the development of radio in Australia, Crown Radio Products Pty. Ltd. have decided to assist genuine amateur builders throughout the Commonwealth by offering the latest in quality radio components direct from the factory. This will mean a big saving in component costs to genuine experimenters. The directors of Crown Radio Products Pty. Ltd. feel that some concrete acknowledgement should be made of the value that amateurs have added to the standing of Australian radio. Crown components are already well known for their quality. They cover coils, transformers, paddars, short wave kits, in fact, practically every component required by the ham. Genuine amateurs should avail themselves immediately of this great Crown offer and write direct to Crown today for full particulars.


Write today for full particulars of Crown's offer to genuine amateurs.

Crown
RADIO PRODUCTS PTY. LTD.

51-53 MURRAY STREET
PYRMONT — SYDNEY

Telephone MW2628
(2 Lines)

A REAR VIEW OF THE TRANSMITTER FOR 50MC

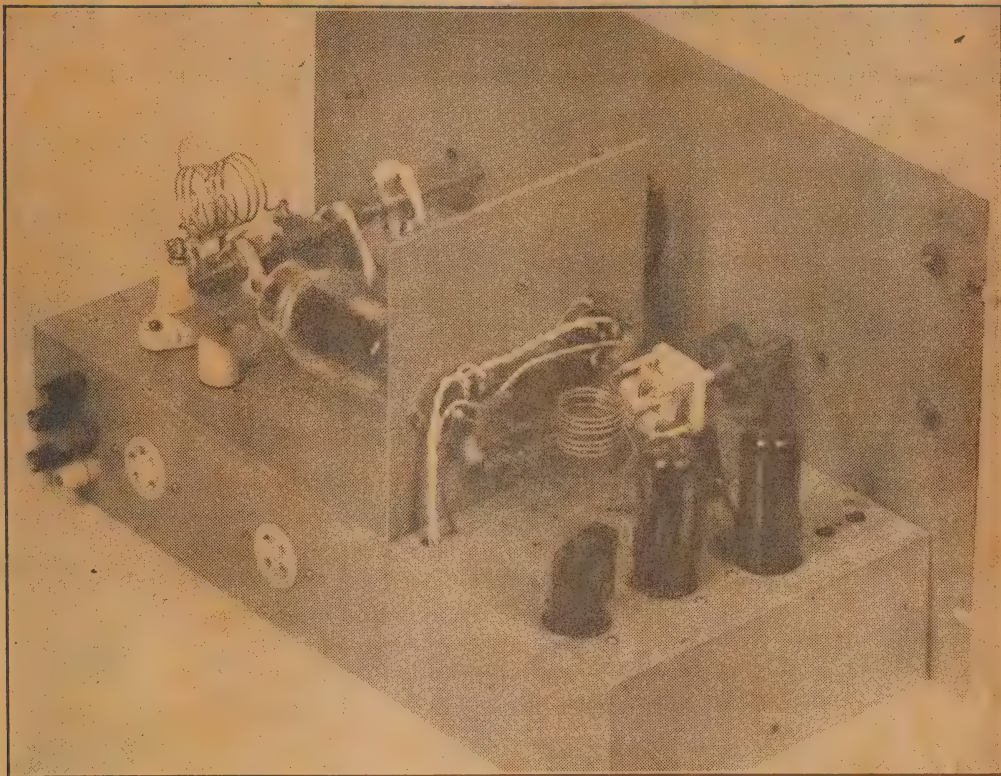

This rear view shows the doubler plate coil and condenser placed for convenient feed to the 807 grids. Grid leaks, chokes and screen bypasses for the 807's are mounted at the sockets.

enough output to drive a second doubler valve, but quite hard to get enough from the second valve as a tripler to drive the final, no matter how much output is available from the oscillator doubler.

VOLTAGES

The Tritet is therefore operated at quite modest voltages—about 150 on the screen and 250 on the plate—with enough output to produce about 1 mill current in the tripler grid circuit.

It is rather important to avoid pushing crystals on 8 mc as many will have found. Overheating, arcing, and even fracture from high grid current can be quite a problem. In our circuit, however, no 8 mc crystal has refused to function, and most of them were home ground to frequency.

The secret in adjusting any Tritet circuit is in the cathode coil. This must be tuned to a frequency higher than the crystal and, in fact, to as high a frequency as possible consistent with good output. As this circuit approaches the adjustment at which oscillation abruptly ceases, the output certainly increases. But just before oscillation stops there

a period of very high crystal current, which might cause damage unless avoided.

If, therefore, you use the voltages shown in the circuit, and keep the cathode circuit tuned to the highest practical frequency, you should not only drive the doubler adequately, but operate your crystals quite safely. If higher plate voltage cannot be avoided, see that the screen does not exceed about 150 volts. It is high screen voltage which really does the damage.

The doubler stage is really the heart of the transmitter because, unless it is operating properly, there will not be enough drive for the final stage.

GRID CURRENT

Assuming that the transmitter is to be modulated, we will require, according to the makers' figures, 8 mills of grid current with grid resistors of 22,000 ohms each.

In practice, however, it is possible to reduce the amount of drive represented by this grid current quite a bit before the 807's begin to misbehave, which misbehavior generally takes the form of "downward modulation," as it is sometimes called.

We have found the minimum grid current for two valves to be about 4 mills if they are modulated, although one can sneak as low as 2 mills and still get away with it without modulation, even if it does sound like murder!

GRID CURRENT

In practice, it should be possible to get 5 to 6 mills grid current from the doubler with 22,000 ohms resistance without manhandling the 6V6. In our case, we compromised between bias requirements for phone and CW, and dropped the grid resistors to 15,000 ohms. The grid current should now be getting on to 8 mills for both valves, and the stage should modulate quite satisfactorily.

In order to get this amount of drive, one must do a little coaxing, not only with the valve, but with the tuned circuits also.

The first thing is to provide adequate drive for the doubler. This isn't hard to do, fortunately, and apart from using as much inductance as possible in the Tritet plate coil, it needn't trouble us further. We have already specified voltages for this valve as being about 150 screen and 250 plate.



Radio Accessories



Price's Radio have the most comprehensive range of quality radio components in Sydney. Satisfaction guaranteed or full cash refund.

BULGIN PHONE JACKS



High quality English miniature jacks to fit standard 'phone plugs, 1" projection behind panel. Contacts silver plated.

SINGLE CIRCUIT 2/6

CLOSED CIRCUIT 3/-

Plugs to suit (PMG type) 3/-

CO-AXIAL CONNECTORS



A simplified type co-axial connector that is ideal for semi-permanent connections on amplifiers, transmitters, etc. N.F. finish with bakelite insulation. Overall length of each section 1 1/2".

2/6

per set.

FUSE HOLDERS



English holders for standard 1 1/2" glass fuses. Clips are silver plated and mounted on bakelite. Can be screwed directly to metal chassis.

SINGLE HOLDER 9d

DOUBLE HOLDER 1/-

MINIATURE LAMP HOLDERS



Miniature E.S. holders for torch and radio dial lamps. A type for all applications.

Type "A" 4d

Type "B" 7d

Type "C" 10d

SCALES



"Radiomac" scales are designed for use with condensers or volume controls. The circular types are finished black with brass markings, the others being black with plated markings.

Type A. Circular 2 1/2" dia. Graduated 0-100 through 180 degrees 1/6

Type B. 2" dia. as above 1/-

Type D. 1 1/2" x 1 1/2" Graduated 0-100 through 180 degrees 1/-

Type E. 1 1/2" x 1 1/2" Graduated 0-10 through 270 degrees 1/6

Type C. 2 1/2" x 1 5/8" Graduated 0-10 through 270 degrees 1/-


MINIATURE 2 PIN PLUGS & SOCKETS



The ideal connector for speakers, pick-ups, etc. Rectangular socket is 1 5/8" x 3/8". Plug is polarised, so cannot be inserted incorrectly.

1/6 per plug and socket.

"Radiomac" NAME PLATES

 

Dress up your equipment with these plates—Black with brass lettering. Size 1 1/4" x 1/4"—in the following titles:

Aerial
Attenuator
Band Set
Band Spread
Broadcast
B.F.O.
Buffer
Crystal
Current
C.W.
Doubler
Earth
Filament
Focus
Gain Grid
High
Input
Intensity
Key
Low
Microphone
Milliamps
Mixer
Monitor
Modulator
Neutraliser
Off-On
Ohms
Oscillator
Output
Pre-amp
Phone
Phones
Pick-up
Plate
Play-back
Power
Power-amp
Record
Radiation
Receive
Rectifier
Regeneration
Short-wave
Selectivity
Selector
Speaker
Sweep
Sync.
Tone
Transmit
Tuner
Volts
Vernier
Volume
Wave Change
X Shift
Y Shift
X Amp
Y Amp
Radio
A Battery
B Battery C Battery

4d each

TOYS for BOYS

A large range of toys is now on show. If unable to visit our store, write for illustrated catalogue.

BROWN HEADPHONES

Type "A" (as illustrated) with adjustable reed movement. 4000 ohms resistance, are the world's best 'phones.

£7/4/3

Type "X" is a popular priced 'phone that is ideal for the boy's crystal set, etc. 2000 ohms resistance, adjustable head-band and long cord.

37/6



TELETRON MOUNTING STRIPS

Without mtg. feet type 17.

No. Lugs per doz.

12 one 1/-
13 two 1/6
14 three 2/-
15 four 2/9
16 five 3/3
17 six 4/-
18 six 4/-



17



24

22

With mounting feet as types


22, 24, etc.

No. Lugs per doz.

22 two 1/6
23 three 2/-
24 four 3/-
25 five 3/6
26 six 4/-
27 eight 5/-
28 seven 4/6



28

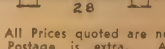

All Prices quoted are net. Postage is extra. Any surplus forwarded with order will be refunded with goods.

CLIX PLUGS & SOCKETS



Best quality English. Plug has helical slots to ensure good contact. Red or Black.

Socket 74d. Short Plug 74d. Long Plug 9d.

BULGIN INDICATORS

A high grade panel indicator with polished nickel plated escutcheon and 1" dia. red plastic lens. Lamp fitting for MES bulbs.

4/-



BOOKS

Write for our leaflet on Technical Publications which includes reprints from "Wireless World" on television—amplifiers etc.



Price's RADIO

5 & 6 Angel Place
SYDNEY

We will have to run the doubler harder than this, and with a screen voltage of 250, the plate should be at least 300, and up to 350 for full output.

Once again we should strive to use a large plate coil, remembering that it must also provide the out-of-phase voltages to drive the 807 grids. We found it most desirable to use a split-stator condenser to assist here, as this coil is subject to loading not only by the output capacitance of the 6V6, but also by some at least of the extremely high input capacitances of the 807's. We just can't afford, therefore, to add more circuit capacitance other than that required for tuning.

For the same reason, capacitive coupling from the ends of the centre tapped coil to 807 grids is impracticable, unless the coupling condensers are tapped well down the coil to avoid this capacitive loading. The actual tapping point for maximum drive and minimum loading is quite critical, and requires some form of variable coupling condenser.

COUPLING

A much simpler idea, and one which gives easier adjustment, is to couple the grids to the doubler tank with a couple of untuned turns of insulated hookup wire inserted at the centre of the tank coil. This method gives as much drive as obtainable from capacity coupling and much less loading from the 807 grids.

Some designers advise tuning the 807 grid circuits and inserting the untuned coil in the doubler plate circuit. Frankly, we don't think there is a great deal of difference, and either method should provide similar results.

The coupling coil is pushed into the tuning circuit until any further coupling begins to affect seriously the tuning of the tank coil. Generally speaking, this critical point will coincide with the greatest 807 grid current.

Two separate grid leaks have been used, because it is very awkward to use a single resistor from the centre-tap of the coupling loop. It is almost impossible to find the exact centre point of this loop, anyhow.

The grid leak values are far too high to have any shunting effect on the tuning coil.

DOUBLER OUTPUT

In brief, therefore, adjustment of the doubler stage means socking the grid with as much drive as the Tritet can offer without exceeding the stated voltages, putting plenty of volts on the doubler up to the limits mentioned, using low-C tuning circuits, and taking care with the coupling into the 807 grid circuits.


The layout allows for the Tritet coils to be accommodated under the chassis, and the doubler plate coil above it, right up against the 807 sockets. This means plate connections a couple of inches long, but these are much preferable to long leads in the actual tuning circuit. Tuning coils and condensers should

HOMECRAFTS

CARRY COMPLETE STOCKS OF
ALL RADIO COMPONENTS
RECORDING ENTHUSIASTS!



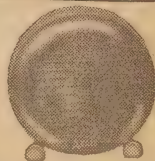The new Capitol De Luxe Traversing Gear. Overhead traversing gear for recording from 8 to 16 inch discs. Precision engineered. As illustrated. Price, 11 Gns.



Aegis Extension Speakers

Cream or Walnut

Walnut Cabinet only --- 34/9

Walnut Cabinet with Speaker 75/-

Cream Cabinet only --- 38/-

Cream Cabinet with Speaker. 77/6



"Byer" recording blanks.
Available in 8", 10" and
12" sizes.

CUTTING NEEDLES
RECORD PRESERVER
MICROPHONES
RECORDING MOTORS

"SCOPE" 6-second IRON

A remarkable soldering iron, ready for use in 6 seconds. Economical, only "on" while in use. Operates from 6 volt battery or 6 or 4 volt transformer. 43/6 ea.
Transformer 30/6 extra.


KITSETS

We will quote you for any
Radio and Hobbies Kitset—


CAR RADIO KITS
AMPLIFIER KITS

Try Our Mail Order Dept.

SPECIALS

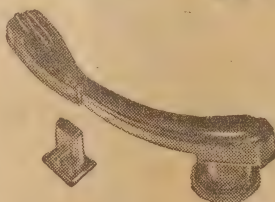

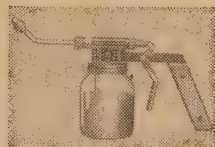PICKUP BARGAIN. Streamlined plastic lightweight. High fidelity, crystal pick-ups, with only 1 to 1 1-8oz. needle pressure. As illustrated. Reduced from 49/6 to 29/11.



THE NEW "ZEPHER" HAND SPRAYER

has hundreds of uses. As illustrated, small size, 24/11. Large size, 26/11.

HOMECRAFTS PTY. LTD.

98-100 CLARENCE STREET, SYDNEY.

Mail Orders, Box 5000, Sydney.

Phone: BX4451.

Also at 26 Hunter Street, Newcastle.

(Continued on Page 99)

The result of exacting research and design, R.E.L. were rewarded with the ultimate

ELECTRONIC MULTIMETER AND PROBE

... and so, they present to you the identical high efficiency instrument at an efficiency price.

Winning on all counts from functional perfection and inherent quality to the fine finish—it is individually built for a rugged lifetime of service and completely equipped for the New Era in Electronics. It supersedes Multimeters.

Quickly it finds the most elusive intermittent, noisy, open or short circuits.

Easily operated without fumbling, it is an absolute necessity to all busy Radio Men. Works from 230 to 260 volt A.C. supply independent of line fluctuations.

Accurately calibrated in separate colours on a 4" square dial (mounted in sloping panel) are direct readings on all tests including: All Voltages, Resistors, Condensers, Coils, Transformers, Valves, Speakers, High Resistance Leaks and Faulty Insulation, up to 1000 megohms. Has both internal and external diode.

Versatility plus sensitivity, enable testing and checking of all circuits: A.F., R.F., U.H.F., and A.V.C., under operating conditions—without disturbance.

The R.E.L. Instrument will read A.C., D.C., and—D.C. volts with input impedance over 10 megohms, for all D.C. ranges and only slightly less for A.C. ranges.

High Resistance D.C. Voltmeter.

0 to 3v 0 to 10v 0 to 30v
0 to 100v 0 to 600v 0 to 1800v

A.F., R.F., and U.H.F. A.C. Ranges

with internal diode or external probe.

0 to 3v 0 to 10v 0 to 30v
0 to 100v 0 to 600v

Resistance five ranges from 0.2 ohms to 1000 megohms.

Robinson Electronic Laboratories turn their

Reward To You!

£26¹/₂
PLUS TAX



N.B. Developed by specialisation, the Robinson Electronic Multimeter is individually constructed and not mass produced. With each instrument is a written guarantee which covers all components for a period of six months.



Immediate Delivery!

"TELE-TAPE" TAPE RECORDERS

A magnificent, high-fidelity sound recorder, custom-built to exclusive U.S.A. design. PLAYS FOR A FULL HOUR! Faithful reproduction of the spoken voice or music. Records at the flick of a switch from the radio, gramophone, or life. Most economical to run, refills are only 37/6 for half-an-hour's recording. Can be cut and edited as required. Immediate playback, and can be re-played an infinite number of times. For full details, write or call to Magnetic Sound Industries. Available on terms.

Exclusive! Vortex Speakers

Exclusive to Magnetic Sound Industries! A splendid job; bass reflex cabinet, complete with the latest loudspeakers giving any radio or gramophone 75% greater realism. Full frequency range, 30-5000 cycles. Individually styled, and custom-built. Vortex Speakers are priced from only 16 gns.

Specialists in Sound.

Magnetic Sound Industries specialise exclusively in sound recording. You are invited to call and discuss any problems you may have, our advice is at your disposal. You'll be interested in comparing at the same time our full range of sound recording instruments including the English Ediswan and the Pyrox. We suggest you build up a library of tape-recorded music of exclusive symphonies, famous USA dance bands, advance Hit Parade numbers, etc. Half-hour reels cost only 37/6.

MAGNETIC SOUND INDUSTRIES (Aust.)

1st Floor, 590 George St., Sydney. Opp. Regent (Sydney Radio Theatre). Open Saturday Mornings M3652.

FOR THE JUNIOR EXPERIMENTER

No junior radio man will get very far without a good knowledge of meters and their uses. This month we let the "Aerovox Research Worker" take you most capably through the paths of meter theory. The article follows aptly on the multimeter in the September issue.

ALTHOUGH the d.c. meter is a standard tool around the laboratory, service bench or "ham shack," its usefulness may be greatly enhanced by a better understanding of the principles underlying its construction and applications.

Despite the fact that the judicious use of electrical instruments is an unflinching hallmark of the skilled electronics technician, there is a tendency on the part of many to accept the meter at its face value without ever gaining an intimate knowledge of its internal functioning.

Actually, a complete familiarity with the capabilities and limitations of the d.c. meter can be gained only through a study of its electrical and mechanical characteristics. This paper will discuss these characteristics and point out certain precautions to be observed in the use of such measuring instruments.

Because the moving-coil, permanent-magnet type known as the d'Arsonval meter forms the basis of about 90 per cent of the meters in common use, being used to measure current, voltage and resistance with different auxiliary circuitry, the present discussion will be restricted to this type.

D'ARSONVAL MOVEMENT

The fundamental principle of all general types of electrical meters is the same; the electrical quantity to be measured is converted into a mechanical motion which is calibrated in terms of that electrical quantity by means of a scale and pointer. In the d'Arsonval type, direct current flowing in the turns of a coil suspended in a steady magnetic field produces an electromotive force which rotates the armature against the counter-torque of a hair spring—by an amount proportional to the current flowing.

A light pointer attached to the armature indicates the rotation of the coil, and therefore the current value, on a semi-circular calibrated scale. Figure 1 illustrates the usual form of this arrangement.

The current-carrying coil is wound on a lightweight frame or armature which, in turn, is supported between sapphire-jewelled pivot bearings which allow it to rotate freely. The electrical connections to the coil are made through spiral hair-springs at each end of the armature.

These fine alloy springs perform several vital functions. Besides providing the current-carrying path between the armature and the stationary parts of the meter, they provide the counter-force against which the meter torque or rotational force acts,

as well as supplying the restorative force which returns the pointer to zero when current ceases to flow.

The coil thus mounted is immersed in a strong magnetic field which is usually provided by a permanent magnet. The stability and permanency of this magnet are of

coil sets up a magnetic field around the coil which interacts with the fixed field produced by the permanent magnet to cause rotation of the coil.


The turning torque developed is proportional to the strength of the permanent magnet, the number of turns in the coil, and the amount of current flowing in the coil. The pointer deflection which results is determined by the strength or counter-torque of the spiral springs. At any given meter deflection, the torque produced by the interaction of the current in the coil and the magnetic field is exactly equal to the counter-torque of the hair springs and an equilibrium results.

Since in any given meter design the current in the coil is the only variable, the deflection of the pointer is directly proportional to the amount of current flowing. The scale graduations in properly designed d.c. meters of this type are therefore linear.

SENSITIVITY

The amount of direct current required to deflect the pointer to the highest graduation on the scale is called the *full scale sensitivity* of the meter. Instruments are manufactured in a wide range of sensitivities ranging from amperes down to a practical limit of about 20 microamperes. In addition to the above, high-sensitivity instruments are available with sensitivities of $\frac{1}{2}$ microampere for full scale deflection. Such high sensitivities are achieved by the use of powerful permanent magnets, lightweight multi-turn coils, and very delicate hair-springs.

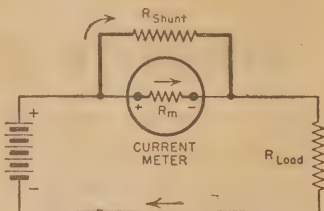Meters having sensitivities of one milliampere or less may be used for measuring any larger value of cur-



$$R_{Shunt} = \frac{R_m}{(N-1)}$$

R_m = Internal meter resistance.

N = Desired scale multiplying factor.

USE OF SHUNT RESISTANCE
TO EXTEND CURRENT-METER RANGE
FIG. 2

importance, as well as the uniformity of the magnetic field produced between its poles.


The pole tips are usually semi-circular in shape to fit closely around the moving coil. The uniformity of field is greatly improved by the use of a cylindrical core of soft iron mounted in the centre of the armature so that the moving coil revolves around it.

The indicating pointer is affixed to the armature at one end and a system of small adjustable counterweights is used on the tail-piece and cross arm of the pointer to balance the complete armature assembly. The angular movement of the moving coil assembly is restricted by a set of cushioned stops.

The completed assembly is extremely delicate and precise. It is interesting to note that most of the components serve several purposes. For instance, the armature frame not only provides the form upon which the current-carrying coil is supported but is also a closed-loop conductor in which eddy currents are induced which oppose the motion of the armature and so provide *damping* of the meter movement. Excessive over-swing or oscillation of the pointer is thus avoided.

THE CURRENT METER

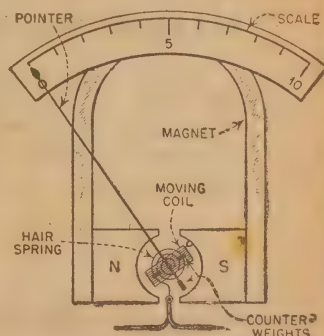Essentially, the d'Arsonval meter is a current measuring device. The flow of current through the moving



ESSENTIAL PARTS OF D.C. METER
FIG. 1

Summertime is Portable-time

Add to your popularity this summer—complete your outings to the beach, etc. with your own home built portable radio set. These kits are easy to assemble and give outstanding performance.



SPRINGTIME PORTABLE

This is not a new kit but has proved so popular over years we still recommend it for outstanding performance. Using RF stage, miniature 1.4v valves, large speaker for tonal quality and an attractive cabinet in leatherette. The complete set is only 13 x 8½ x 5½.

SENIOR PORTABLE

Using miniature valves

2—1T4

1—1R5

and an RF stage

1—1S5 1—3V4

for improved performance under difficult conditions. A 6-inch speaker for improved tone.

Cabinet Size 12½ x 8½ x 6½.



HANDY TALKIE

A truly miniature portable cased in leatherette but with improved performance using 5 miniature 1.4V tubes and an RF stage.

BATTERIES

... to re-equip your portable for the coming holiday season — make sure you have plenty of spare batteries on hand. We recommend Diamond miniature and standard batteries for all types of battery receivers.

JOHN MARTIN PTY. LTD.

116-118 Clarence St., Sydney. 'Phone BX5061 (5 lines). Telegrams: "JONMAR," Sydney


rent by the proper use of *shunts*. If a conductor having a resistance equal to the internal resistance of the meter is connected in parallel with it, the current will divide equally between the two paths and hence twice as much current will be required to give full-scale deflection of the meter.

If a shunt is chosen which has one-fourth the resistance of the meter coil, the currents through the parallel resistances divide in the ratio of 4 to 1, and since only one-fifth of the total current flows through the meter, its full-scale indication is multiplied by a factor of five.


Figure 2 shows the connection of a shunt to a direct-current meter and the equation commonly used to determine the shunt resistance required to extend the scale by a factor N . The internal resistance of the meter may be determined from the published characteristics of that type, or by measurement. In multi-range instruments it is usual to select shunts which multiply the scale calibration by multiples of ten for ease in reading.

D.C. VOLTMETER

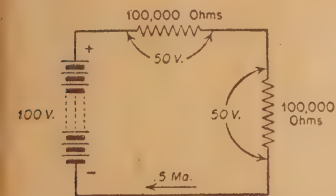The same basic movement which is used to measure direct current is also employed in voltmeters. In this



UNDISTURBED CIRCUIT CONDITIONS

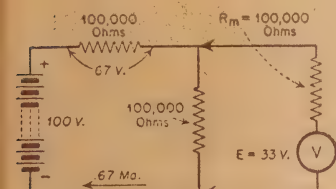


CIRCUIT "LOADED" BY VOLTMETER
FIG. 4

case, resistance is added in series with the meter in the manner shown in Fig. 3.

Such external multiplier resistors may be used with a high sensitivity milliammeter or microammeter to measure voltages ranging from millivolts to kilovolts. The meter is still performing its original function as a current measuring instrument, but in this case it is measuring the current which an unknown voltage causes to flow in a known resistance. The voltage is therefore determined by Ohm's Law (E equals IR) and the meter scale may be calibrated directly in terms of voltage.

Meters for voltmeter applications

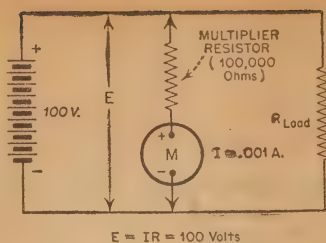

USE OF D.C. METER
AS VOLTMETER

FIG. 3

are classified according to "ohms-per-volt" ratings, i.e., the number of ohms which must be contained in the voltmeter circuit for each volt which the meter is to indicate. For example, to limit a voltmeter using a one-milliamperic basic movement to full-scale deflection when 10 volts is impressed, the total resistance of the circuit must equal 10,000 ohms, by Ohm's Law. A total of 15,000 ohms would be required for 15 volts full scale, &c.

Thus a .001 ampere meter one milliamperic full scale is rated at "1000 ohms-per-volt." The same meter can be made to read 500 volts full scale by using a 500,000 ohm multiplier in series with it. In such cases, where the required multiplier resistance is very large, compared with the internal meter resistance, the latter is usually ignored since the error introduced is much less than the reading accuracy of the meter.

However, if it were desired to make a 1000 ohms-per-volt meter read 1 volt full scale, it would be necessary to include the meter resistance in the total value of 1000 ohms required. If the internal resistance of the meter is 100 ohms, the correct value of the multiplier would be 900 ohms since a 10 per cent error would be introduced if the meter resistance were neglected.

Since the voltmeter is always connected across the voltage drop being measured, it is important to use an instrument having a total resistance which is large compared to the circuit to which it is connected. Otherwise, serious inaccuracies result since a low resistance meter "loads" the circuit being measured so that the voltage drops indicated are not those which exist in the undisturbed circuit.

A simplified example of such misuse of the voltmeter is illustrated in Fig. 4. To reduce such errors, basic meters having full-scale sensitivities of 50 microamperes (20,000 ohms-volt) or 100 microamperes (10,000 ohms-volt) are used in high quality voltmeters.

THE OHMMETER

Just as the d'Arsonval current meter is used to determine voltage when the current and resistance are known, it may be used equally well to read resistance by indicating the current which flows when a known voltage is impressed across an unknown value of resistance.

Such an instrument, calibrated directly in ohms, is called an "ohmmeter" and is widely used in a variety of circuit types of which Fig. 5 is a typical example.

In this circuit, a battery or other source of voltage is provided which is capable of producing a full-scale deflection on the meter when the test terminals (A and B in Fig. 5) are shorted. Variations in battery voltage and other circuit constants are compensated for by adjustment of a rheostat (R_2).

If an unknown resistance is inserted between the test terminals, the meter deflection will be reduced proportionately. The meter scale can, therefore, be calibrated directly in terms of the external resistance required to limit the meter current to that value.


When the unknown resistance is equal to the internal resistance of the ohmmeter circuit, the meter will read half-scale. The formula used for the calibration of this simple ohmmeter type is also shown in Fig. 5. For the measurement of extremely low or high value of resistance, more complex ohmmeter circuits are employed.

METER ACCURACY

Direct current meters are supplied in many degrees of accuracy according to the requirements of the application. Such applications vary extremely from meters for use as primary laboratory standards having rated accuracies of .1 of 1 per cent to mere indicators of the presence or absence of electricity.

Meters rated at better than 1 per cent accuracy fall into the "precision laboratory" category and should be used only in protected, "well behaved" circuits requiring such high accuracy. They are usually of the "portable" type which are used with the needle in a horizontal position for greater accuracy and have mirror-scales to reduce parallax errors in reading.

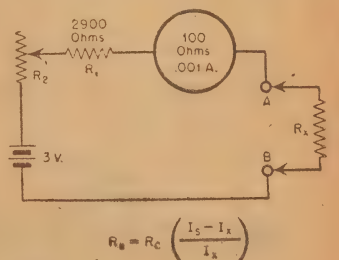In the accuracy range below 1 per cent are the great majority of "general utility" or "panel" meters which are the "work horses" of the electrical instrument family. They are usually mounted in test equip-



Where:

- R_x = Unknown resistance.
- R_c = Circuit resistance (A and B shorted).
- I_s = Meter current (A and B shorted).
- I_x = Meter current (R_x in circuit).

TYPICAL OHMMETER CIRCUIT
FIG. 5

University news:

SIGNAL TRACING & SET ANALYSIS



With the most up-to-date
and Versatile Instrument

THE SUPERTRACER MODEL AST

This is the most modern, up-to-date, and efficient service instrument that anyone could desire. It is easy to use and gives rapid and accurate location of faults in radio receivers and similar equipment. It speeds up testing, servicing, and production, and will rapidly detect faults which render a receiver inoperative, or which make it intermittent or lacking in sensitivity, or which cause oscillation, distortion, or hum.

The instrument comprises a two-stage tuned R.F. amplifier, a diode detector, and two-stage A.F. amplifier, and, of course, a loudspeaker and power supply. In addition, a vacuum tube voltmeter measuring up to 500 volts A.C. or D.C. at a resistance of 11 megohms on D.C. and 10 megohms on A.C. is provided. The tuning range of the R.F. circuits is 175 to 490 K.C., 550 to 1550 K.C., 1.5 to 4 megacycles, and 6.3 to 18 megacycles. R.F. sensitivity is such that input voltage of the order of a few millivolts may be detected on all ranges, so that the instrument is suitable for use in any district where alternating power mains are available. A capacity type R.F. multiplier in the input circuits in conjunction with the V.T.V.M. enables stage gain measurements to be made.

TEST PROBES: The R.F. test probe is fitted internally with a very small series capacity of a few micro-microfarads, so that it does not

produce an appreciative detuning effect when applied to the grid or plate of R.F. or I.F. stages in a receiver. The A.F. test probe is a conventional shielded lead for feeding A.F. into the tracer or A.F. out from the tracer for testing A.F. amplifiers or speakers. The D.C. probe contains a series 1 meg isolating resistor, so that the V.T.V.M. may be used to measure plate bias or A.V.C. voltage under actual operating conditions without disturbing the action of a receiver.

VACUUM TUBE VOLTMETER: The V.T.V.M. features a centre zero scale for direct voltage measurement, so that voltages which are either positive or negative with respect to a receiver's chassis are instantly indicated without the necessity of reversing test leads or operating a reversing switch. Zero is at the left for alternating voltage ranges, and operation covers the audio frequency range. Voltage ranges are 0/5, 0/25, 0/100, and 0/500 volts at an input resistance of 11 megohms on D.C. and 10 megohms on A.C. ranges. In conjunction with the amplifying stages of the tracer, the meter will indicate R.F. or A.F. voltages down to a value of less than 1 millivolt. Indications are provided by a large, clearly marked rectangular meter with illuminated scale fitted in an attractive modern plastic case measuring 4½" x 4". The V.T.V.M. and tracer may be used simultaneously for observing signals at two distinct points in a receiver. This feature greatly facilitates location of intermittent faults. Operates from A.C. 220 to 260 volts.

RADIO & ELECTRONIC TEST EQUIPMENT

University

ment panels and switchboards in a vertical position. The average accuracy of this class of meters is about 2 per cent.

The accuracy rating of all d.c. meter types is usually given in terms of the percentage of full-scale reading to which the meter is guaranteed. A single range meter reading 100 volts full scale and rated at 1 per cent accuracy would thus read within 1 volt of the correct value at any deflection. At 10 volts this meter could, therefore, be in error by as much as 1 volt, or 10 per cent. Good engineering practice dictates that meters be used at a minimum of one-third full-scale deflection for this and other reasons.

POINTS TO WATCH

The manufacturer's nominal accuracy rating does not insure accurate results from a meter in the hands of an inexperienced technician or an instrument which has been subjected to abuse. The following tabulates some of the mechanical and operational factors which may cause large errors in the reading of d.c. meters of the d-Arsonval type:


(a) Stray Magnetic Field Errors. Since the deflection of the meter depends on the strength of the permanent magnet, serious errors may be introduced by stray magnetic fields from other meters, current carrying conductors, magnets and other ferrous materials. Expensive meters are usually provided with adequate magnetic shielding. Some errors are also caused by mounting small meters in heavy steel panels. Meters especially calibrated for such mounting are usually so marked.

(b) Balance Errors. The delicate system of counterweights which balance the moving-coil assembly may cause "zeroing" or reading errors if improperly adjusted. The balance of the movement may be checked by holding the meter in the three positions shown in Fig. 6. If the pointer does not indicate zero in each posi-

tion, the movement is not perfectly balanced. Unbalance is most serious in vertical mounted meters.

(c) Overload Errors. Permanent damage or burn-out may be caused by repeated or heavy overloads of the meter movement. Excessive current through moving-coil types causes heating of the coil and springs. Heating of the latter results in "annealing" or loss of spring tension which impairs accuracy. Overloads also cause "needle banging" which may damage pointer or pivots.

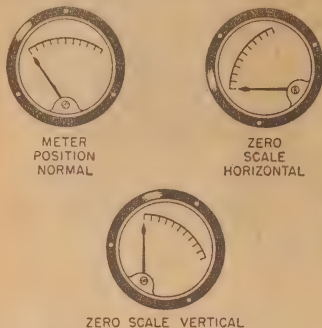(d) Sticky Movement Errors. The meter movement may be prevented from moving freely by several mech-



TEST FOR MOVEMENT BALANCE
FIG. 6

anical defects. Chief among these is chipped jewels or damaged pivots due to rough handling. Sticking may be manifest in the failure of the meter to reproduce a known reading when approached from values above and below the known value. Light tapping of the meter case is frequently resorted to as a cure. Meter sticking is also caused by small magnetic particles which may be gathered by the magnet of a meter which is removed from its case and left unprotected.

OPTAR— A New System of Optical Ranging

(Continued from Page 17).

the interplay of frequencies heard in the earphone.

Not the least impressive feature of the device is the extreme economy of operation. It is powered by a single flashlight cell, operating with a current drain of 60 millamps. This operates the motor and also supplies the primary impulses for an interrupter circuit producing 1000 volts from a transformer and a selenium type voltage multiplier-rectifier.

The drum speed is given as 2.5 rev. per sec, and the eight comb sectors each representing 45 degrees, produces 0.2 milliwatt at spot frequencies between 600 to 2000 c/s.

The device will operate for 100 hours from one cell and simply pressing a button puts it into operation. ("Electronics").

THE ELEMENTS OF BOOKKEEPING

(Continued from Page 39)

As time goes on you can see how valuable your ledger will become to you. It will not only tell you what your sales are for the year to date, but what they were last month, the same month last year, or the whole of last year.

Should you have an opportunity of purchasing a consignment of stock at a special price, you turn up your purchases account and can see at once whether such a purchase represents two, three or six months normal purchases. In this way you can get the advantage of special offers and also prevent over-stocking.

In a later article I propose to deal with "The Handling of Credit Accounts" and to show you how to keep a record of credit purchases and sales on credit. The records are quite simple and the same ledger that you have been shown in this article will be used.

RADIO ACCESSORIES

We specialise in Radio Parts and stock all reliable brands. We can supply: Coils, I.F.s, Transformers, Resistors, Tubular Condensers, Valves, Wires, Flex, Meters, Testing Equipment, Radio Manuals, Irons, Toasters, Pressure Cookers, Jiff Toasting Irons, Trimmers, Padders, Gang Condensers, Cabinets, Motor and Pickups, Record Changers, Solder Irons, Solder and Electrical Accessories, 4 and 5 Valve Mantel Sets—Portable Sets, Console Radio and Radiograms, etc. Mantel Console and Radiogram cabinets, TECNICO Electric Lawn Mowers, TECNICO PHILIPS and TELEVERTA Radio Sets.

DAVIS RADIO CO.

Wholesale Radio Distributors

1st Floor—Wembley House,
841 George St., Sydney.
Phone M3917
(OPEN SATURDAY MORNINGS)

Special Offer to
Campers, Hikers, Air Cadets,
Scouts, Guides.

R.A.F.


OFFICIAL

POCKET BOOK

This 320-page cloth-bound compendium is crammed full of authentic practical information on such a wide range of useful subjects as: camp erection; field cooking and recipes; weather information; airman'ship; signals, ciphers and codes; camp and fields works; knots and cordage; camouflage; health and sanitation; first aid treatment; explosives and small arms; relative ranks and rank badges of all Services; pennants and flags; field sketching; movement by road, rail and sea; fire precautions; weights and measures; aero-engine charts. This valuable book is yours for only two shillings, post free. Send now.

COLLINS RADIO

409 Lonsdale St., C1.,
Melbourne.

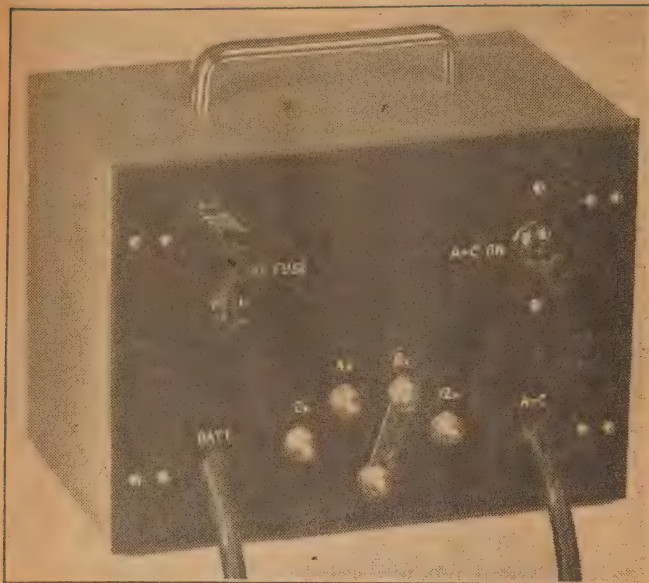

This view illustrates the general attractiveness of the finished job. Although the inclusion of an accumulator to show the charge rate is of secondary importance, there is room for it on the front panel. Note the use of the selector switch bar.

sary to use a transformer which suited the type of rectifier, bearing in mind the required output volts and the output current.

Unfortunately, the varied types and sizes of such rectifiers are too diverse to permit one design to cope with all of them. Accordingly, we made a survey of the catalogue types and, after considering many angles, we chose the bridge type LT53 as one which is not too expensive and one which, as a standard type, will be available for a long time to come. This rectifier, when coupled to a tapped transformer, produces a versatile charging unit capable of delivering a useful rate of charge current.

Although this rectifier is now a standard item, it is at present in the "just available" category and in

R & H BATTERY CHARGER

Here's a project which many readers have been waiting for — a battery charger designed especially for use around the service bench, the garage and the home workshop. It will charge accumulators ranging from 2 to 12 volts at the useful rate of 3 amperes. It is simple to construct and draws a minimum of current from the power mains.

MANY years ago, when accumulators and eliminators were the order of the day, battery chargers were popular items. They could be bought in a variety of shapes and sizes and there were plenty of parts available for those who wanted to build their own.

The advent of a.c. type tubes changed all that, and to such an extent that it became difficult to get together enough parts to build even a simple charger for the car battery. This is of some consequence, in these days of rising prices, for the useful life of an accumulator depends very largely upon the maintenance given to it.

CARS AND CYCLES

In the case of cars and motorcycles, the engine-driven generators should keep the battery charged but it doesn't always work out this way if there are lengthy periods of inactivity or night parking. Apart from the inconvenience of a flat battery, its life is likely to suffer if left in this condition.

This is one instance where our new battery charger can come into the picture. It is portable, it operates from the a.c. mains, it can deliver a worthwhile charge rate of

NIT No. 5

3 amperes and what's more, it can cope with any size of accumulator from the single 2-volt cell up to the 12-volt size.

In the design of a unit like this, the electrolytic type of rectifier can be ruled out as a "messy" arrangement. A high current valve type rectifier can be set aside because of the heavy filament drain, leaving the metal rectifier as a logical choice. These are reasonably compact and require no other consideration other than adequate ventilation.

Three types of metal rectifier can be used, namely the half-wave, the full-wave and the bridge type. Many versions of these types have appeared in the shops, a goodly proportion being ex-disposals. Readers have used them for a variety of purposes but, in each case, it has been neces-

sary in some cases there may be a little delay before it will be procurable in all States. This also applies to the transformer and supplies will increase just as soon as the distributors get the stock position organised.

You will note that the tapings on the transformer take into account the variation of the internal impedance of the rectifier with applied voltage. The design figures are worth repeating. For one 2-volt cell, the RMS voltage of the transformer should be 8.5 volts, for two 2-volt cells the RMS voltage should be 10 volts, for three 2-volt cells the RMS voltage required is 11.5 volts and for six 2-volt cells the RMS voltage required is 17 volts. These RMS figures are for the open-circuit voltages at the tapings of the transformer when used with the LT53 bridge type rectifier. The transformer should be rated at a secondary RMS current of 1.4 times the d.c. mean current,

RESISTOR WATTAGE

The other component associated with these two major items is the ballast resistor. The 1 ohm resistor, in conjunction with the effective resistance of the transformer, provides the right amount of "ballast." This resistor will obviously carry the same amount of RMS current as the trans-

by Raymond
Howe

former secondary winding, which is 1.4 times the mean d-c current of 3 amperes.

Simple Ohms Law calculation indicates that something like 17 odd watts will be dissipated in this resistor when the full charge current flows. The 30 watt size is the largest available but nevertheless is satisfactory for the purpose.

Considering the circuit diagram as a whole, you will see that a neon indicator is connected across the incoming mains leads which attach to the primary winding of the transformer. This winding is tapped for 230 and 240 volts to take in any variations in the mains supply in different localities.

The tapped secondary winding has already been covered. These tappings are taken to a selector switch which is adjustable to suit the size of battery to be charged. In view of the current drain, we discarded the idea of using a non-shorting rotary switch, even though the paralleling of contacts would increase their current carrying capacity.

CONNECTIONS

Instead, we adopted the simple arrangement using five 3-16th inch brass bolts and a strip of brass slotted to enable it to be slipped under the washers at any of the four range positions merely by loosening the nuts a turn or so. The result is a cheap and yet effective switch.


The connections to the rectifier are clearly marked both on the circuit diagram and the rectifier itself. You should have no difficulty there. The outgoing leads to the battery are taken from the rectifier lugs marked with red and blue, the red being the positive lead and the blue the negative lead. A 5 amp fuse holder is wired in series with one of these leads. Although we have shown it as being in the positive lead, it does not matter in which lead the fuse is wired.

The front panel and attached tray-type chassis carry all of the components and wiring. The front panel is made up from 3-16th inch bakelite. A metal panel would have been cheaper but the general scarcity of self-locating insulating washers for the selector switch bolts swung the choice in favor of bakelite. Naturally, the front panel, the chassis and the neon indicator mounting bracket will be part of the kit for this unit. Incidentally, we have grouped the items on the front panel to enable a meter to be fitted if your ideas run in that direction.

HOUSING

The complete unit is housed in what we have previously adopted as our standard instrument case. Such standardisation lends for more ready availability of these items. The case is modified slightly in the way of further ventilation holes. In this respect we added two rows of 4-inch diameter holes along the back of the case, one row being about 1 3-8 inches from the bottom edge and the other being the same distance from the top edge. In addition to these,

CIRCUIT OF BATTERY CHARGER

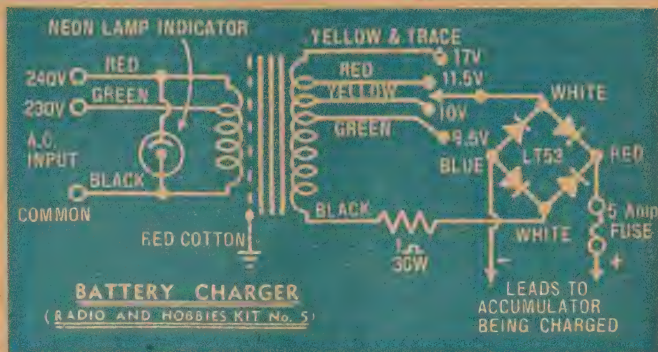

The simplicity of the circuitry is evident from this schematic diagram. The color-coding on the transformer leads is for the Ferguson PF265. Color-coding of other brands will be supplied with the transformer. Using a standard 15 watt pilot lamp in place of the neon indicator will result in additional heat being generated within the case.

four 1/2 inch diameter holes were drilled in the bottom of the case directly below the cooling fins of the rectifier, with another four 1/2 inch diameter holes directly below the ballast resistor.

The standard case has four indentations pressed into the bottom to act as mounting feet. If your case does not happen to have these, attach four rubber feet, otherwise the ventilation will be impaired. Standing the case on a couple of wooden slats will further improve ventilation under the case.

COLOR CODE

Coming to the actual constructional side, you will agree that there is really very little to be done. The inside photographs indicate clearly where everything goes. In mounting the transformer, straighten the leads and pass them through the two holes provided for them in the chassis and into each of which a grommet has been pressed. We used 3-16th inch bolts to hold the transformer although 1-8 inch size could be used if washers are placed under the head.

Sort the transformer leads out according to the color code supplied and lay them into place. Commenc-

ing with say, the heavy gauge secondary leads, trim them to a suitable length one by one and remove the outer spaghetti covering and the enamel coating on the wire to a distance of about 3/4 inch. You will notice that there are two wires for each tapping, one coming out from the winding and the other returning. Bare both wires and twist the bared portions together so that they make good contact. It is a good plan to tin and solder them after being twisted together.

Place the bared portion between two washers under the head of the appropriate bolt in the selector switch, bending the wire around in a clockwise direction to avoid being ejected by the turning of the bolt head. See that the wire under one bolt head does not short to an adjacent bolt.

SWITCH BOLTS

Each bolt in the selector switch carries five 3/16th washers and two nuts, two of the washers being under the head at the back of the panel, the third between the first nut and the outside of the panel, the remaining two being between the two nuts.

The leads from the primary winding of the transformer are soldered to a 6-tag mounting strip to which


PARTS LIST

- | | |
|---|--|
| 1 Standard instrument case 9 1/2" x 6 1/2" x 5 1/2" | 1 250v, 1/2W neon indicator lamp. |
| 1 Front panel, 3/16th inch bakelite, 9 1/2" x 6 1/2" | 1 6-tag mounting strip, 3 rubber grommets, 1/2" inside dia. |
| 1 Panel-mounting chassis, 7 1/2" x 5 1/2" x 1" with 5" side brackets. | 5 2" by 3/16th dia. brass bolts with 10 hexagon brass nuts and 25 brass washers. |
| 1 Power transformer, tapped primary for 230 and 240 volts, tapped secondary rated to carry 4.2A with off-load voltage tappings of 8.5v, 10v, 11.5v, 12v. (Ferguson PF265 or similar). | 1 1/2 doz. 8" by 1/2" brass bolts with nuts. |
| 1 12v. 3A bridge type metal rectifier, LT53. | 1 Piece scrap brass 2 1/2" by 7/16th in. for selector switch. |
| 1 0hm 30 watt wirewound resistor. | 1 Piece scrap metal 6 1/2" by 1 1/2" for neon indicator bracket. |
| 1 5A fuseholder, (Slydlok or similar). | 2 25 amp. battery clips, 1 3-pin flat plug. |
| 1 Cordgrip BC adaptor. | 3 yds. (approx.) 3-core rubber-covered power cable (approx. 40/36). |



for the **MUSIC LOVER...**
from SPECIALLY DESIGNED SPEAKER BOXES

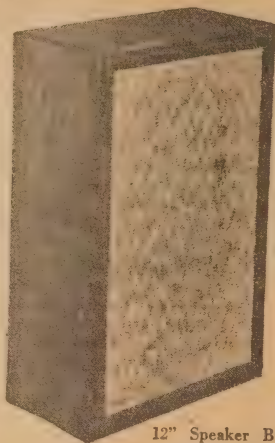OUR ENGINEERS HAVE OVER A PERIOD OF TIME DEVELOPED A SPEAKER BOX FOR A 12" SPEAKER FOR USE IN YOUR DRAWING ROOM.



12" Speaker Box
Item No. 68

● A NEAT AND COMPACT CABINET, POLISHED IN ANY COLOR SO AS TO TONE WITH YOUR EXISTING FURNITURE

● SOLIDLY CONSTRUCTED OF FIRST GRADE TIMBER, AND SCIENTIFICALLY PADDED THROUGHOUT, THE BOX MEASURES 24" x 36" x 12".

● Write for our illustrated literature showing this item and other Sound System Accessories.

STEANE'S SOUND SYSTEMS PTY. LTD.

Head Office: 60-80 MILLER ST., MELBOURNE. FJ 9140, FJ 9149, FJ 4543

And at 367 Kent St., Sydney. MA 2588, M 3136.



DO YOU KNOW!
AEGIS have been making
Coils and I.F.'s for ...

18
YEARS

and have the
most comprehensive
range of quality
components
available!


Obtainable from
selected wholesalers
throughout Australia

This Month We Feature ... COILS of the BC Band

Type M9 Aerial
" M10 R.F.
" M11 Osc.

Made to exacting standards from finest quality materials. Aegis Coils are second to none. The Broadcast coils listed above are mounted on a high quality moulded bakelite base with numbered silver plated pins protruding 5/16 of an inch. Permeability Iron Core is locked with retaining spring. The round covering can measures 2 1/2" high x 1 3/8" diameter, and is fitted with eyebolts (1-3) completed with nuts, with 1 3/8" mounting centres. Chassis hole of 1" minimum is required. All windings coated with high frequency lacquer. Remember, when ordering, specify type of converter Valve.

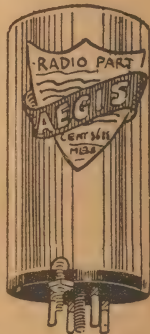Available from selected wholesalers throughout Aust.



AEGIS
MANUFACTURING COMPANY
208 LIT. LONSDALE STREET,
MELBOURNE, Vic.

also connects the incoming a-c mains leads and the wiring to the neon indicator lamp. Bend the lugs on the tag strip at right angles to give added clearance from the case bottom.

The fine multistrand red-cotton covered lead from the transformer is the internal shield and should connect to the chassis. The logical point is the tag of the 6-tag strip which bolts to the chassis under the same bolt which holds the rectifier.

Three-core rubber-covered cable is used for the a-c mains lead with the green wire connecting to the chassis. At the other end fit the conventional 3-pin flat plug so that the green wire connects to the "earth" pin.

BATTERY CABLE

The same type of cable is used for the leads to the battery. The black and green wires are connected together and called the negative lead. The remaining red lead is used for the positive merely to retain the somewhat standard color-coding for polarity. The 25 amp. size of battery clips are fitted to the free end of this cable. After stripping the rubber covering for a distance of about 9 inches, cut, say, the red wire a few inches shorter so that with the battery clips attached and the cable hanging free, the clips do not short together.

Both the battery cable and the a-c mains cable are clamped to the chassis at convenient points so that any unintentional strain or pull is not transmitted to the connections.

For those wiring runs between the ballast resistor and rectifier, the fuse-holder and rectifier and the selector switch and rectifier, use electrical wiring cable or the leads from a scrap length of the power cable. Five ampere fuse wire is readily available on the usual "household" card or, as an alternative, you could use one strand from the 40/36 wire in the power cable.

Well, that's all there is to it. It is quite straightforward with no headaches and represents but a few hours' effort.


When using the charger, always make sure that the battery clips are attached to the appropriate terminals of the accumulator, otherwise the accumulator will be damaged. The positive lead of the charger should connect to the accumulator terminal marked positive and so on.

SPECIFIC GRAVITY

When the charger is switched off, it is a good plan to remove one of the clips from the accumulator. Although the "back" current is very small—of the order of a milliamperes or so—the precaution is worth taking.

The condition of charge of an accumulator is best determined by measuring the specific gravity of the electrolyte with a hydrometer, although the terminal voltage reading will give some indication, provided that the accumulator is under a nominal load.

TWO VIEWS OF CHARGER UNIT

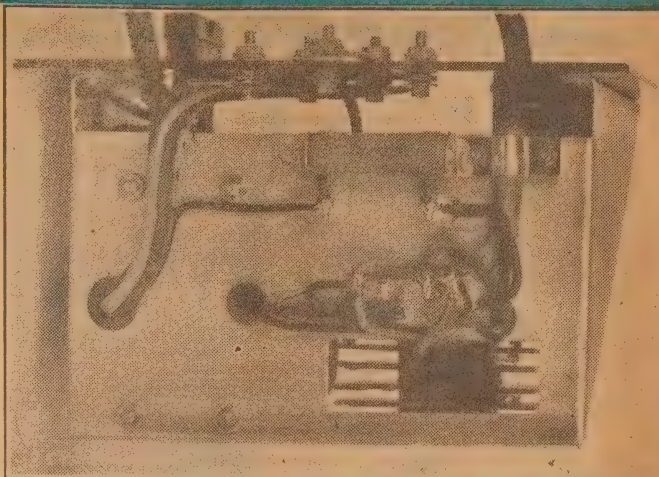


This underneath view shows the transformer wiring and the location of the ballast resistor. The standard 30 watt 1 ohm resistor is 1 inch longer than the one shown in the photograph. Note the holding clamp for the incoming power cable. The tag mounting strip is held under the bolt securing the rectifier.

There should, however, be some relationship between the specific gravity and the terminal voltage. A fully charged accumulator will reach a terminal voltage of 2.5 to 2.7 volts per cell (about 2.3 volts for an old battery), although this figure will drop to 2.2 volts or slightly less immediately the charging current is removed. The specific gravity of a fully charged accumulator will be in the vicinity of 1.270. This figure will be modified by the climatic temperature, being higher for cold climates and lower for hot climates.

If when the accumulator is fully

charged there is wide discrepancy between the actual specific gravity of the electrolyte and the normal figure, it could be an indication that strong electrolyte has been added at some time or that a large quantity of spilled electrolyte has been replaced with distilled water. Whatever the cause, it is necessary that the specific gravity of the electrolyte be adjusted.

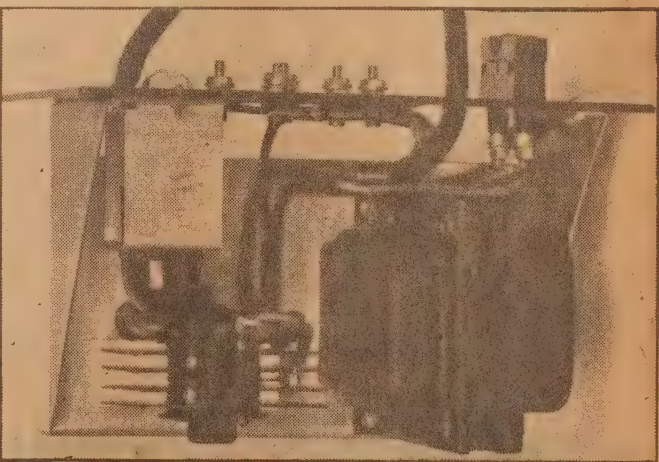Whichever way you go about obtaining or producing the electrolyte always remember the very important point that water should never be added to acid in the mixing process. Always add acid to water.




The actual location of most of the components can be seen from this photograph. The clamp for the outgoing battery cable is held under one of the transformer mounting bolts. Note the make-up of the tray-type chassis and the ventilation cut-out underneath the rectifier.

Choose your equipment from this famous range!



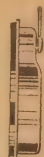MIC. 3 DIAPHRAGM-ACTUATED crystal microphone, specially designed for the reproduction of speech frequencies. With rising response from 1000 c/s, this microphone has exceptional sensitivity. Price: £1/8/2.




BACK



MIC. 19 SINTERCEL fulfills the requirement for a flat insert with good sensitivity and a frequency response 40/8000 c/s. Unaffected by vibration, exceptionally robust construction. Price: £2/13/0.



 
MIC. 18 MICROPHONE SPEECH INSERT provides high acoustic qualities with minimum bulk. Where exceptional slimmness is required, this insert is recommended. Price: £1/16/0.



MIC. 14 STANDARD SPEECH MICROPHONE INSERT with nickel-plate brass case which gives high corrosion resistance, mechanical strength and rigidity. Price: £1/8/2.



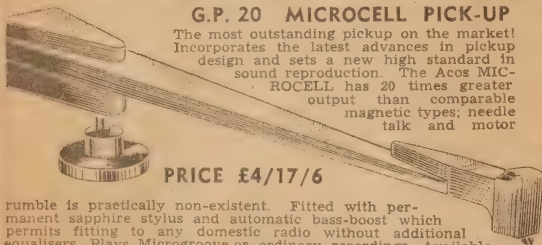TYPE "A" MICROPHONE. Specially designed for clear production of speech. Ideal for public address; office and factory call systems; amateur and mobile radio transmitters, etc. Price: £6/17/6.



G.P. 20 MICROCELL PICK-UP

The most outstanding pickup on the market! Incorporates the latest advances in pickup design and sets a new high standard in sound reproduction. The Acos Microcell has 20 times greater output than comparable magnetic types; needle talk and motor

PRICE £4/17/6

rumble is practically non-existent. Fitted with permanent sapphire stylus and automatic bass-boost which permits fitting to any domestic radio without additional equalisers. Plays Microgroove or ordinary recordings. Available from all Radio Stores.


CARTRIDGE ONLY (G.P.19) Price: £2/15/0

G.P. 10 UNBREAKABLE PICK-UP



PRICE £2/8/6

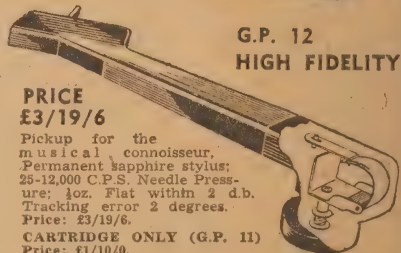Sturdy construction; ninety degree lift-back and exclusive needle pressure adjustment. Low Harmonic Distortion. Output 1.5 volt. Price £2/8/6. CARTRIDGE ONLY (G.P.9) Price, £1/2/1.



G.P. 12 HIGH FIDELITY

PRICE £3/19/6

Pickup for the musical connoisseur. Permanent sapphire stylus; 25-12,000 C.P.S. Needle Pressure; 4oz. Flat within 2 d.b. Tracking error 2 degrees. Price: £3/19/6. CARTRIDGE ONLY (G.P. 11) Price: £1/10/0.

AMPLION (A/sia) Pty. Ltd.

36-40 Parramatta Rd., Camperdown, Sydney. Phone LA2828.

SOLE AUSTRALIAN REPRESENTATIVES

A COURSE IN TELEVISION

All modern television systems use a composite signal containing not only the picture information but the synchronising pulses necessary to hold the sweep oscillators at the receiving end in step with those at the transmitter. This article suggests typical methods by which the synchronising pulses are extracted from the signal.

PART 18—SYNCH. SEPARATION CIRCUITS

THE need for synchronising pulses is self-evident. It is impossible to build simple oscillators which do not show some tendency to frequency drift and this applies to those which

ture on the tube screen. In terms of carrier amplitude, they extend into a region not occupied by the picture signals and all synch. separation circuits are, therefore, designed to take

The signal voltage from the last I.F. transformer, which needs to have a peak value of about 15, is fed through separate coupling networks to the detector and to the synch. separation tube.

This latter is a pentode whose operating conditions have been arranged deliberately to restrict the amplitude of signals it can handle and to show a very sharp "knee" at both the top and bottom bend.

The network of resistors is arranged to provide a moderate screen voltage but a very low value of plate voltage, typical figures being 50 and 10 respectively. A bleed current through the cathode resistor holds the bias steady at a value which approximates or slightly exceeds plate current cut-off for the tube under the particular operating conditions.

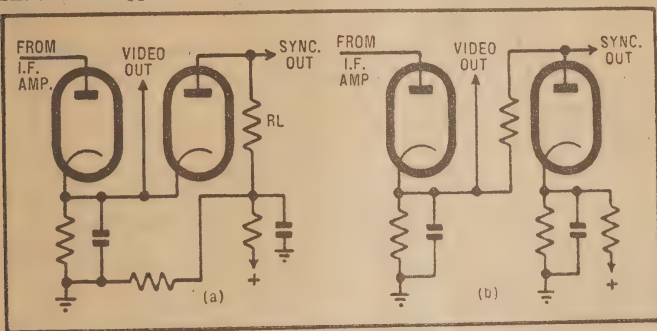


Figure 1. A pentode synch. separator for positively modulated signals.

control the vertical and horizontal spot movement across the television screen.

The technique, therefore, is to design the sweep oscillators to operate at approximately the correct frequency, then apply master pulses from the transmitter to trigger off each separate cycle of operation. This takes care not only of variations from one receiver to the next, but also of the smaller but inevitable variations in the transmitter sweep circuits.

It will be recalled that the exact nature of the pulses in relation to the carrier depends on whether positive or negative modulation is used.

In the case of positive modulation, the black level corresponds to about 30 per cent of the peak carrier amplitude and the synchronising pulses cut a rectangular slice into the remaining carrier down to near-zero modulation percentage.

SYNCH. PULSES

With negative modulation, the picture signal peaks up to about 75 per cent of the maximum carrier amplitude, the synchronising pulses rising in sharp rectangular wedges to the nominal 100 per cent value.

We need not concern ourselves here with the exact amplitude, duration or repetition rate of the pulses. The significant point in each case is that the synchronising pulses extend into the infra-black region, where they cannot effect the pic-

advantage of this amplitude difference.

For the sake of simplicity, it is easier to extract the pulses at a point where the signal is at a high relative amplitude and it can, theoretically, be done just prior to the detector or at a convenient point along the video amplifier chain. Pre-detector separation, however, requires considerable I.F. gain and a high detector input signal and it is therefore most attractive in designs which feed the detector output direct to the picture tube.

Figure 1 illustrates the principles of one circuit of this type, designed for use on the British positive modulation system.

LIMITING EFFECT

When the grid receives an input signal, the plate current rises rapidly to follow the wave front but, at a value of 3 or 4 volts, the plate current reaches its saturation value above which it cannot substantially increase. The effect is therefore to square off all modulation exceeding a peak value of 3 or 4 volts.

As already mentioned, the peak value may originally have been 15 odd volts and, assuming positive modulation, most of the modulation thus "squared off" corresponds to the picture intelligence. In other words, all that the tube succeeds in passing is essentially the synch. pulses representing the first 30 per cent of peak carrier modulation.

By shifting the bias so that the fixed value corresponds with the

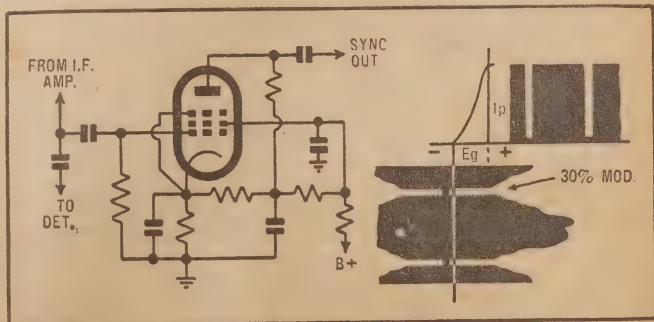


Figure 2. Diode separators for positive modulation which resemble (a) the series and (b) the shunt diode limiter seen in A.M. communication receivers.

POWER & VIBRATOR TRANSFORMERS

A.C. Vibs.						Retail
PF 122	240	6	220	40	6.3V @ 2A	33/6
PF 125	240	6	250	60	6.3V @ 2A	43/-
PF 119	240	6	325	125	6.3V @ 4A	62/-
PF 132	240	12	200	40	12.6V CT @ 1A	33/6
PF 126	240	12	250	60	12.6V CT @ 1A	47/6
PF 146	200,30,40	12	325	150	12.6V CT @ 2.5A	67/-

FILTER CHOKES

Induct. D.C. M.A. Res.					Retail
CF 100	50	1500	10		18/-
CF 101	30	870	25		18/-
CF 102	15	300	60		12/-
CF 103	30	420	60		26/-
CF 104	30	580	75		31/-
CF 105	15	250	50		24/-
CF 106	12	200	100		24/8
CF 107	30	360	100		34/8
CF 108	12	135	150		37/8
CF 109	20	225	150		35/-
CF 110	12	100	200		43/8
CF 111	16	165	200		45/10
CF 112	10	70	250		46/2

SPECIAL CHOKES

CF 113	5	70	250	Swinging choke	50/8
CF 114	1.1	23	375	Ballast choke	24/-
CF 115	.017	.6	12 amps	L.T. choke	10/-

OUTPUT TRANSFORMER TO VOICE COIL
Full Frequency Range (30-15000)

Code No.	Pr. Imped.	Sec. Imped.	Watts	Retail
OP24	5000 SE	8.4, 2.1, with feed back	5	44/10
OP23	3250 SE	12.5, 8.4, 2.1	10	65/1
OP19A	5000 PP	12.5, 8.4, 2.3	10	102/10
OP51	4500 PP	15.5, 12.5, 8.6, 2.7, 2	20	90/-
OP63	15000 PP	15, 3.75	15	100/-
OP64	10000 PP	12.5, 3.125	15	100/-
OP65	10000 PP	8.4, 2.1	15	100/-

OUTPUT TRANSFORMER TO VOICE COIL
Special Full Frequency (20-30,000)

OP25/40	10000 PP	40, 10	15	130/-
OP25/16	10000 PP	16, 4	15	130/-
OP25/15	10000 PP	15, 3.75	15	130/-
OP25/12	10000 PP	12, 3	15	130/-
OP25/10	10000 PP	10, 2.5	15	130/-
OP25/8.4	10000 PP	8.4, 2.1	15	130/-
OP66	5000 PP	8.4, 3.7	15	130/-
OP67	5000 PP	15, 6.5	15	130/-

OUTPUT TRANSFORMER TO LINE—

Full Freq. Range.

OP22	3250 SE	500, 125, 8.3	10	65/1
OP19b	5000 PP	500, 250, 125	15	102/10
OP21	8000 PP	500, 250, 125	15	82/10
OP62	10000 PP	500, 125	15	100/-

OUTPUT TRANSFORMER TO LINE—

Special Full Freq. Range

OP25/500	10000 PP	500, 125	15	130/-
OP25/250	10000 PP	250, 62.5	15	130/-

VIBRATOR TRANSFORMERS

Code No.	Pr. V.	D.C. Out.	M.A. Buffer	Full Sec.		
VT 100	32	200	40	.005	Sync.	21/-
VT 101	6	90	15	.008	"	19/6
VT 102	6	150	25	.005	"	23/10
VT 103	6	200	50	.005	"	25/-
VT 104	6	250	60	.005	"	37/-
VT 105	12	250	60	.005	"	37/-
VT 106	6	300	75	.008	"	52/-
VT 107	6	250	60	.005	Sync. Low Rad.	30/6
VT 108	12	90	15	.008	Sync.	21/8
VT 109	24	90	15	.008	"	23/10
VT 110	12	150	25	.005	"	26/6
VT 111	24	150	25	.005	"	25/-
VT 112	12	200	50	.005	"	26/6
VT 113	24	200	50	.005	"	54/2
VT 114	12	300	75	.008	"	37/-
VT 115	24	300	75	.008	"	55/6
VT 116	24	250	60	.005	"	30/-
VT 117	12	250	60	.005	Non Sync. Low Rad.	31/-
VT 119	32	150	25	.005	Sync.	25/6
VT 121	6	180	30	.005	"	25/4
VT 122	6	400	50	.005	"	50/-
VT 123	12	320	125	.005	Sync.	63/3
VT 124	32	250	60	.005	"	30/-
VT 127	6	200	50	.005	Sync. Low Rad.	25/8
VT 128	12	250	60	.005	Sync. Low Rad.	38/-

RECEIVER POWER TRANSFORMERS

Code No.	Prim. H.T.V.	M.A.	Filaments	Retail
PF 135	240	150	30 6.3V @ 2A, 5V @ 2A	24/-
PF 108	240	325	45 6.3V @ 2A, 5V @ 2A	30/-
PF 198	240	285	50 6.3V @ 2A, 5V @ 2A	30/-
PF 151	200, 30, 40	285	60 6.3V @ 2A, 5V @ 2A	34/-
PF 165	200, 30, 40	385	60 6.3V @ 2A, 5V @ 2A	39/10
PF 170	200, 30, 40	385	80 6.3V @ 2A, 5V @ 2A	39/10
PF 168	200, 30, 40	385	80 6.3V @ 2A, 5V @ 2A	45/-
PF 130	200, 30, 40	285	100 6.3CT @ 2A, 6.3V @ 2A, 5V @ 2A	46/-
PF 150	200, 20, 40	385	100 6.3CT @ 2.5A, 6.3V @ 2A, 5V @ 2A	56/-
PF 152	200, 30, 40	285	125 6.3CT @ 3A, 6.3V @ 3A, 5V @ 2A	66/-
PF 181	200, 30, 40	385	125 6.3CT @ 2A, 6.3V @ 2A, 5V @ 2A	60/-
PF 174	200, 30, 40	385	150 6.3CT @ 2A, 6.3V @ 2A, 5V @ 2A	70/-
PF 173	200, 30, 40	425	175 6.3CT @ 3A, 6.3V @ 2A, 5V @ 3A	110/-
PF 140	200, 30, 40	385	200 6.3CT @ 3A, 6.3V @ 3A, 5V @ 3A	111/-
PF 171	200, 30, 40	385	250 6.3CT @ 4A, 6.3 @ 3A, 5V @ 3A	144/-
PF 201	240	225	50 6.3 @ 2A	29/11

LINE TO VOICE COIL TRANSFORMERS

MT111	500	Pr. Imped.	Sec. Imped.	Watts	Retail
MT100	600		12.5, 8, 2.3	10	36/9
MT101	500		4, 3	15	36/9
MT124	600, 500		4, 3, 2.7, 2.3, 2	25	36/9
MT125	600, 500		15, 12.5, 8.4, 6.5	25	66/-

MODULATION TRANSFORMERS

MT118	8000, 6000 PP	10000, 7000	25	86/-
MT119	8000, 6000, 3800 PP	10000, 7500, 6500	50	111/-
MT120	500 to 20000 in steps.	6500, 4500, 3500	50	206/-
MT121	500 to 20000 in steps.	500 to 30000	125	276/-

Output Transformer To Voice Coil—P.A. Range

Code No.	Pr. Imped.	Sec. Imped.	Watts	Retail
OP1	5000, 2500 SE	12.5, 8, 2.3	10	39/10
OP54	5000, 2500 SE	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	10	45/8
OP39	5000, 2500 SE	15	10	39/10
OP33	5000, 2500 SE	5, 2.7	10	39/10
OP41	5000 SE	3.7	10	46/-
OP53	30000, 20000	2.2	10	36/9
OP2	5000 PP	12.5, 8, 2.3	15	65/1
OP55	5000 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP3	6600 PP	12.5, 8, 2.3	15	65/1
OP66	6600 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP4	10000 PP	12.5, 8, 2.3	15	65/1
OP57	10000 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	73/10
OP5	10000, 6000, 5000 PP	12.5, 8, 2.3	15	65/1
OP58	10000, 6000, 5000 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	15	76/2
OP59	10000, 6000, 5000 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	25	93/8
OP60	10000, 6000, 5000 PP	15, 12.5, 8.4, 6.5, 4, 3, 2.7, 2.3, 2	32	116/8

OUTPUT TRANSFORMER TO LINE—P.A. Range

Code No.	Pr. Imped.	Sec. Imped.	Watts	Retail
OP1A	5000, 2500 SE	500	10	39/10
OP44	5000, 2500 SE	500, 250, 125	10	47/-
OP34	5000 PP	600, 300, 200, 150, 130, 100	15	81/4
OP6	5000 PP	500, 250, 125	15	65/1
OP7	6600 PP	500, 250, 125	15	65/1
OP50	8000 PP	600, 300, 120, 60, 30	15	126/-
OP8	10000 PP	500, 250, 125	15	63/1
OP8M	10000 PP	500, 250, 125	15	71/3
OP9	10000, 6000, 5000 PP	71.5, 62.5, 55.5, 56	15	65/1
OP10	5000 PP	500, 250, 125	15	81/10
OP12	6600 PP	500, 250, 125	25	81/10
OP38	6600 PP	500, 250, 125	25	140/-
OP12	10000 PP	76, 50, 36, 27, 12.5, 7.5, 3.6, 2.7	25	81/10
OP13	10000, 6000, 5000 PP	500, 250, 125	25	81/10
OP35	10000, 6000 PP	500, 4000, 8.4, 2.2	25	120/-
OP14	5000 PP	500, 250, 125	32	102/10
OP48	6600 PP	140, 70	32	117/8
OP13	6600 PP	500, 250, 125	32	102/10
OP15M	6600 PP	500, 250, 125	32	104/1
OP16	10000 PP	500, 250, 166, 125, 100	32	102/10
OP17	10000, 6000, 5000 PP	83.5, 71.5, 62.5, 55.5, 50	32	102/10
OP36	3800 PP	500, 250, 125	32	102/10
OP18	3800 PP	17.6	60	108/7
OP61	3800 PP	500, 250, 125	60	108/7
OP37	6400 PP	1000, 75, 25, 10, 8, 4	80	133/8
OP49	8800, 6000 PP	500, 250, 125	105	150/8
OP20	11600, 8400 PP	500	150	210/-
		500, 250, 125		276/-

ALL PRICES SUBJECT TO ALTERATION WITHOUT NOTICE

top "knee" of the curve, it is possible to produce timing pulses of the opposite phase.

While the circuit is essentially simple and versatile, its operating conditions must be critically adjusted to ensure consistent performance and to produce pulses which do not show an excessive picture signal content.

This same type of circuit can also be supplied with the rectified signal from a diode detector but this calls for an even greater signal from the last I.F. transformer and also sets up an inter-dependence between the polarity of the detector and the synchronising signals.

Diodes are commonly used in separator circuits, having the obvious advantage of simplicity. By applying an initial voltage to the plate or cathode, thus "biasing" the diode, it can be made to conduct over specific portions of the input voltage cycle.

Figure 2 illustrates two possible diode separator arrangements operating in conjunction with the detector and arranged to handle a positively modulated signal.

A "bleed" circuit from the H.T. line in figure 2a maintains the diode plate at small positive potential. The cathode is connected to the detector cathode, which produces positive going signals in the presence of an R.F. input carrier.

BURSTS OF SIGNAL

The idea is to arrange the circuit such that the two cathodes are more positive than the plate of diode 2 over the whole of the normal picture signal modulation. When the carrier amplitude suddenly drops to zero during timing pulse intervals, the cathode potential drops below plate potential and diode 2 conducts. Thus bursts of signal appear across the load resistor RL corresponding to the synch. pulses.

This type of separator has the known good qualities of a series diode noise limiter, the only complication being that some signal components can appear across RL by reason of the capacitance between the diode elements. To avoid

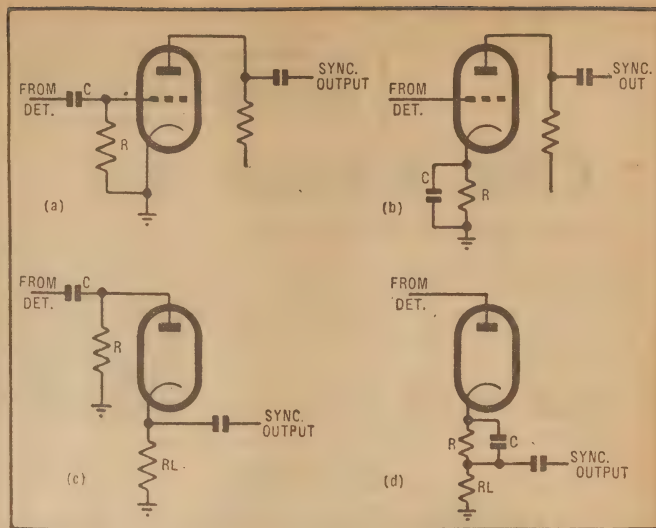


Figure 3. Synch. separator circuits for negatively modulated signals using amplifying valves (a & b) and diodes (c & d).

this effect, the separator diode needs to be a high permeance low capacitance type, while RL can have as much shunt capacitance as can be permitted by the operation of the circuit. In other words, the design problem is the same as that which governs the detector diode.

Figure 2b shows an alternative arrangement in which the separator diode functions after the manner of a parallel noise limiter. In this case, the cathode is biased to a point approximately equal to the peak amplitude of the pulse signals, as produced at the detector cathode.

The pulse wave-front, representing from zero to 30 per cent modulation, is fed to the synch. circuits via RL. Diode 2 does not conduct during this time, because its cathode is more positive than the plate.

The moment the plate tends to go more positive, as during the

example, the anode bend detector which is used in some English receivers. However, the reader will by this have grasped the general approach to the design requirements.

With negative modulation, the synch. pulses form the modulation peaks and, while the separator must still operate on the amplitude difference, its operation is reversed. The requirement is to select and amplify only the peaks of signal, ignoring the modulation content up to 75 odd per cent.

Figure 3 suggests various principles which are adopted to achieve this end. All assume that the output of the detector is positive-going and that it is applied to the synch. separator input.

Figure 3a has the appearance of a grid detector and that essentially is what it is, except that the input signal has already been rectified.

On the succession of positive peaks the grid draws current through R and sets up a charge across C, making the grid initially negative with respect to earth. The time constant of R and C is such that the grid "base" potential remains more or less constant and sufficiently negative to hold the valve to cut-off over the picture signal interval.

POSITIVE GRID

The grid swings positive and plate current flows only during the brief high amplitude synchronising pulses. Thus, the plate current is ideally cut off during the time when picture intelligence is being transmitted, rising steeply to form a pulse when the grid is carried positive by the high amplitude pulse on the carrier.

Obviously, the time constant of R and C is the key to successful operation of the circuit.

Figure 4b shows a rather similar but alternative arrangement. Here the high initial bias is obtained in

(Continued on Page 95)

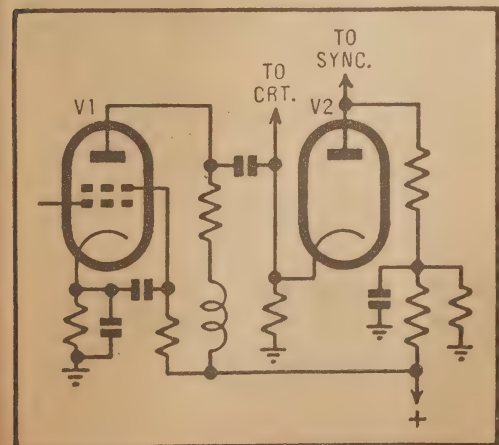



Figure 4. This simple diode and the final video amplifier gives a d-c restoration effect as well as synch. separation.

CAR RADIO KIT

As described in Radio & Hobbies. Complete with all components excluding aerial. Modern miniature valves—8 inch Rola Speaker. Will fit any model car.



PRICE £4/10/-

12-volt, 2-amp. Kit, 5/- extra.

In addition to the well-known standard BRAMCO range we can now offer these efficient miniature components.

For full details see opposite page.



GRAMOPHONE MOTORS

Motor and magnetic pick-up.
Auto-stop — 10" turntable.

£5/8/6

With Crystal Pick-up £6/-/-

10" turntable with magnetic pick-up. Auto-stop.

PRICE £6/2/6

Motor and magnetic pick-up.
12" turntable — heavy duty
motor. **ONLY £7/15/-**



£120

**Easily operated by
non-technical users.**

Complete with microphone, amplifier, and two speakers, enclosed in an attractive carrying case, this unit is capable of performing the following functions.

- (1) RECORDING FROM MICROPHONE
- (2) RECORDING FROM RADIO OR PICKUP
- (3) PLAYBACK FROM RADIO
- (4) PLAYBACK FROM COMMERCIAL RECORDINGS
- (5) A SMALL PUBLIC ADDRESS SYSTEM.

ON DEMONSTRATION AT
100 CLARENCE ST.

£120

HOMECRAFTS PTY. LTD.

DIVISION OF ELECTRONIC INDUSTRIES LTD.

98-100 CLARENCE STREET, SYDNEY. Also at 26 Hunter Street, Newcastle.

MAIL ORDERS: Box 5000, G.P.O. SYDNEY. PHONE: BX4451.

ANNOUNCING!

MIGHTY



MIDGET

The Bramco mighty midgets are well named "mighty" midgets—they are greatest in performance and smallest in size.

Use their new coils in your next set and prove beyond doubt this not extravagant claim.

FEATURES:

1 Smallest I.F. Transformer manufactured in Australia.

2 $\frac{1}{8}$ " connecting posts for easy wiring.

3 Protection against over heating of interior.

4 All aerial and R.F. Coils constructed with tapped secondary for use if required.

5 Polystyrene tropic proofed.

6 All Oscillator Coils available for various converters.

7 Backed by the Bramco name for consistency of performance.

THE BRAMCO RANGE

Replacement Speaker Windings (ask for complete leaflet).

Wire Wound Resistors (3 watt 1/3)
 (5 watt 1/10)
 (10 watt 3/9)

Tapped Crystal Set Coil 5/6
 R.F. Choke 1/9

AS ILLUSTRATED

Aerial Coil—standard	S.A.1	8/9d.
Aerial Coil—iron clad	S.A.2	9/6d.
R.F. Coil—standard	S.R.F.1	8/9d.
R.F. Coil—iron clad	S.R.F.2	9/6d.
Oscillator Coils		8/9d.
I.F. Transformer—standard	S.I.F.1	13/9d.
I.F. Transformer—I/C	S.I.F.2	14/9d.

MINIATURE

Midget Loop Aerial LOI		7/6d.
Midget Aerial Coil I/C	M.A.1	8/9d.
Midget R.F. Coil I/C	M.R.F.2	8/9d.
Midget Oscillator Coils		8/9d.
Midget Oscillator Coils on resistor		4/9d.
Midget I.F. Transformers	M.I.F.1/2	13/9d.

In preparation: 2nd edition of the FREE Bramco manual for radio servicemen.

Order a sample set of coils from your usual suppliers today.

MANUFACTURED BY BRAMCO RADIO COMPONENTS

REPRESENTATIVE PHILIPS AGENCIES: 27 HUNTER ST., SYDNEY. BW6436.



Here's your answer, Tom!

Tom is doing his level best to follow the "wheres and the whyfors" of our designs but it's hard going, because we seem to arrive at the most unaccountable conclusions. His immediate difficulty is to understand some of the back-bias arrangements we use.

TOM says that he can understand the general principle. If a resistor is connected in the B-minus lead, there must be a voltage drop across it, and one end becomes negative with respect to earth. Make the resistor the right value and you get the right bias. "All very clear," says Tom, "but from there on I get lost."

Well, you're not doing too badly, Tom. Plenty of beginners can't get

same thing to add a few weeks to the life of the batteries.

Then there's the diode/amplifier valve which may be quoted in the lists as having a plate current of several milliamps under certain conditions. But the chances are that, if resistance-coupled, it won't draw more than a half-milliamp, which is a very different story.

The IF amplifier in a superhet may draw from 10 to 15 milliamps "flat out," but the point is that it seldom has to work that way. Most of the time the set is tuned to a strong station, and the action of the AVC cuts the drain back to half the expected figure . . . and this is the one usually taken as a basis for the bias calculation.

So the story goes on from one stage to another; but, in the end, the designer has saved many milliamps, and the whole set may draw only 60 instead of something around 80. In a battery set the reduction may be from 18 or 20 to 10 or 12 in a typical case, which means a lot in terms of battery life.

So there you are, Tom. Even though you may not appreciate the finer points, at least you will understand the process by which the figures are reached.

The back-bias voltage always seems to be calculated for the output valve. How do you get on about valves which don't require as much bias?

It's as easy as falling off a log, Tom. Let's say that the output valve requires 15 volts of bias and that another valve somewhere only needs 3 volts. You simply arrange for the resistor to produce 15 volts with the current flowing, then establish a tap one-fifth up from the earthed end, where the voltage could be expected to be 3.

The tapping can be a sliding clip on the main resistor, or you can use two separate resistors which have the correct total value, but in the ratio of one-fifth to four-fifths . . . that is 1:4.

For example, if the total resistance had to be 500 ohms, then it could be made up of two resistors in series, one of 100 ohms and one of 400 ohms. On odd occasions we have used three or even four resistors in a back-bias network to meet the needs of several valves.

A further method is to use large resistors to tap off a proportion of the total bias for individual stages.

Thus, there might be 15 volts across a 500 ohm resistor, as already suggested. If two 0.1 meg. resistors are connected in series across the 500 ohm unit, the resultant value and the total bias would not be effected to any extent. However, at the junction of the two resistors $7\frac{1}{2}$ volts would be available and any other required value could be obtained simply by varying the proportion of the two resistors.

The method has the advantage that effective hum filtering can be provided by bypassing the junction of the high value resistors with comparatively small condensers. On the other hand, filtering in a circuit involving only a few hundred ohms is very much more difficult.

How can one measure the actual grid bias if it cannot be done with an ordinary voltmeter?

You can forget the "if," Tom, because bias cannot be measured easily through the usual high resistance grid circuit. An ordinary voltmeter has an effective internal resistance of only a few thousand ohms and its connection to the grid completely alters the operating conditions.

Where back-bias is used, the only way its value can be arrived at is by measuring the voltage applied to the bottom end of the grid resistor. Where a high resistance divider is used across the back-bias resistor



that far on their first attempt. But let's take your first question.

You always seem to allow for a lot less current in your designs than one would expect from valve lists. Are the lists wrong, or are you wrong, or am I barking up the wrong tree?

Well, Tom, the lists certainly aren't wrong, and we don't think we are. You'll have to draw your own conclusions.

Actually the question is quite an old one, and we have answered in various articles many times before this. But it works out this way:—

The valve lists show that a 6V6 will draw just about 50 milliamps of cathode current under the maximum class A conditions. In so doing, it will deliver some $4\frac{1}{2}$ watts of audio power.

This is more power than most ordinary receivers need to deliver, so designers quite frequently raise the bias by a couple of volts, sacrificing a spot of power output but saving 10 milliamps or so of high-tension current. It makes life easier for both the valve and the rectifier, and therefore offers a possible extension in service life.

In battery sets they often do the



it is necessary to measure the total bias, then check the values of the divider resistors and do a little figuring to work out the proportion available at the valve.

All this assumes that the valve is not drawing grid current, or that the bias is not being upset to some extent by a small leakage through coupling condenser or such like, connected to the grid.

Fortunately, one can get some idea of this by reading the plate current and then noting whether it changes

when a piece of wire is shunted across the grid resistor. If the plate current changes when the grid resistor is shorted out, it is pretty clear that slight current is flowing in the grid circuit and corrective action may be called for.

Incidentally we have not mentioned such specialised instruments as valve voltmeters which can be made to measure grid volts directly. However, it will be some time before you get around to using these, Tom.

If back bias is built up across a resistor, why doesn't it upset the operation of other valves which draw current through the same resistor?

Rather facetiously one could say . . . "Because the other valves never get to know about the resistor."

You see, the back-bias resistor is really a part of the power supply and the voltage drop across it can be lumped in with the voltage drop across the windings of the transformer, the rectifier and the filter system. The back bias resistor represents just a couple of hundred extra ohms but it is so placed that it makes available a negative voltage negative with respect to earth.

The only bias which can affect a valve is a voltage inserted between the grid and the cathode circuit. If, perchance, we return the cathode and the grid circuits both to earth, there just isn't any bias on the valve, no matter how much resistance and what-have-you is connected in the power supply.

Thus, it is quite possible to have a back-bias system for the output valve, zero-bias on other valves and cathode bias, if you like, on any that are left.

Some of your sets use back-bias for all the stages. If I were also to connect cathode resistors to some of these valves, would the bias on them be increased?

My word it would, Tom. Bias can be applied either as a negative voltage to the grid or as a positive voltage to the cathode. If a valve were operating with, say, minus 3 volts on the grid from a back bias source and you were to connect several hundred ohms of resistance in the cathode circuit, the cathode might easily go 3 or 4 volts positive with respect to earth. Adding the

two effects would produce a total bias of 6 or 7 volts.

In an RF or IF stage, this would lead to a drastic reduction in overall gain. In an audio stage, the provision of extra—or should we say excessive bias—would lead to distortion.

What happens in the case of detector and oscillator valves, which appear to operate without bias? Does this shorten the life of these valves?

Your expression "appear to operate" is very appropriate, Tom, but appearances can be deceiving.

Externally an oscillator valve or a grid detector do not appear to make provision for bias, because the grid return resistor is always taken back to the cathode or filament. Even where a cathode resistor is provided for a second tube section, as in a converter valve, the oscillator grid resistor ducks straight back to cathode, thus obviously avoiding bias for the oscillator section.

But here's the point: The moment the oscillator commences to operate, its grid swings positive over parts of the oscillation cycle, grid current flows and builds up a bias across the grid resistor. You can measure the current with a milliamp meter or measure the voltage with a suitable probe-type valve voltmeter. The condenser, which is always included, prevents the coil from shorting out the resistor and also has a storage effect on the grid voltage which is generated.

So there it is, an oscillator generates its own bias. As a rule, the plate voltage on an oscillator is limited or fed in such a way that nothing too drastic happens if the stage stops oscillating, but such is not always the case. An oscillator is best kept oscillating for its own protection.

As for a grid detector, it is supposed not to oscillate, even though it may be brought very close to the condition to obtain maximum gain. In this case you will always find that the plate is supplied from a low voltage supply or through a large resistor, so that high plate current cannot flow, even with no effective bias on the grid.

And, last, but not least, a grid detector is one of the few circuits which requires zero bias for its correct operation.

Transformer problems need no longer trouble you, consult our engineers for your requirements of

POWER, AUDIO, OUTPUT, INPUT, VARIABLE, POTENTIAL, AND CURRENT

TRANSFORMERS

No problem or transformer too large or too small, single or three phase. Standard 500 watt and 2KVA variable transformers available, prices on application.

Tape recorder heads, play back, record and erase. Astatically wound in heavy cast shield giving hum-free recording and play-back, finished in enamel or chrome plating also 4 sect 30 kc oscillator coils to operate with 6V6 or similar tube, all available immediately from

NOVA ELECTRICAL & ENGINEERING CO.

311 SUSSEX STREET, SYDNEY, MA1786.




**Tape it
Easy**

with

'DUREX' TAPE

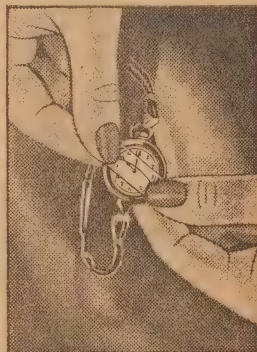Cracked your watch glass?
Protect the face temporarily with strong, clear "DUREX" Tape.



Handy Plaid Dispenser with
300 ins. 3-in. TAPE, 2/6
150 ins. 3-in. TAPE, 1/3

Also a Heavy-Duty Dispenser
at 15/- plus tax, and a refillable
plastic Hand Dispenser at 3/-
Tape extra.

SEALS WITHOUT MOISTENING
TRADE MARK

DUREX
BRAND
Cellulose **TAPE**

TRANSPARENT AS GLASS
AVAILABLE EVERYWHERE

Made in Australia by
AUSTRALIAN DUREX PRODUCTS
PTY. LTD., Lidcombe, N.S.W.

D7/110

**Pocket
Book**

The **STORYTELLER**
MAGAZINE **6^D**



It didn't matter very much, in the meantime, whether the basic amplifier was very good or just plain good.

But what do I mean by a "good" amplifier? The answer can only be very general but the group would include plenty of transformer-coupled triode outfits, the ever popular phase-splitter to pentodes-with-feedback circuit and even many single-enders within their power limitations. It must be assumed that the circuitry is right, that a good output (or interstage) transformer has been used and that the treble has not been poured down the drain by reason of Miller effect and capacitive losses.

NO PROPHET!

Take any one of these very ordinary amplifiers, fit it out with a good compensating pre-amplifier and it'll out-perform electrically the accessories you can buy today for home listening.

Not being a prophet (or the son of a prophet), I can't forecast whether future pickups, speakers, records and programmes will show up the difference between the good and the very good amplifiers. Of course, those who have invested in the big 807 triode jobs need have no apprehensions on this score, which is prob-

Let's Buy An Argument

So many letters have come to hand during recent weeks that we had to abandon any idea of displaying or quoting them all. Every one has been carefully read, of course, but for the purpose of publication, we have been forced to select excerpts only, from those which best represent certain trends of thought.

ONE such trend is likely to prove an embarrassment personally, unless something is done about it. Too many people are "agreeing with Mr. Williams" that expensive amplifiers are not warranted and you can't tell the difference anyway. Now wait a minute!

Carried to the bitter end, this might suggest that "anything goes" in the way of an amplifier and that readers who have spent a lot of money on expensive outfits have been sold electronic "pups."

SUBTLE DIFFERENCE

For heaven's sake, let's get the position straight. One objective of the first article was to dis-abuse those who were kidding themselves about "Subtle differences" between a lot of perfectly good amplifiers, whilst using records, pickups and speakers with very serious and very obvious limitations.

It is plainly futile to fret about fractional percentages of distortion in the amplifier, while 10, 15 or 20 per cent is being inflicted on the system by the devices fore and aft.

I contend that many preferences were based on the conflict (or combination) of random qualities, affecting distortion and frequency response; that the proper approach was to study carefully each link in the chain and to apply quite deliberately whatever compensation was necessary to achieve the required end result.

ably reward enough for the effort to build them.

One thing is certain, however. A lot of poor amplifiers will show up badly by contrast, under the strain of reduced background noise and wider dynamic range.


Turning now to some individual letters, I must acknowledge a lengthy and well-informed screed from Mr. Small, of Albury.

OUR EARS

He fully agrees with my remarks about phase and direct coupling but suggests that treble losses, due to Miller effect, &c., are of little consequence in the average system, which is limited—or has to be limited—to 7 or 8 kc at the top end.

That may be true enough, but the curves published with the Miller effect article told their own story. You can judge for yourself how important it is for those who have

by **W. N.**
Williams

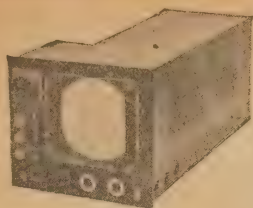

CATHODE RAY

Indicator Unit Type A1

This is an Ideal Unit to be converted to an oscilloscope or stripped for the excellent parts, valves, etc.


Parts are:

- 1—5BP1. Valve complete with socket and nu-metal shield.
- 6—6AC7. (1852) Valves.
- 3—6H6. Valves.
- 12—Potentiometers.
- 10—Block Condensers.
- 40—1 watt. I.R.C. Resistors.
- 1—3 position 2 bank Switch.
- 1—Toggle Switch.

All enclosed in neat metal case as illustrated.


Easily worth £25.

OUR PRICE £8/10/-

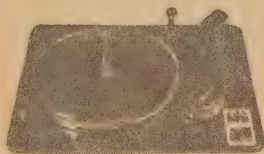

PLESSEY RECORD CHANGERS

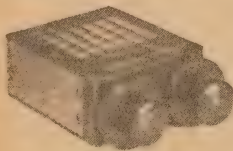We have a few of these well-known British Made Changers left. They play 10 inch and 12 inch records mixed, and have excellent tone. £11/10/-
The price is, each



BUZZERS

Excellent Army Type Buzzers with two adjustments as used in Don 5 and Freddie Telephones. Just the thing to learn the morse code. 4/6
PRICE, ONLY

Army Type Morse Keys 3/6

Complete Morse Code Practice Sets, built up on Testboard with battery 10/-



FERROTUNE FOUNDATION KITS

made by Kingsley Radio.

TYPE KFT1

Consists of Chassis, Straight Line Dial, Ferrotuned Aerial and Oscillator Coil Kit (no gang required) and 2 IF Transformers. Will build up into a really efficient and reliable radio. Usual Price £5/18/-.

OUR PRICE £3/10/-



FERROTUNE FOUNDATION KITS

TYPE KFT3

Consists of Chassis, square dial, Ferrotuned Aerial and Oscillator Coil Kit (no gang required), and 2 IF Transformers. Can be built into either straight or reflexed 4 Valve Broadcast Miniature Receiver.

Usual Price £5/12/-.

OUR PRICE £3/5/-



HEADPHONE SETS

Dynamic Headphone Sets with lead, in excellent condition.

These sets are easily worth £4 per set.

Our Special Price is

only 15/-

Transformers to suit head-phones. Each 4/6

Transformers to suit micro-phones. Each 4/6



LOOP AERIALS

Use low loss plastic covered wire. Suitable for all standard sized portables.

Easily worth 10/6.

OUR PRICE 4/-



CAR RADIO AERIALS

Job Line. 2-piece Aerials. Brass Chrome plated. Less Insulators. 5' 6" fully extended.

Easily worth 25/-.

OUR PRICE 12/6

Job Line. 4-piece Aerials. Brass Chrome plated. An excellent aerial which is extremely small when collapsed. Easily worth 45/-.

OUR PRICE 25/-



PHONE PLUGS & JACKS

As illustrated. P.M.G. Plugs, brand new and perfect 2/6

Single Circuit Jacks to suit 2/9

NOTICE

ALL PARCELS WILL BE SENT REGISTERED POST UNLESS OTHERWISE STATED

Postage or freight must be included with order.



Motor Spares Ltd

547 ELIZABETH ST. MELBOURNE.

True flat response—if you can afford and arrange it—is “safer.” It sounds consistently better and it is much less likely to pick out imperfections in the programme and hurl them at you with undeserved emphasis. In other words, there is no chance of the peaks in your own outfit coinciding with those already in a faulty signal.

So far so good, but at the end of his letter, Mr. Gordon attacks my ideas of theory and practice and, in so doing, leaves himself wide open. Judge for yourself.

Says Mr. Gordon:

"One may draw a circuit for a 6V6 calling for 12.5 volts bias and a 12,500 ohm load. To put this into practice one must have (A) a plate supply as immovable as Mt. Everest (B) a 6V6 that follows the curves exactly and (C), an impedance that is invariable at 5000 ohms."

Then again, "You can design a 15 valve amplifier with 30 db of feedback from output to input, but, boy oh boy, try to make it go in practice."

Well, Mr. Gordon, I have, during a brief existence, taken many valve curves for publication and know the care with which "average" valve samples are selected and operating conditions kept under control. All valves are held within certain tolerances during manufacture and "theory" will tell you, not only what a reference valve is supposed to do but what percentage variations can be expected from the published design centre values.

The same goes for the effects of reactive load, line variations and all the other snags your fertile mind can invent.


As for the amplifier with feedback, I agree that you can run over a circuit, mark the various grids and plates with plus and minus signs and assume that feedback will be negative with this point connected to that.

But that isn't design.

theory. The perpetrator would have blissfully ignored phase rotation and phase loop calculations. These latter would indicate the critical frequencies and the degree of feedback likely to produce instability.

Not that I blame anyone for failing to work it all out, because it is rather heavy fare. But the point is that the full theory is there if you want to use it. And, if my guess is any good, the aforesaid theory would forewarn you that the proposed design was impractical, thereby agreeing with the stuff called practice.

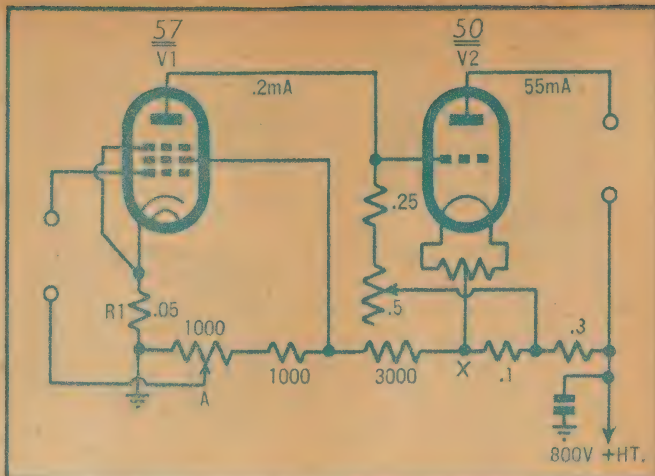Mr. Radcliffe, of Canberra, supports remarks about amplifier per-



A direct-coupled "Loftin White" type circuit suggested by Mr. Redcliffe. That

formance generally and stresses the importance of correct tone compensation. But, to demonstrate his impartiality, he proceeds thereafter to defend direct coupled amplifiers, which are apparently my "pet aversion."

I quote . . . "Of greater importance is the pickup, tone compensation system and the speaker. This becomes obvious when you consider that the cheapest mantel radio sounds better on live programmes than on recordings, while feeding the output of the same set into a first class speaker system (preferably multi-speakers with dividing networks) makes a staggering improvement.

"In short, have a good amplifier by all means but, if cash is limited, spend less on the main amplifier and spend more on the accessories.

"Even a Williamson sounds sour if there is hum . . .

"Speaker placing and room acoustics receive far too little attention . . ."


"Finally I'll stick my neck right out and utter a word in defence of direct coupling, or rather the old Loftin-White method . . . Not because I think it is better, but because I think it gives the best results per pound of capital outlay. The original Loftin, now practically forgotten, is worth studying in the light of modern conceptions of negative feedback."

There is no need to comment further on the first few points, but I can't let the reference to direct coupling pass.

The original Loftin-Y

The original North-white circuit was indeed very popular, but one must remember that it had to compete only with very dubious transformer coupling and with valve and component difficulties which made resistance coupling much more tricky than it is now.

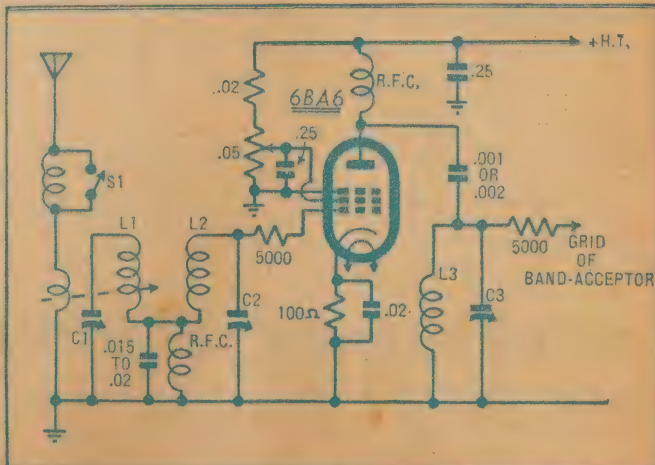The combination of triode output, the absence of questionable con-



An R.F. stage suggested by Mr. Hosken for use ahead of his band acceptor. It could be the basis of a very effective tuner.

BENDIX AIRCRAFT COMMUNICATIONS RECEIVERS RA10FA



Frequency range 4 bands 150-400 Kcs. 2.0-5.0 mcs. 2.0-5.0 mcs. 5.0-10.0 mcs. H.T. dynamotor 24v input 250v at 100 mA output. Small 24v A.C./D.C. motor. Filaments wired for 6v A.C./D.C. Socket ready mounted and space for rectifier and A.C. power supply. Valves used: 3-6SK7, 6K8, 6R7, 6C5, 6H6, 6K6. **£11/10/-**
Price, less valves F.O.R.
Remote control box with calibrated dial, etc., to suit above. Each .. **35/-**

4W FLUORESCENT LAMPS.

Colour: Blue. Length, 5½ inches. Ideal R.F. indicators.
Price, .. **2/6**
Each .. **25/-**
Per Dozen
Packing and Postage, 6d each.

A.W.A. CRYSTAL CONTROLLED TELERADIO TRANSMITTERS

15/20 WATT.
Frequency Range 2-10 mcs. Valves: 4-Type 6V6G; 1-Type 807.
Complete with built-in Vibrator supply for 12-volt operation. Ideal for Ships' communications, etc. **£25/-/-**
F.O.R. Complete
Excellent Condition.

DISPOSAL VALVES, TESTED

1K7G	8/6	954	12/6
3Q5GT	10/-	955	12/6
6AC7	14/-	956	12/6
6AC7	20/-	9001	10/-
6H6GT	7/6	12A6	10/-
6SH7	8/6	12SG7	10/-
6SH7GT	8/6	12SK7	10/-
6SL7GT	12/6	12SR7	10/-
6Y6G	12/6	EA50	7/6
7193	8/6	CV6	8/6
852	25/-	VT90 Micropop	10/-

NEW VALVES


1D8GT	15/-	7C7	11/6
6R8	15/-	7F7	11/6
6F6	15/-	83V	11/-
6GR8	12/6	811	70/-
6H6	10/-	828	35/-
6J3G	11/-	837	25/-
6J7G	12/6	966A	25/-
6K8G	12/6	879/2K2	15/-
6S07	12/6	1294	11/6
6X5GT	12/6	1293	11/6
7A6	10/-	VR54/EB34	5/-
		VR65A	5/-

COAXIAL CABLE

Polystyrene Insulation.
PS 11/M 72 ohm, 60ft. lengths. Only 5/18 inch O.D.
Price, per length .. **30/-**
Packing and postage: N.S.W., 1/6; Qld., Tas., Vic., 2/6; S.A., W.A., N.T., 3/6.

SCR 522 GENEMOTORS

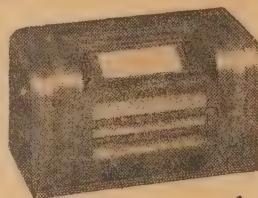28 volt input D.C., regulated and filtered output filtered D.C. 300 volts at .26 amps; 150 volts at .01 amps; 14.5 volts at 5.0 amps.
Completely shielded in metal case, 12 x 8 x 5 inches.
Price, F.O.R. Each .. **45/-**



Weight packed, 70lb.

BRAND NEW BREVILLE 5-VALVE DUAL WAVE RECEIVER

With 5 spare valves and vibrator cartridge FREE.

6 volt vibrator operated. Attractive walnut cabinet. Brand new, in original packing case. Ex-Amenities. 12 months written guarantee. Large, straight line tuning dial. Instruction sheet supplied with each model. 7-inch permagnetic speaker. Local, interstate and overseas reception.

USUALLY PRICED AT £45/17/6
OUR PRICE, F.O.R. .. **£29/10/-**

U.H.F. A.S.V. RECEIVERS AR301

Complete with 11 valves: 2—R.F. stages, 954 a.corn; mixer and oscillator. 2—955 acorns; 30 mcs. I.F. channel. 4—6AC7s; detector 6H6; cathode follower 6AC7; rectifier 5V4G.
Coaxial switching motors 24-volt D.C. Frequency range, 160-190 mcs.
Weight unpacked, 30lbs.

Suitable with minor alterations for conversion to F.M. Band (88-108 mcs.). Television Band (175-200 mcs.). 144 or 288 mcs. amateur bands.

Complete with valves as above in vented metal case, size, 7½ x 8½ x 18 inches.
Price, .. **£8/15/-**
F.O.R.

TELEPHONES Type H. Mk11

Field type complete with magneto, bells and sound-powered push-to-talk handset (no batteries required). Mounted in metal carrying case with strap. Size 10 x 5½ x 4½ inches.
Brand new in original sealed cartons. Weight packed 12lbs.
Price, F.O.R. .. **£3/17/6**

GENEMOTORS



Command type as illustrated, 28 volts, 1.1 amp. input. Output 250 volts, 60 mA. .. **32/6**
No. 11 type 12 volt input, output 350v 40 mA. .. **30/-**
12 volt input, output 480v. 40 mA. **35/-**
28 volt input, output 330v. 135 mA. **65/-**
28 volt input, output 350v. 350mA. **70/-**

TWIN METER CONTROL UNIT



Comprising: 2 imported 2 inch flush mounting meters, 0-5 mA., D.C. and 20V. D.C.; 2 7,500 ohm potentiometers; 7 position 10 amp. rotary switch; S.P.-S.T. toggle switch; plugs, sockets, shock mounts, etc.

Price, **£37/6**
Ea.
Packing and Registered

Postage: N.S.W., 1/9; Qld., Tas., Vic., 2/9; S.A., W.A., N.T., 3/9.

METERS

0-30 mA. D.C. 3-inch round flush .. **25/-**
0-30 volt D.C. 3-inch round flush with datum indicator .. **30/-**
0-300 mA. thermocouple. New .. **15/-**
0-3 Amp. R.F. thermocouple. New Imported 2" square flush .. **17/6**
0-4 Amp. R.F. thermocouple. New Imported 2" square flush .. **17/6**
20 mA. D.C. 300 amp. scale, 3in round flush .. **25/-**
20 volt D.C. 2in. square flush, imported. New .. **20/-**
40 volt D.C. 2in. square flush, imported. New .. **20/-**
50 Amp. D.C. 2in. round flush, imported. New .. **30/-**
20 volt and 200 volt D.C. 2in. round dual reading with leads. New .. **20/-**
Packing and Postage 1/6 each.

GENERATORS

12 volt 60 amp. D.C. .. **£9/10/-**
(F.O.R.) Each
Ideal for home lighting plants, battery charging, plating, etc.

PUSH BUTTON SWITCHES

5-pole each 2 pair of contacts. Made in U.S.A. Ideal for receivers, multi-meters, etc.
Price, .. **12/6**
Each
Packing & Postage, N.S.W., 9d; Interstate, 1/6.



ELECTRONIC EQUIPMENT CO.

Please add exchange to all cheques. Make money orders and postal notes payable at Lewisham. Sorry, no C.O.D.

—29b West St., Lewisham, Sydney.

OPP. END OF LEWISHAM HOSPITAL (ADJOINING RAILWAY LINE)

LM3555

lenses and the presence of some negative feedback combined to give the circuit what were then rather unusual qualities, provided you could find enough volts to drive it.

But I don't see that it escapes the fundamental criticism I levelled at direct coupling generally. You still have to set the bias by meter or by trial and error and any drift in one valve has a magnified effect on the next. Try to use modern high-slope types and the position becomes downright critical.

To be sure, there is some feedback present in the circuit, but it is current feedback and it raises the output impedance of the triode so that it begins to look like a pentode. This is hardly what we require for good distant response.

BAND ACCEPTOR

No, Mr. Radcliffe, direct coupling isn't a pet aversion, but I still think it's the hard way to go about building an amplifier, Loftinwhite notwithstanding.

Of course, I run the terrible risk, in so saying, of having the Editor "request" me to design a direct coupled circuit—objections notwithstanding!

My reference to Mr. Hosken and the complications of his Band Acceptor, recently featured, has called for a rejoinder which is being published forthwith (in precis.).

Says Mr. Hosken:

"To derive its benefits, there is no need for more than one series tuned band acceptor in a receiver. It would then be placed last in the sequence of R.F. amplifiers. Paradoxically, one of its benefits is simplicity."

A circuit is appended showing an R.F. stage with band-pass input and a tuned plate output circuit, which is intended to feed into the grid of a single band-acceptor stage. The aerial loading circuit is optional. The "wings" of the band acceptor selectivity curve could be used to offset the taper on the other curves.

TUNING SYSTEM

Tuning would require a four-gang condenser with frame earthed as normal, coupled to a single gang with frame insulated. All tuning coils would be standard broadcast components and ordinary trimmers would be used for alignment.

"By comparison with television and F.M. receivers, this must surely be classified as a simple circuit."

Fine business, Mr. Hosken. If the process continues, we'll end up with something every quality enthusiast will really want to build. Now that four-gang . . . ?

Mr. Hosken also comments on the possible effect of phase delay in the harmonic structure of the steep-fronted transients, pointing out that the effect may be more noticeable on these than on regular musical sounds. Clicks are converted to pips . . . &c.

I fully agree and it does not in any way affect my original statement that phase rotation and frequency limitation are alternative expressions of the same phenomena. To reproduce a steep-fronted transient

(Continued on Page 103)



SPECIALLY IMPORTED SUPER TORCH

Turning head torch No. 4733 is all chrome plated on solid brass case. The reflector can be adjusted to shine the light to any angle. It is equipped with a safety switch, adjustable focus, bottom cap holds spare globes, and clip for fixing torch to belt, leaving hands free.

Complete with 2 standard No. 950 "Eveready" batteries and globe. 19/6 posted

C.O.D. orders accepted. Spare globes available—7d each.

PORTABLE ELECTRIC PHONOGRAPH 240 VOLT A.C. MAINS OPERATED

This self-contained portable electric phonograph is housed in a leatherette covered carrying case and is complete ready to operate from any 240 volt A/C power or light socket. It has an amplifier with 8" speaker and electric phonograph motor and crystal pickup built into the cabinet. It is equipped with a volume control and on-off switch.

Supplied ready for use with 2 yards of power lead £15/19/6


at

Freight and packing £1 extra. Country

Orders accepted. No C.O.D. interstate.

Limited number available, as this instrument

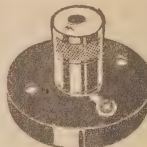is specially reduced from £21/10/-. Place your order now and avoid disappointment.



NEW INVENTION CRYSTAL DETECTOR

The "Red Spot" highly sensitive semi-fixed permanent crystal detector is now available from Radio House Pty. Ltd. for 9/6, 10/- posted. The "Red Spot" will take the place of the old type crystal and cat-whisker and give much better and more constant results. When necessary, it is easily adjusted by means of the knurled cap as illustrated.

£29/10/- BUYS THIS 7-VALVE DUAL-WAVE RADIO INCLUDING MAGIC EYE TUNING

This ready-wired and tested radio chassis is complete with valves and 12" speaker, and is especially designed for the reception of overseas stations. Ultra-modern circuit incorporates iron-core coils and I.F. transformers, automatic volume control, latest valves: 6SK7, X61M, 6AR7, 6SJ7, 6V6, 5Y3GT, 6U5; large modern edge-lit straight-line tuning dial, four controls: volume control, station dial, tone control, wave change switch; provision for phonograph pickup connections. Overall size of chassis 16" x 10" x 9 1/2" high. Price, £29/10/-, complete, less cabinet, plus freight. Mantel model cabinet to suit, leatherette covered, size approximately 21" x 13" x 13" high, £4/17/6.



THIS MONTH'S SPECIAL

Battery operated bed lamp in attractive coloured cases, green, white, blue and pink. Size 5" x 3" x 2 1/2". Attaches to the head of bed, complete with self-contained battery and pendant switch.

21/- or 22/6 posted

RADIO HOUSE

PTY. LTD.

2 STORES

296-298 PITT ST.
Opp. Water Board

6 ROYAL ARCADE SYDNEY.
Opp. Queen Victoria Bldgs.


Homecrafts

PTY. LTD.

**LARGEST STOCKS
KEENEST
BARGAINS FOR THE
RADIO
ENTHUSIAST**



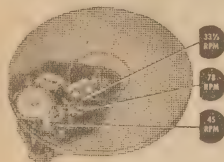"Collaro" Model 504 Gramo. Unit. Synchronous Motor Automatic Stop. Three Models Available.
With Crystal Pickup .. 26 0 0
With Magnetic Pickup .. 5 8 6
With High Fidelity Lightweight Pickup .. 6 0 0



TRIPLE SPEED GRAMO MOTORS

Imported American synchronous type T.S. Electric Motors; 33-1/3, 45 and 78 r.p.m. Complete with turntable as illus. ... £12/19/6



The new Palec VCT2 Valve and Circuit Tester. This outstanding instrument is now available for immediate delivery; 10,000 ohm per volt. Will test 800 types of valves. Price complete: £39/15/-, plus S.T. £3/6/3. Terms, £8/12/3 dep., 12/- weekly.




AMPHENOL STEATITE SOCKETS. Ceramic 5-Pin Sockets as illustrated. 1/11.




HYPERFIDELITY PICKUPS

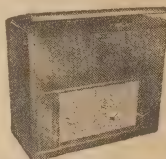Headmaster type Pickups. Complete with three cartridges, tonalizer and transformer ... £10 14 6
Replacement Cartridges ... £1 8 6
Tonaliser ... 2 16 0
Transformer ... 2 6 9
16" Arm only ... 1 19 6




RADIO CABINETS

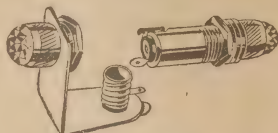Beautiful walnut piano finish standard model, £13/19/6. Model with deep well for record changer, £14/7/-. Also available in blonde finish Standard model, £16/9/6. Model with deep well for record changer, £16/17/-. Country and Interstate Clients add 15/- packing charge.




E.M.A. Type F (faceted jewels), wide vision type with nut and spacer for 3-inch hole mounting, 1/8 each. With back loading pilot light assembly, 3/9 each. Front loading type, 6/- each. Colors: Red, Green. Finish: Nickel Plated.

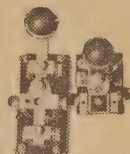Type FM Midgest Type, 3-inch diam., with nut and spacer, 1/8.



MORSE KEY BARGAIN

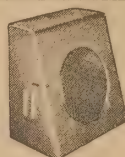Brand new Army type Morse Keys. Small type, as illustrated, only 1/11. Large type, as illustrated, only 2/11.



STREAMLINED STEEL SPEAKER BOXES.

As illustrated. With Brown Crackle Finish. Suitable for Speakers up to 8". As illustrated. Price 28/6.

RECORDEX RECORD RACK

The new improved gramo. record rack. Holds 25 10in. or 12in. records. Complete with index card and gummed identification numbers for records. Price as illustrated, 22/6



HOME BROADCASTER MICROPHONES

Will work with any ordinary radio. Adds fun to a party. Cut to only 7/11 each.



CAPITOL DE LUXE CHASSIS SOCKET PUNCHES


The best quality chassis punch in Australia. Made of best case hardened steel. Price, as illustrated, for standard 1 1/2" hole, 40/- For miniature valves, 20/- For new Innoval Series Valves, 3/-, 36/-.



PICKUP BARGAIN English Sheffield High Fidelity Moving Coil Pickups. Complete with matching transformer. Reduced from £4/19/- to 29/11, as illustrated.

COUNTRY AND INTERSTATE CLIENTS PLEASE ADD FREIGHT OR POSTAGE.

DISPOSAL VALVE BARGAINS!!

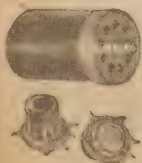

Type EF50 High Gain RF Pentode, 6.3V. 9-pin lock-in socket ... 15/-
Type EA50 6.3V. VHF Diode, suitable for the Vacuum Tube Voltmeter Test Probes ... 15/-
Type 954 6.3V. Det. Amp. Pentode Acorn Base. As illus. ... 15/-
Type 955 6.3V. Det. Amp. Osc. Acorn Base. As illus. ... 15/-
Type 7A6 Twin Diode ... 15/-
Type 807 Beam Power Amplifier ... 15/6
Type 100th 100 watt. Triode ... 49/6

Type STV L80/80 Type Multi Circuit Voltage Regulator 14/-
Type 42 SPT 4V. Cossor Screened Pentode 13/-
Type 5BP1 6.3V. Cathode Ray; 5" screen, elect. deflection. Plus sales tax ... 37/6
Type 7C7 Triple Grid 6.3V. 8-Pin Lock-in ... 15/-
Type 2X2 High Vacuum-Rectifier, 4-pin ... 29/3
Type 834 7.5V. 4-pin Power Amplifier ... 15/-
Type 6SH7 Sharp Cut Off RF Pentode ... 24/-
Type 830B 10V. Triode, 600 watt. ... 15/-
Type RL18 6.3V. Rigid Wire Base V.H.F. Triode 13/-

10% Discount to Licensed Amateurs.

290 LONSDALE STREET, MELBOURNE . . . CENT. 4311

TRADE REVIEWS AND RELEASES

"Q-PLUS" INTRODUCE NEW R-F STAGE BRACKET


Latest release from "Q-Plus" is a dual-wave coil bracket with R.F. stage, which is both compact and attractively priced. Employing single-hole mounting, it should be readily adaptable to most chasses.

THE body of the unit, excluding shaft and core screws measures $5\frac{1}{2} \times 2\frac{1}{2} \times 2$ inches. It is subdivided into three compartments housing respectively the aerial, R.F. and oscillator sections. A number of tag strips and flexible leads provide the necessary connections.

A three-position switch is used and there are blank sections at the top of each switch bank for handling dial-lights and pickup-switching as required.

All coils are fitted with miniature variable cores for inductance adjustment, with simple mica trimmers for alignment. High efficiency is claimed, with a sensitivity better than 1 microvolt on the broadcast band.

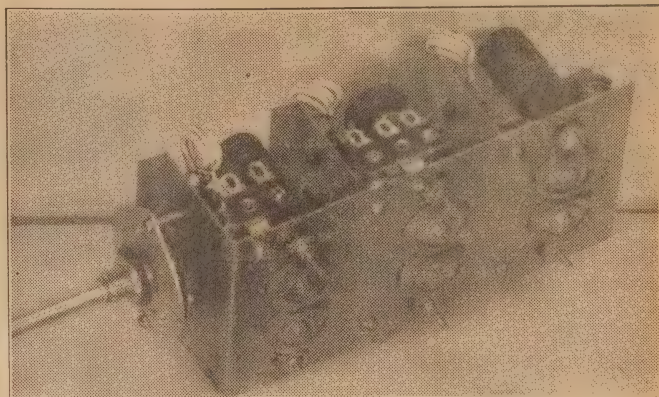Four different unit types are available at the moment, which cover the most popular converter



valves, including the 6BE6 and the battery converter type 1R5. Coverage includes the normal broadcast band and either 13-42 or 16-50 metres on the short waves.

The new units will be available through all "Q-Plus" distributors. Retail price is 95/-.

FILTER, R-F CHOKES FROM RCS


New components added to the R.C.S. line include a 60-milliamp filter choke and a series of multi-pi R.F. chokes.

TYPE number of the filter choke is type TC66 and it is rated at 20H., 60 milliamps, with a d-c resistance of 650 ohms.

The winding is carried on a trolitul



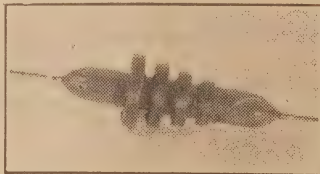bobbin which offers good protection against breakdown to the core. The corners are rounded to obviate



breakage, while "U" shaped terminations are provided for the leads to obviate difficulties which might arise from soldering.

An aluminium clamping bracket also provides mounting facilities.

The R.F. choke illustrated is the RF83 type, with four graduated sections and an inductance rating of 2.5 millihenry. Other types in this range have from 3 to 6 sections and inductance ratings from 1.7 to 9.0mH.

All these components are being handled by R.C.S. distributors.

'WINDOWMOUNT' AEGIS AERIAL

Intended for use especially in flats and offices, the Aegis "windowmount" aerial can be installed neatly and quickly.



THE problem, in steel-frame buildings is often to install the aerial in a position where it can pick up a reasonable amount of signal. Even a wire hung out the window is likely to be still in the "shadow" of the steel frame.

The new Aegis aerial solves this problem in a neat fashion. The complete kit includes a mounting bracket which can be fixed either horizontally or vertically on the window frame. A bakelite moulding, attached to this, supports a screwed, aluminium whip aerial approximately 7ft long.

This is connected to the receiver with ordinary insulated lead-in wire, as supplied. List price for the complete kit is 30/-. Supplies are available through all Aegis Distributors.

TRADE CATALOGUE FROM UNITED RADIO

WE have just received a specimen copy of the new illustrated U.R.D. Catalogue. This complete 52-page octavo publication is an invaluable guide for the radio and electrical trader. All items are listed and the catalogue completely in-

dexed. The retail price is given for each item, together with a discount code. Enclosed with every copy is a confidential discount code schedule.


Copies are available to the trade only from United Radio Distributors Pty. Ltd., 175 Phillip Street, Sydney.

MAXWELLS FIRST WITH THE LATEST

Midget POWER PACKS

These ULTRA MIDGET Power Packs are the only ones suitable for PERSONAL PORTABLES — STANDARD PORTABLES — or BATTERY RECEIVERS.

Replaces Standard and Minimax batteries.

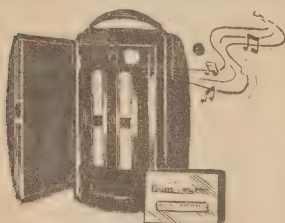

CONVERTS YOUR BATTERY PORTABLE TO AN ELECTRIC SET.



Size
4½ x 3½
x 1½"

PRICE

£5/19/6

Postage, 1/11


INPUT 200/240 Volts. A.C. FITTED with flex and plug.
ENGLISH manufacture.

Radio & Hobbies No. 1 Kit Set

5 Valve B/C Super-het complete with 8" Speaker.

£14/10/-

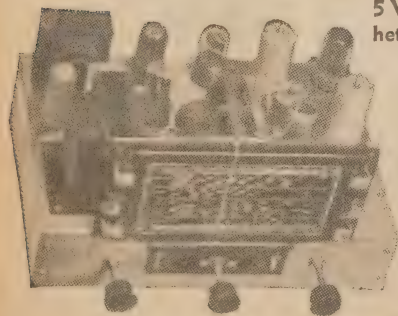This simple to construct set was fully described in R. & H. JULY issue.



SPECIAL OFFER OF STANDARD SIZE 5 VALVE SENIOR PORTABLE KIT SET



This Radio & Hobbies designed 5 Valve portable with R.F. STAGE **£14/17/6** is really a splendid performer and our special price includes cabinet, 6" ROLA SPEAKER, batteries, etc., to the last nut and bolt. Size 12½ x 6½ x 8½.

MAXWELL'S RADIO

48 ELIZABETH ST., MELBOURNE. CENT. 4913.

Same Day Despatch

Add Postage to all Amounts

NEW SPEAKER SOUNDS GOOD!

WIDE-RANGE ROLA 12-OX

A few months ago, we heard a new, wide range speaker at the Rola factory in Melbourne, and were impressed with its performance. A sample model of the speaker has now come to hand, and further tests indicate that it fulfills its earlier promise.

THE type number is 12-OX, indicating that the speaker is really a special version of the 12-0, already well known throughout the country.

This new speaker actually has three cones. The main cone is similar to that of the 12.0, but the surround has been treated with a softener which has reduced its main resonance to 50 cycles per second.

The second cone is a small, free-edged curvilinear type cemented to the voice coil. As an integral part of this cone there is also a dustcap which re-inforces the extreme top end of the scale.

An output transformer is not supplied with the speaker. The makers are quite happy for the user to connect via a high-grade component made by some reputable firm, as against doing the job themselves. The standard Rola transformer, while adequate for the 12-0, isn't good enough to cater for the extreme range of the 12-OX.

Testing this speaker with the audio generator shows a smooth bass response down to 30 cycles or so, without any pronounced cone resonance. The middle register disclosed no obvious peaks or tweets. There appeared to be a drop round about 5kc, the response rising again between 8 and 10kc. The cut-off was quite sharp at about 11½kc.

LISTENING TESTS

This general performance is very much like the imported twin cone speakers, and the 11½kc limit isn't really important with today's radio and records. It's plenty high!

On listening tests with a wide-range tuner, the high frequency response was immediately obvious in the predominance of the 10kc beat between adjacent stations. On "clean" programmes the reproduction was extremely "live" and realistic, but the distortion from poor programmes and records etc., was most pronounced.

To the seeker after quality, the Rola 12-OX will therefore impose the same requirements as have already been suggested for other wide-range speakers, with present sources of signal. With a wide-range tuner, some trap or filter will be essential in most locations to obviate the 10kc heterodyne.

Some limitation also may have to be placed on the treble response when the speaker is used to reproduce old or doubtful recordings.

In other words, the new 12-OX is not a speaker which should be bought and connected carelessly to any old receiver. The absence of excessive bass resonance and the extended treble response might

easily give the effect of distorted, "reedy" reproduction. It will need to be properly baffled, for example with a vented enclosure and preferably used with a treble filter system, which will allow the response to be varied to suit the programme material.

Supplies, when available, will be released through Rola distributors and trade houses. The retail price is under £6.



The new Rola 12-OX has three cones giving it an effective response to nearly 12 Kc and a bass resonance of approximately 50 cycles. Used with adequate baffling it provides wide-range listening for less than £6 retail.

Your Workshop is Incomplete

without these two
modern Electric tools

QUIRK'S SOLDERING IRON

—it's HOT in 6 seconds!



This revolutionary lightweight soldering iron is now available to you after years of painstaking research. It operates on an entirely new principle from 2.5/6.3 volts, A.C. or D.C., with the amazing heating time of 6 seconds on 4 volts—and this slender little iron gives a heat equal in effectiveness to that of irons with 150 watts rating! Because it is lighter and smaller than most, it offers greater ease and speed in handling. Working in a maze of delicate wires becomes easy and heat is applied only where and when it is required. Whichever way you look at it "Quirk's" Soldering Iron is the new idea for efficient, economical soldering.



QUIRK'S ELECTRIC DRILL

To the electrical handyman, the home cabinet maker or metal worker, this efficient drill brings accuracy at speed. It drills anything from composition board to steel, drives small wire brushes and sanding pads. This drill is light and compact with an easy grip switch. Available for 32, 50, 110 or 240 Volt supply.

Contact your local dealer or write direct to

QUIRK'S VICTORY LIGHT CO.
229 CASTLEREAGH ST., SYDNEY. 'PHONE M 3114



Gadgets and circuits which we have not actually tried out, but published for the general interest of beginners and experimenters.

A SIMPLE TONE COMPENSATING PREAMPLIFIER


In common with many other readers who have purchased lightweight magnetic pickups, Mr. H. N. Anderson of Toorak, Victoria, found that the results were not very pleasing when the pickup was fed into a standard medium gain amplifier without tone compensation. His solution to the problem is the simple pre-amplifier with compensation, the circuit of which is reproduced here.

HIGH quality lightweight magnetic pickups in general have a substantially flat output over their working range and at the same time their output is a good deal lower than that of crystal pickups or older magnetic types. At the same time, standard gramophone recordings are made with the bass end deliberately attenuated so that the playing time can be extended.

Without special provision for the new pickups, the amplifier output is apt to sound thin and weak.

Our correspondent noticed this circuit in a back issue of an overseas technical journal. The original used a pair of 6J5s but he found that these tended to be noisy and substituted a 6SN7-GT which completely cured the trouble.

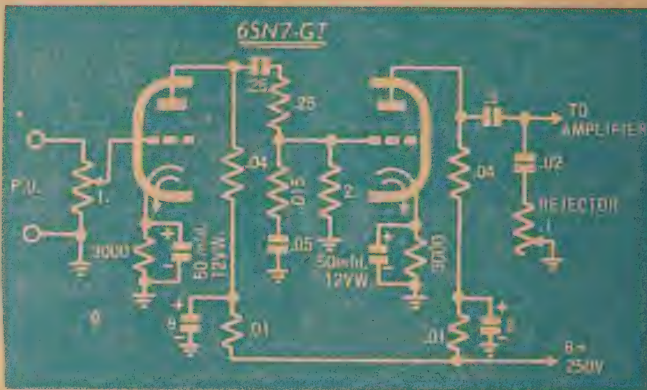Faults in the individual valves probably accounted for the trouble but it is worth remembering that the overall gain required for a light-



weight-magnetic is quite high and it is as well to make sure that pre-amplifier valves are in good condition.

The circuit is very simple and consists essentially of two triode amplifier stages. The volume control is in the input circuit but if this tends to cause noise when the knob is rotated it would be permissible in many cases to place it after the pre-amplifier.

Fixed bass compensation is achieved by a resistance capacity network in the plate circuit of the first valve and a variable top-cut tone control is included in the output circuit so that the scratch on some of the older

recordings can be attenuated. A pair of decoupling networks which are included to prevent motorboating complete the circuit. Note that most pickups will require a load resistance of something like 50,000 ohms. This can be connected in parallel with the pickup either at the volume control or at the pickup, as convenient.


ONE VALVE RECEIVER

Another reader, Mr. H. L. Briggs of Devonport, Tas., sends in the circuit of a one valve receiver about which he is very enthusiastic. Apparently the original used the 6 volt A609 triode but there are many other valves which could be used just as successfully provided suitable adjustment to the filament voltage is made.

The two volt type 30 is a good choice and frequently this valve will work quite well with an ordinary 1.5 volt torch cell for the filament supply. In the 1.4 volt series the 1H5-GT can be used. Simply ignore the diode connection.

Our correspondent's circuit shows the R.F. choke as an optional component but we suggest that it is a good idea to include it, otherwise the setting of the reaction control is likely to be unstable. By the way, we suggest that the switch be placed in the positive filament lead rather than the common negative lead.

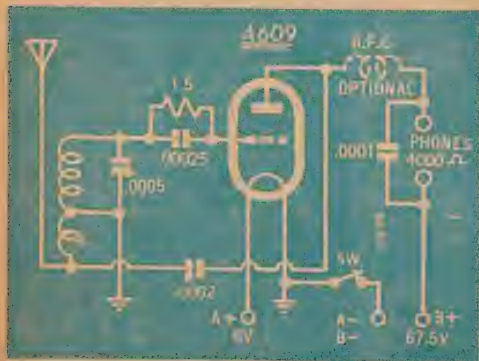Should the high-tension accidentally be shorted to earth with the present connection, the filament of the valve will be damaged.



The coil consists of 110 turns of 30 gauge wire in the case of the grid winding and 30 turns of 36 gauge in the case of the reaction winding. The windings are side by side on a $1\frac{1}{2}$ " former.



Periscopic Prisms

A perfectly ground prism originally used in tanks for periscopic sighting. Two of these prisms will give full periscopic effect; one prism will give upward sighting. Original cost to Army, £6/15/-.
Special Price, each .. **10/6**
Post N.S.W., 1/- per prism.
Interstate, 1/6 per prism.

RANGE FINDERS


Horizon and Bubble type. A beautiful precision-made instrument with valuable lenses and revolving calibrated disc. Can be used for measuring depression as well as elevation in feet. Original cost to R.A.A.F. £35.
Our Price, **£10/10/-**
Each ..
Post Free

CALICO

Super quality calico by the ROLL! This is the best quality we have handled for some time. In 30yd. Rolls, 36in wide.
PER ROLL .. **64/8**
Post Free.

Or in 5yd. lengths .. **10/9**
Post 1/3 extra.

P.M.G. ADJUSTABLE MORSE KEYS

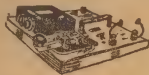

Genuine P.M.G. Morse Keys, with adjustable buzzer, brand spanking new. Cost the Army £4/10/-.
OUR PRICE .. **10/- ea.**
Without batteries, which are easily obtained at any electrical store.
Postage: N.S.W., 1/6; Interstate, 2/6.

Only 10/- ea.

BLUE DRILL WORK SHIRTS

All sizes, a good, strong wearing shirt.
Each .. **14/11**
Post: N.S.W., 7d; Interstate, 1/3.

Bearing & Distance Plotter

For measurement of bearings and distances. It is provided with a protractor and scales. Made of celluloid.
Price, each .. **3/-**
Post 6d.

COURSE & WIND CALCULATOR

A super precision made instrument. All aluminium. Original cost to R.A.A.F. £24.
Our Price, Complete with well-made wooden case, 12" x 12" x 4". **£3/10/-**
Only, each ..
Post: N.S.W., 1/-; Interstate, 1/6.
LUMINOUS DIALS.

AIRCRAFT FUEL GAUGES

190 Gal. Capacity. Cost R.A.A.F. £25.
Our Price, each .. **10/-**
Post, 1/6 extra

Imported Prismatic Binoculars

We have a grand assortment of Binoculars, including some of the best German, English and French makes.

LARGE RANGE AVAILABLE

6 x 24 ..	£10 10 0	Wide Angle	£12 10 0
6 x 30 ..	12 10 0	Wide Angle	14 10 0
8 x 24 ..	13 10 0	Wide Angle	15 10 0
8 x 30 ..	15 10 0	Wide Angle	17 10 0
Wide Angle 7 x 50 ..	£25 0 0		

Well packed. Post, Ins. Free.

GROUND SHEETS

Brand New Ground Sheets, 74 x 38.
£1 value.
Special Price, each .. **13/6**
Post: N.S.W., 1/-; Interstate, 1/6.

FEATHER SLEEPING BAGS

Warm and cosy lightweight bags, weight only 3lb., roll up into small carrying bag.
Each .. **78/6**
Post: N.S.W., 1/9; Interstate, 2/6.

Khaki Drill Jackets

Coat Style, ex-R.A.A.F. In sizes SM and M.
Only, each .. **9/6**
Post: N.S.W., 1/-; Interstate, 1/6.

Gas Bottles

As used to inflate rubber dinghies. Will hold many pounds of pressure. Approx. 12 inches long, 3 inches in diam. weight 3 1/2lb. Sturdily constructed with screw top release valve.
Only .. **10/- ea.**
Post: N.S.W., 1/6; Interstate, 2/6.

OIL PAINT

A genuine Oil Base Paint, extra good quality. Gray, Red, Cream, White, Chocolate, Light Stone, Dark Stone, Mid Stone, Green.

4 Gallon Drum, .. **£5/10/-**
Please add 1/6 per drum cartage to rail. Freight payable at your nearest attended railway station.

SPEED INDICATORS

Perfect Condition made by Elliot Bros. of London. In three ranges:—100 to 500 revs, 400 to 2000 revs, and 800 to 4000 revs.

£5/15/- ea.
Post 2/6 extra.

TRAVELLING RUGS

Pure Wool, soft and woolly, in pleasingly colored overchecked designs, 3/5lb.

in weight. Brand NEW .. **46/6**
Post: N.S.W., 1/3; Interstate, 2/-.

SUPER QUALITY ELASTIC CORD

in 40ft. Lengths.
3/16in in diameter.
This cord is comprised of 14 strands of best quality elastic and covered with cotton. Price, per 40ft. length .. **6/6**

COURSE & SPEED CALCULATORS

A beautiful precision made calculator with Port Drift and Starboard Drift Indicator, may be used for many types of calculating. Complete with neat dovetailed wooden case, 11" x 6" x 2 1/4"; fitted with brass hinges and catches and leather handle. Cost Air Force £12/10/- each.
Our Price, Each .. **15/-**
Post: N.S.W., 1/3; Interstate, 2/-.

COMPUTORS

Height and Airspeed Computers, aluminium calibrated disc types. Original cost £7/15/- each.
Each .. **7/6**
Post: N.S.W., 1/-; Interstate, 1/6.


American Directional Gyro Indicators

Brand New. Contain a specially precision-made Gyro.
ONLY, each .. **15/-**
Post: N.S.W., 1/3; Interstate, 2/-.

Aircraft

Luminous Compasses

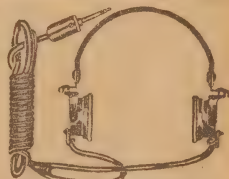Brand New. Liquid filled, 3 1/2" diameter x 3" deep. Ideal for ships, small-craft, etc. Original cost £19.
Our Price, Each .. **£3/15/-**
Post: N.S.W., 2/-; Interstate, 3/-.



HEAD PHONES

Brand new S.T.C., complete with cord and plug.
2000 ohms Impedance .. **£1/4/6**
Suitable for crystal sets. Postage 1/6 extra.

REFLECTOR GUNSIGHTS



Ex-Air Force. Containing best quality condenser lenses and adjustable reflector. Parts can be used for many purposes.

£2/5/- ea.
Postage 2/6 extra.

COMPONENTS
INCLUDE THESE
VALUABLE LENSES.



1 No. 1 Diam. 3 3/4" Foc. Len. 10in. No. 2 Diam. 3 3/4" Hollow Ground No. 3 Diam. 3 1/2" Foc. Len. 4 1/2in. plus No. 4 Diam. 2 1/2" Foc. Len. 6 1/2in. plus No. 5 Diam. 1 1/2" No. 6 Diam. 1-18 Amber Coloured ordinary.

Sorry, No C.O.D. SPECIAL ATTENTION PAID TO MAIL ORDERS AND WE GUARANTEE PROMPT DELIVERY.

DEITCH BROS.

DEPT. R., 70 OXFORD STREET, SYDNEY.

MANUFACTURERS OF
COMMERCIAL RECEIVERS
FOR 12 YEARS


CLASSIC

8 Valve World Range Chassis

WITH MATCHED DUAL SPEAKERS

£27'10/-

FREIGHT
EXTRA

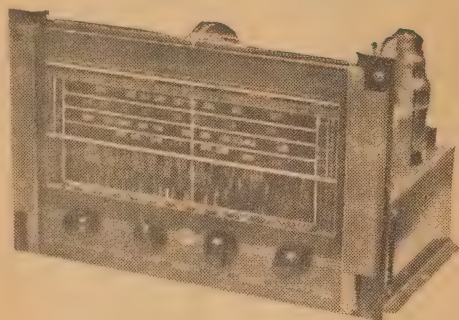

COMPARE THESE FEATURES

Eight valve world range chassis with push-pull output. Uses new Philips ECH33 converter valve for better long distance reception. High gain audio with inverse feed back and tone control gives you the best reproduction from your favorite recordings. Radiogram switch combined with short-wave switch. A.C. switch incorporated with tone control. Large calibrated edge lit dial with main stations in each State in prominent type, with counterweight drive. Provision for F.M. or television tuner. Permatuned iron cored coils and intermediates.


RECORD-CHANGERS AND PLAYERS

Collaro type 500 changers on A.C.504 players with crystal pick-up. Available for above chassis.

CLASSIC RADIO

FOR
QUALITY
WITH
ECONOMY

WITH 12" SPEAKER

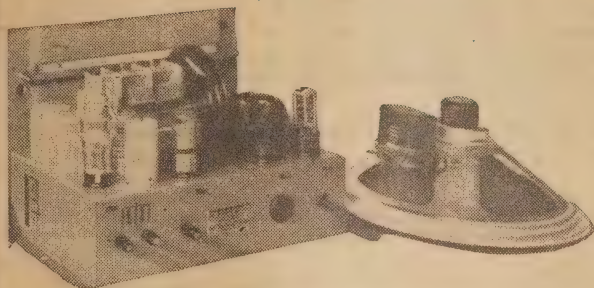


£21

FREIGHT EXTRA

Specifications are the same as 8 valve chassis, but with single 6V6 output valve and single 12" speaker.

LARGE VARIETIES OF
COMBINATION AND
CONSOLE CABINETS
AVAILABLE FROM £11/10/-

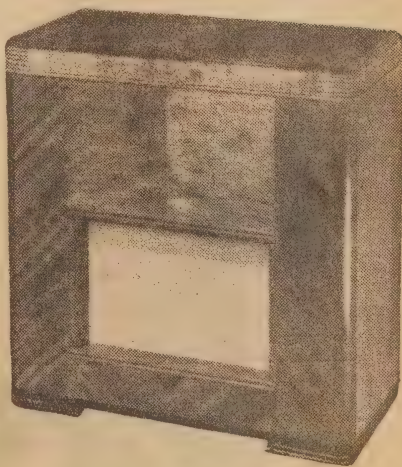Model illustrated is in piano finish, with beautiful maple veneer and removable Dial and Motor Panels. (Motor compartment recessed to take any STANDARD RECORD CHANGER.) £22/10/-.



245 PARRAMATTA RD., HABERFIELD
PHONE UA2145

Build your **R & H** ^{No. 4} ^{No. 5} Kits with **R.C.S.** components

for greater range, higher all-round performance and greater tonal fidelity

As you have or will read elsewhere in this issue R. & H. Kit No. 4 is a 5-valve dual waver, whilst Kit No. 5 is a universal battery charger. The use of genuine proven R.C.S. components will ensure that you get the results from these kits that the Technical Editor of Radio and Hobbies expects. R.C.S. components have been proved for over 25 years; today, they give you all the benefits that the latest overseas developments in electronics can offer.


SEE YOUR LOCAL RETAILER, OR WRITE TO R.C.S. FOR FULL LIST OF R.C.S. COMPONENTS WITH PRICES TO BUILD R. & H. NO. 4 AND 5 KITS

If for some reason, your local retailer is unable to supply R.C.S. components, write to R.C.S. for full details of R.C.S. components with which to build these kits, also for your copy of the very complete and comprehensive price list. We will also advise you of the name of your nearest retailer with full stocks of R.C.S. components to build these kits.

OTHER R.C.S. COMPONENTS INCLUDE—



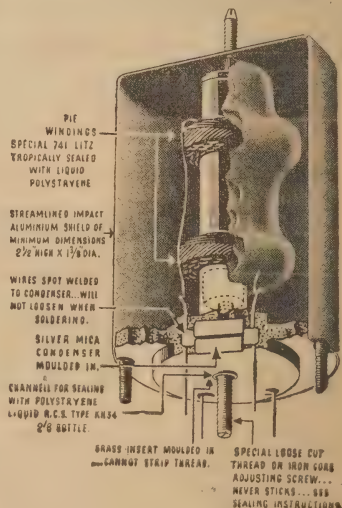
Cross section of R.C.S. intermediate transformer



R.C.S.
RADIO PTY. LTD.

174 Canterbury Road,
Canterbury, N.S.W.

AN AERIAL RADAR LABORATORY

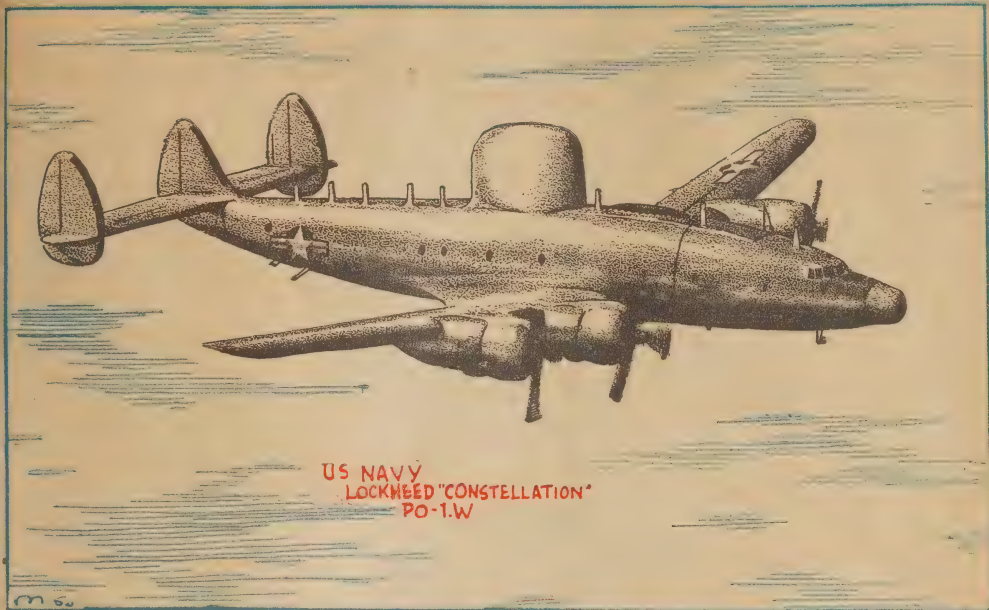

Familiar on many of the world's main skyways as a luxury airliner, the Lockheed Constellation has now made its appearance as a long-range radar patrol plane that will extend the range of "vision" of the Fleet. Early this year the US Navy disclosed the existence of this "flying laboratory." It was revealed that the modified Constellation, given the official designation PO-1W, would carry and test airborne early-warning equipment designed for faster detection and location of hostile air and surface forces.

PHOTOGRAPHS of the PO-1W released officially show two large "radomes," one on the top of and the other below the fuselage. These undoubtedly house scanning antennae. There are rows of antennae on both upper and lower exterior surfaces, while an elongated nose structure is a noticeable alteration to the familiar Constellation outline.

Basically, the Constellation is a low-wing monoplane with a sleek, finely-streamlined fuselage that gives a curious dolphin-like outline. A distinctive feature is the triple-finned tailplane of unusually great width. The four motors each develop more than 2000 horsepower.

The PO-1W, specially modified by the Lockheed Aircraft Corporation of Burbank, California, underwent a long series of tests by the factory before being handed over to the US Navy for tests of its early-warning radar devices and procedures.

Reports at the time of the completion of the factory tests emphasised the value that was being placed on the use of such an early-warning

radar plane, able to patrol well in advance of the fixed ground installations and relaying information on impending attacks well ahead of the surface radar system.

Radar cannot "see" beyond the optical horizon since the high frequencies that are employed do not bend around the earth's surface. The only way to extend the range of radar, is to take it aloft so that its horizon is greatly extended.

RANGE LIMITS

Shipboard and surface radar can "see" only to the optical horizon and enemy aircraft may, therefore, get in "underneath" its searching electronic fingers and may be undetected until they are well in towards the ground defences.

Airborne early-warning equipment located in a high flying aircraft patrolling many miles in front of a threatened point can see further down the horizon. Approaching aircraft or ships can thus be picked up much earlier than would otherwise be possible.

When a hostile aircraft is spotted by airborne radar, word can be radioed back to the ground station, alerting it for action and giving the location and direction of the impending attack.

The PQ-1W shares with its "parent" Constellation the ability to stay aloft for many hours and to cover great distances.

Its flying crew of pilot, co-pilot, flight engineer, radio operator, technicians, and radar operators, have bunks available for relief of crew members on long patrols.

Flight tests are reported to have disclosed that the bulky radomes and other external devices do not materially affect the performance of the aircraft.

With its great range—over 5000 miles non-stop—the PO-1W can remain aloft for periods on patrol missions from shore stations.

Top speed is 350 miles an hour, providing operational flexibility, since the aircraft can reach its patrol station quickly or be diverted to some new danger spot.

HOW TO MAKE A DRILLING STAND

Many times the home constructor needs more than two hands to negotiate a ticklish drilling job. A drilling stand is the obvious answer. This article tells you how to make such a stand from easily obtained materials.

THIS drilling stand is intended for use with one of the well-known type of breast drills having a length of plain spindle at the end remote from the drill chuck.

The base for the stand is composed of a piece of hard wood, 12in x 7½in x 1½in thick, care being taken to ensure that it is flat. The column


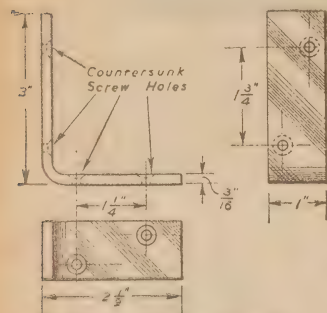


Fig. 2.—Details of angle brackets.

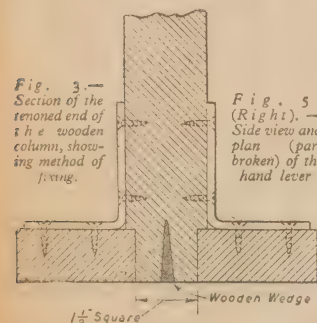

is preferably of the same material, being 2in square section and 20in long. The column is tenoned into the base as shown in Fig. 3, ensuring that the column is square both ways with the base.

GUIDE BRACKET

The two angle brackets (Fig. 2) can be secured to the base and column by means of wood screws (Fig. 3); these will give added strength and, provided that the brackets have been squared up accurately, they will ensure that the column remains square to the base. A piece of 3/16in M.S. plate is screwed on to the wooden base to form the drilling table, as indicated in Fig. 1.

This is made by bending a piece

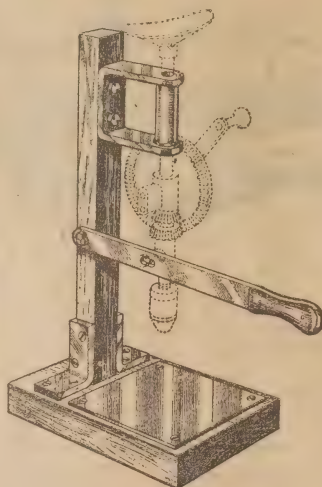


Fig. 1.—The completed drilling stand.

of M.S. to the shape and dimensions shown in Fig. 4, the two guide holes being drilled after bending. While drilling, the bracket should be packed with a piece of wood to avoid spring-

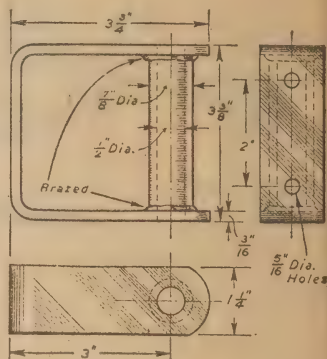



Fig. 4.—Three views of the guide bracket.

removed and the bore reamed out with a ½in reamer so as to form a good fit on the breast drill spindle.

The complete bracket can be bolted to the column of the stand by means of two 5/16in bolts.

HAND LEVER

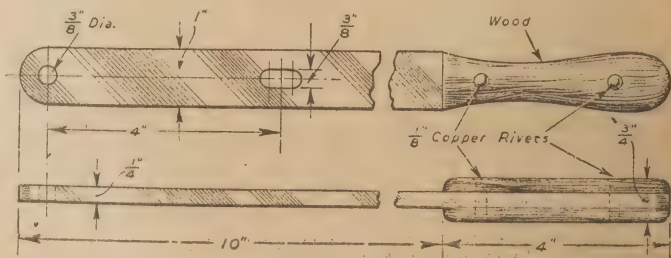This is made of M.S. and constructed as shown in Fig. 5. The elongated hole is filed to suit on



ing; the two holes are drilled slightly under ½in.

The guide tube is composed of brass and can either be turned or a piece of brass tube used, but in either case the bore must be slightly under ½in. The ends of the tube are faced or filed until they are a good fit inside the bracket. A ½in bolt is then passed through both the bracket and tube and tightened. Due to the small bore, the bolt may have to be filed down slightly to suit.

The tube can now be brazed to the bracket as indicated in drawing. After brazing, the bolt can be

assembly, so as to allow for the angularity of the hand lever when operated to give the necessary movement up or down.

ASSEMBLY

Care must be taken on assembly to leave enough room between the chuck and table to allow for the largest drill used and also a medium-sized job.

When drilling with short drills, the job will have to be packed up to the required height by means of wooden blocks.

RADIO CONTROL FOR MODEL AIRCRAFT

The final instalment of a series of articles on the radio control of model aircraft. The same type of equipment can be used to control other models. Details of the author's latest apparatus are given here.

By GIL MILES

SIMPLE receiver designed around the now available Hivac sub-miniature gas triode, the XFG-1, shown in fig. 32 with a typical circuit in fig. 30.

The manufacturers of this valve state: "The useful life of the XFG-1 is critically dependent upon the peak anode current, which is determined by the precise circuit condition and is not readily measurable. The mean anode current can, however, be measured and should, if possible, be adjusted to 1.5 mA or less in order to prolong the valve life as much as possible."

The variable resistor in the anode circuit and the antenna length are both used to adjust the anode current to the preferred value. Many variations of this circuit are possible and although differences were noted between individual valves, the two adjustments mentioned will take care of each case.

The standing current of 1.5 mA should drop to approximately 0.2 mA with a strong signal and to approximately 0.5 mA with a weak signal.

A companion transmitter to the XFG-1 receiver can be built around a 3A5 or its equivalent the Mullard CC90 valve. It will prove a stable oscillator providing precautions are taken to see that all leads are short and rigid, especially the tuning coil and its mounting.



Fig. 34 The author's 9ft wingspan model is shown here together with the control transmitter and aerial. The small switch box can be seen lying on top of the transmitter. Note the halo aerial which gives all round horizontal polarisation.

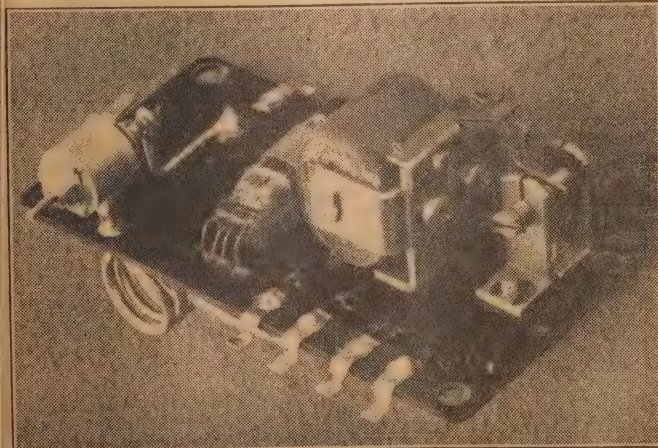


Fig. 32 Photograph of the latest receiver used by the author, the circuit of which is shown at Fig. 30. The coil is seen under the panel with the tuning condenser above. Then comes the thyatron and the relay operated escapement.


These valves are operating within their rating with 2 watts input and when coupled to an antenna cut to the dimensions as shown in figure 31, will give plenty of output even at 40mc/s.

Keeping the antenna height between $\frac{1}{4}$ and $\frac{1}{2}$ wavelength above ground is good practice, and if necessary in the interests of portability the outer $\frac{1}{4}$ wavelength section of the top could be folded at right angles to the main length, in fact some improvement in the shape of the horizontal all round radiation pattern of a simple dipole can be gained by simply folding the antenna in the shape of a sine wave i.e. when looking down on it from on top.

Fixed to the tail unit and shown in figure 35, can be seen the rotating vane, which can be stopped in either of two positions to give rudder left or rudder right movements to the model.

So that tests can be carried out in the field and adjustments made with ease, it is suggested that the

AMATEURS—DISPOSALS—EXPERIMENTERS

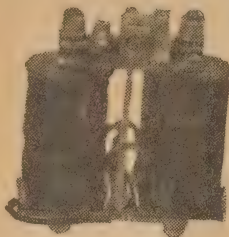

RELAYS

Twin Coil type can be adjusted to work on as low as 1 m.a.; extra coil is for use in locking if required.

4/6 post free.

Twin Coil American type, Multiple Switching Contacts.

7/6 post free.



MIDGET GENEMOTORS

Input—28 Volts at 1.1 Amps.
Output—250 Volts at .06 Amps.
Size—4 1/2 x 2 1/2. Weighs only 3 1-8lbs.
Perfect for use with 32 Volt domestic Receivers.

32/6


Postage and Packing, 3/-.



VIBRATOR POWER UNIT

6 Volts input, tapped Voltages to 220 volts, including Bias Voltages. Used with 101 type Transceivers. Fully tested before despatch.


£3/0/0 F.O.R.

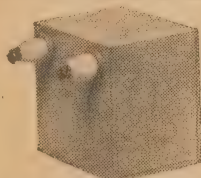

H.V. TRANSFORMERS

80 to 3200 volts, 500 cycle type. Excellent as a spark coil for electric fences.

10/- F.O.R.

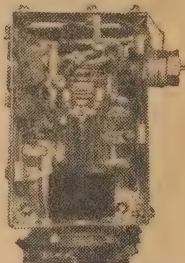


H.F. OSCILLATORS

Complete with 7193 valve, ready to use. Tuned by a split stator condenser worth this amount alone. An excellent driver for your 144 m/c. Transmitter. Alternatively, modulate the unit as it stands.

15/-

POST FREE.

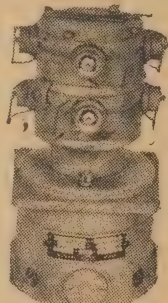

MOTORS

24 Volt Low H.P. Motors, complete with Coaxial switching Unit. While they last.

35/- post free.

MISCELLANEOUS VALVES

EF50 Valve and Ceramic Socket.

15/- post free.

EA50 Valve and Socket (Miniature Diode).

7/6 post free.

AV11 H/W High Voltage Rectifier.

15/- post free.

7193 High Frequency Triode to 300m/c.

7/6 post free.

6H6 Twin Diode (Metal)

7/6 post free.

CONDENSERS

Oil filled, .01 5000 VW. 5/-

Oil filled, .02, 10,000 VW. 6/6

Oil filled, 2 mfd. 600 VW. 4/6

Mica (Porcelain Case), .001, 5000

VW. 7/6

Postage 1/6 extra.

MICROPHONES

No. 3 Hand as used with No. 11, 101, 109, etc.


12/6 post free.

Respirator, Carbon type.

5/- post free.

Double Button Carbon.

6/- post free

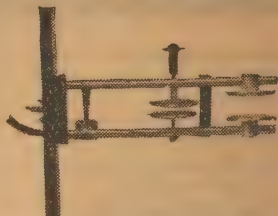

LECHER BARS

Silver plated, complete with sliding aerial taps and tuning discs, suitable for 144 m/c.

7/6


POSTAGE 2/- EXTRA.



GENEMOTORS

Ideal for use with Home Built Car Radios. Complete with High and Low Tension Filter, input 12 volt, output 220 volt at 60 ma.

30/- F.O.R.

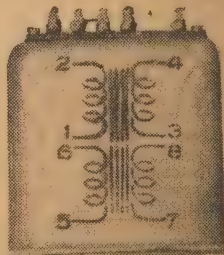


LINE TRANSFORMERS

Four 600 ohm windings, excellent for use with Public Address and other types of Amplifiers.

12/6

Postage and Packing, 2/-.

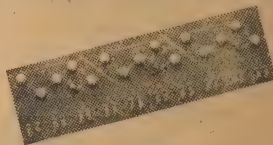

TERMINAL BOARDS

With 15 plated terminals, also 23 pair of plated bridge type terminals with plug-in shorting bars.

7/6

POSTAGE 2/6 EXTRA.

Address all mail to—

Box 14, P.O., Haberfield,
N.S.W.

PARAGON RADIO

Available also at—

No. 5 Royal Arcade,
Sydney.

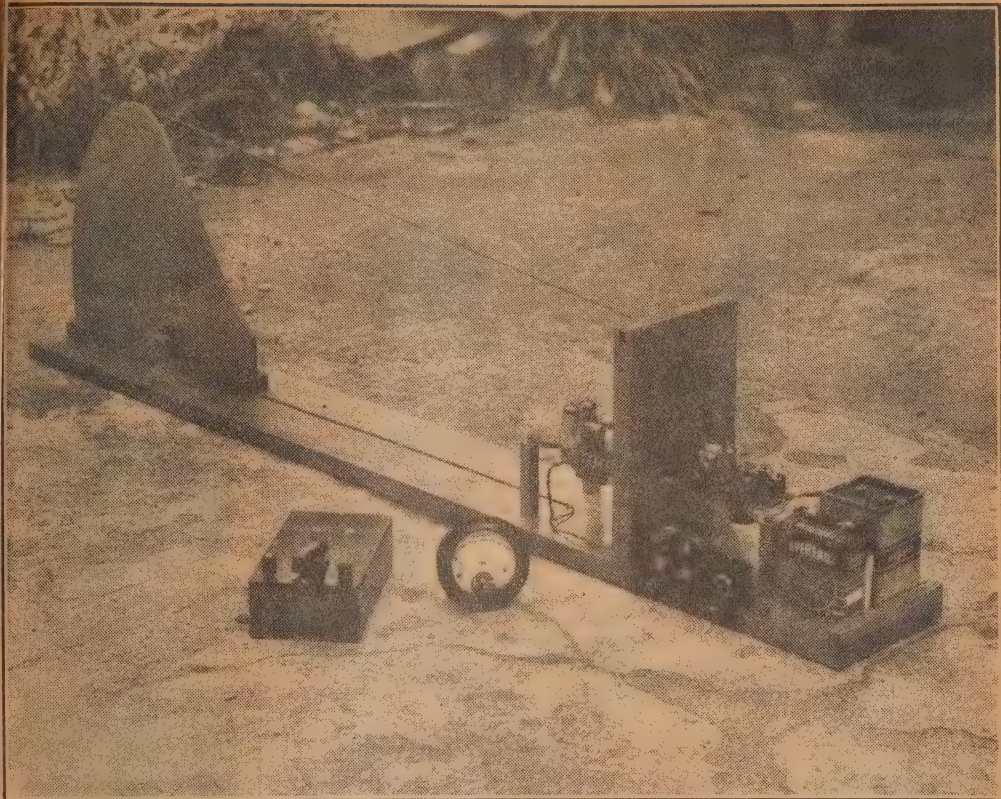


Fig. 33 Above is a complete receiving gear set up for field testing. Small dial lamps glow to simulate rudder movement. The meter plugs either into the box to operate as a voltmeter, or in to the test panel to check the equipment.

complete receiving system be set up on a board similar to that shown in fig. 33. The simple receiver and escapement would not require so elaborate a setup as that shown, but it is still desirable to mount the components and wiring in similar positions to their final place in the model.

It might not at first be apparent, but the leads to the escapement are part of the antenna system, and for that reason alone, it is worth while setting everything up as described.

When working properly, it is an easy matter then to transfer everything into the model with a reasonable chance of success and, believe me, here is one instance where a haywire installation will be a handicap!

The author's 9' span model, crystal-controlled transmitter and antenna are seen in fig. 34. The model made in Melbourne by Mr. Des Belot, of the West Preston Model Aeroplane Club, has already had two years of free flight to its credit.

The transmitter provides a carrier for engine control and two audio tones as modulation for left and right, each function obtainable instantly and at will without the necessity of going through a sequence.

A control box small enough to be held in the hand can be seen on top of the transmitter in figure 34.

Fitted with a push button switch for carrier cut off and a telephone type key switch for rudder left, right and neutral.

The engine ignition circuit is arranged so that the engine will only

run while the carrier is "on," a momentary break of the carrier stops it, thus providing a safety feature should a radio fault develop or the model fly out of radio range.

The two radio units are shock


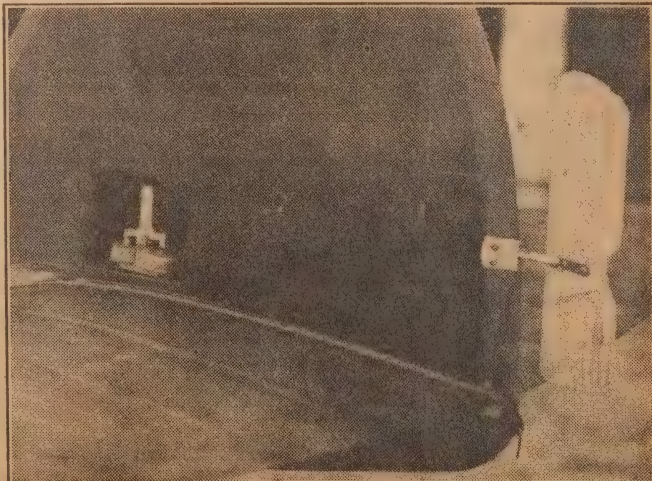


Fig. 35 Here is the control vane mounted on the tail unit of the model with the operating relay inside the stabilizer section.

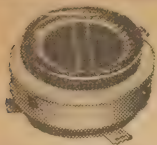


COMPASS, TYPE P.8
5 1/2 in. dia. x 2 1/2 in. deep accurate
Aircraft type navigation compass.
Reconditioned **37/6**
as new
Vic. 2/-; N.S.W., S.A., Tas., 3/6;
Qld., W.A., N.T., 5/-.



R.A.A.F. ASTRONOMICAL INSTRUMENT can be utilised to measure horizontal and vertical angles such as those encountered in road making and irrigation work. It is fitted with scales calibrated in degrees, two levels and adjustable mountings. **£2/15/-**

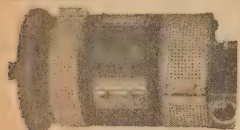Postage and Packing: Vic., 2/-; N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.



BATTERY CHARGING GENERATORS

All generators checked and tested before despatch.


	£ s. d.
24 Volt, 1500 Watt ..	12 10 0
12 Volt, 750 Watt ..	12 10 0
12 Volt, 500 Watt ..	10 10 0

The 24-volt 1500-watt Generator can be used for 32-volt system without any alteration.



24 Volt Regulator and Cutout

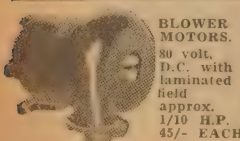Made by Bendix Aviation Corporation. Suitable for use with above generators in home lighting plants. **£3/10/-**



BLOWER MOTORS.
80 volt.
D.C. with laminated field.
approx.
1/10 H.P.
45/- EACH

Please add similar postage on Electric Motor.

Waltham

TRADING CO.


393 Flinders St., Melbourne, C.1.
Mail Order Dept., 319 Swanston St., Melbourne.



HYDRO-METER

For Temperature and Humidity readings, as supplied to the Air Force. No Home, Farm, Factory or Dairy should be without one of these. **Price .. 19/6**

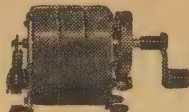
Postage and Packing: Vic., 1/6; N.S.W., S.A., Tas., 2/-; W.A., Qld., N.T., 2/6.



BELL-RINGING HAND GENERATORS

Suitable for installing in the Don V Telephone, to convert to Bell Call System **37/6**

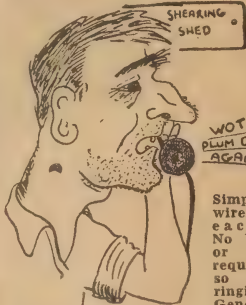Postage and Packing: Vic., 1/6; N.S.W., S.A., Tas., 2/3; Qld., W.A., N.T., 3/-.



Incorporated and each Telephone is contained in a light, strong, compact steel waterproof case.

High class equipment that has been tried, tested and proved by the British Army in the field. Effective range, 3 to 4 miles. Complete Set, comprising 2 Telephones and 100 yd. Reel of Twin Wire, **£8/12/6**

Additional Telephones, £3/17/6 each.
Extra Reels of Twin Wire, 17/6 per 100 yds.

And you will hear it for the first time if you install an English "H" Type Portable Telephone

Quick communication is an essential timesaver and these Telephones have proved invaluable to Farmers and Homesteaders.

Simple to install by connecting two wires from each unit. No batteries or power required. Also a Bell-ringing hand Generator is

COOK HOUSE.
Farm 20

YOU HEARD
ME THE
FIRST TIME



TANK WHIP AERIALS

Two four foot sections, ideal for car aerials, or fishing rods. Each **15/-**

MINE DETECTORS

The war-time mine detector is now doing a very useful peace-time job and has proved invaluable to PLUMBERS, GAS-FITTERS and MUNICIPAL COUNCILS. It originally worked on the principle of finding the metal casings of mines. It would just as easily—in fact, frequently did—and the coins in the pockets of the user. When it found them it whistled.

Metal pipes and cables can be traced under the ground. This saves the laborious, costly and time-wasting digging of "search holes" when the underground path of the pipes is uncertain, as it frequently is. And throughout all the metal detector "whistles while it works."

The unit consists of two interchangeable sweep coils, one large and one small, and is complete with carrying pack, valves and headphones, packed in strong wooden transit cases, 10 in x 12 in x 4 ft 6 in (total weight 80 lbs.). **PRICE £8/10/- EACH, F.O.R.**

AIRCRAFT GILL MOTORS

These contain a 24-volt motor, approx. 1/10th H.P. that can be revolved in either direction, A.C. or D.C. A magnetic brake and a 5000 to 1 reduction gearbox. **£2/17/6**


R.A.A.F. NAVIGATORS' PLOTTING BOARDS, 18 ins. x 18 ins. BRAND NEW. COMPLETE WITH PLOTTING ARM. **25/-**

ALL GOODS CONSIGNED Freight on Delivery unless otherwise stated. Sorry! No C.O.D.



COMPASS

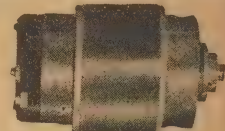Liquid Damped, Card Type, 6 1/2" dia. x 3 1/2" deep, fitted with large viewing prism, ideal for small craft, etc., for normal navigation and also taking bearings. Each **£6/10/-**



SELSYN MOTORS

50 volt 50 cycle, ideal for use with Rotating beam aeriels. **30/-**
Postage and Packing: Vic., 2/-; N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.



WESTERN ELECTRIC U.H.F. FOUR VALVE MIDGET RECEIVER

Frequency 233 to 253 Mega-cycles Valves 3-945, 1-955 Super Regenerative Receiver. Brand **£2/19/6**
New. Postage and Packing: Vic., 2/-; N.S.W., S.A., Tas., 3/6; Qld., W.A., N.T., 5/-.



AIRCRAFT BOMB AIMING SIGHTS BARR & STROUD MK IX.

A. Containing liquid damped compass, 5 in. dia. x 2 in. deep, with corrector box, many useful gears and also a rack and pinion. Two spirit levels, etc., in strong wooden carrying box, 12 in x 2 1/2 in. x 8 1/2 in., which has two mortice type catches and metal handle. **£2/10/-**


ELECTRIC MOTORS

24 volt D/C - A/C. 1/40th H.P. with Laminated field. Brand **£2/10/-**
New. Postage and Packing: Vic., 2/6; N.S.W., S.A., Tas., 2/6; Qld., W.A., N.T., 3/6.


The "Halo" antenna was chosen because it is easy to transport and its radiation is horizontal, being practically equal in all directions. If the transmitter to be used is



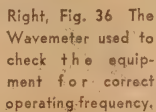not crystal-controlled, it is essential that some check be kept on the transmitted frequency. The simple wave meter of fig. 36 and fig. 37, when properly calibrated, will cover both allotted frequencies. It is sen-




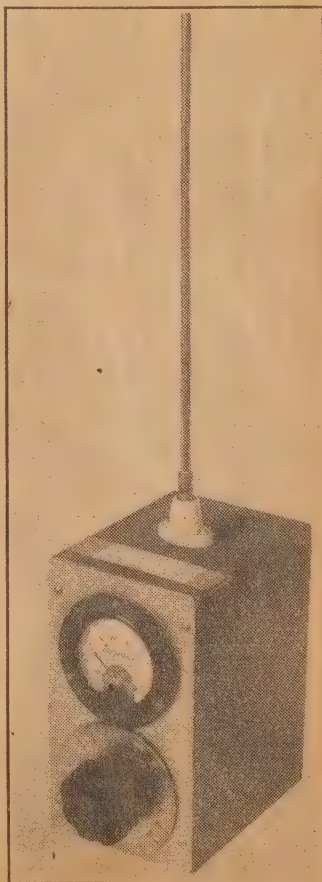Left, Fig. 37 The circuit of the wave-meter shown in Fig. 36.



24-volt A.C.-D.C. Geared Electric Motor

100
Revs.
per
minute.

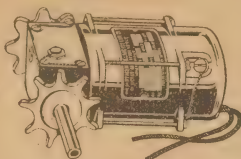

55/-. Cost £8/10/-.

THIS MONTH'S BARGAIN LIST

English Diagonal Cutting Pliers, 6/6
Extra Long Nose Radio Pliers. 8" long, pair 9/6
American Feeler Gauges . . . 3/6
Dental Inspection Mirrors . . . 5/6
Vacuum Gauges, 0.30in. 27/6
Pressure Gauges, 0-200lbs. . . 25/-
New Leather Flying Helmets 32/6
Army Paint, Brown or Buff. Gal. 29/6
Brand New Army Boots, Size 9 only. Pair 26/6
English Spiral Screwdrivers . 16/6
Rear Vision Mirrors. Chrome Car Tow Ropes, 13ft. long . . 9/6
Gasket or Workshop Snips . . 4/9
English Barbers' Scissors, Pr. 12/6
Brand New Micro Switches . 6/-
Hobbyists' Drills. Doz. . . . 6/-
Morse Keys and Buzzer. Ideal for Boy Scouts. Cost £5, for Genuine British 4-draw 22 magnification Rifle Range Telescope £6/19/6
Pocket Compasses, English . . 5/9
Pocket Telescopes 12/9
Pocket Folding Telescopes, optic glass lenses. Good range Workman's Tool Bags, made from solid leather and canvas. Ideal for plumbers or bricklayers. 18" x 8". Each . . . 12/6
Finest Quality Waterproof and Rotproof Tarpaulins. 9 x 9 £4/10/-
8 x 10, £4/15/-. 9 x 15, £7/15/-. 9 x 12, £5/19/6. 12 x 12, £7/15/-. 12 x 15, £9/5/-. 18 x 14, £13/10/-. 18 x 16, £14/15/-. 20 x 18, £19/19/-. 30 x 20, £33/10/-.
6 x 7 Genuine Japara Covers. Ideal motor cycle covers . . 37/6
Stainless Steel Pocket Knives, with 2 blades 8/6
American - style Expanding Wristlet Watch Bands, chrome plated 9/6
Gold Plated 16/6
Brand New English Pendulum Type Kitchen Clocks, Cream and Green 35/-

SURGEONS' SCALPES
SMALL 4/6
LARGE 5/6

Many other uses — Hobbyists, Chiropody, Photography, etc.

BRAND NEW WESTON DOUBLE READING MILLIAMPMETERS
0-40 0-120, 25/- each.



Flexible Silver Cine Screens. 6ft x 42" 12/6
Altimeter or Height Meter. Lots of interest. Fit one to your car 30/-
Brand new £3/10/-



A Lucky Repurchase.

£3/19/6

Brand New Army Phones

Ideal for Farms

Install one in your workshop or house. Equal to P.M.G.

Made in England Brand New 5-in-1 POCKET SCREWDRIVERS

Ideal for Engineers, Mechanics, Hobbyists.



5/9

Carry one in your pocket. 5 screwdrivers in one.

R.A.F. AIR PUMPS AS USED IN LINCOLN BOMBERS

Can be used as Low Pressure Compressors or for Low Pressure Spray Guns, Brazing,



Useful for Gas Torch

55/-


Glass Blowing or Tinning, etc.

PHOTOGRAPHIC BROMIDE PAPER—KODAK

Fraction of New Price

5½ x 5½	5/- per pkt, 144
8½ x 6½	12/6 " " "
9½ x 7½	17/6 " " "
10 x 10	22/6 " " "

REDUCED PRICE

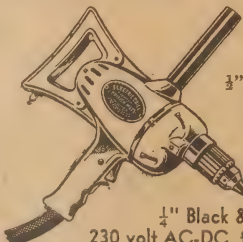

British Made "Wolf"
¾" AC-DC 230 volt Electric Drills, £15/3/9

Also

½" Black & Decker 230 volt AC-DC, £8/19/6

Never again at these prices. Brand new. Limited stocks available. Grinding and Buffing Sets to suit Black and Decker Drills . . . 25/-

Perspex Sheet takes the place of glass. Ideal for car windows, etc.

24 x 18 3/32"	£1/12/6
22 x 14 3/16"	£1/1/-
18 x 12 3/16"	17/6

SURPLUS


512 ELIZABETH ST., MELBOURNE, C.I.

PHONE: FJ5904. Just 4 doors from

BRAND NEW AMERICAN PUMPS

USED BY THE R.A.A.F.

STEINLESS STEEL VANES

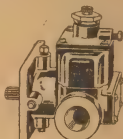

WILL PUMP ANY LIQUID

400 GALS. PER HOUR 55/-
200 GALS. PER HOUR 50/-

Brand New ENGLISH RECTIFIERS

Make yourself a battery charger.




6v. 2 amp . . 24/6
6v. 5 amp . . 32/6
6v. 10 amp . . 57/6
12v. 5 amp . . 57/6

Transformers to suit above Rectifiers, 2 and 5 amp 37/6

AT LAST

Complete Battery Charger

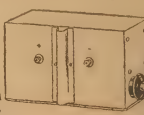Fitted with brand new English Selenium Rectifier



Works off 230v. A.C. Household Supply.

Charges any battery from 2 to 6 volts at 5 amps, £5/15/- complete.

BRAND NEW CAR FIRE EXTINGUISHER




Made in U.S.A. Fixed price £5/10/-
OUR PRICE £3/5/-

Genuine Pyrene. Fit one to your car.

Limited Quantity available.

BRAND NEW CARPENTER'S BRACES

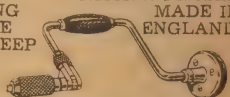COMPLETE WITH RATCHET BALL BEARING HANDLE MADE IN ENGLAND.



Wonderful Value. Worth 50/-.
OUR PRICE, 32/6. BE EARLY.

SURPLUS STORES

PLEASE ADD FREIGHT OR POSTAGE

Mail Orders Carefully Packed

STORES

512 ELIZABETH ST., MELBOURNE, C.I.
Victoria Street. PHONE: FJ5904

**RAAF AIRPLANE
COMPRESSOR**
Two Stage
Limited Numbers
Highest Quality
£5/5/-



DRILLING OR ENGRAVING



HANDPIECE
Brand New 20/- each
Burrs 2/6 packet of 5.

**AT LAST AT LAST
RAAF RUBBER DINGHIES**



**Ideal Rivers,
Lakes, Beach, etc.**
£5/5/- complete with hand
pump.

Invaluable for flooded areas.

**JUST ARRIVED
ARMY GROUND SHEET AND
CAPE**

Ideal for
campers,
cyclists,
hikers



16/6

Direct from
English Army
disposals



**Engineers' Special Outsize Screw
Calipers, 4" Dividers and inside
Screw Calipers, each 4/6**



**BRAND NEW
BRITISH
METRO-VICKERS**
0-1 Milliammeters
2 1/2" diameter, 32/6


JUST ARRIVED.
Brand New SNAP
SHOT CAMERAS, with
carrying strap. Special
Price 17/6
Cake Mixers, water
driven, works off any
water tap, as good as
electric. Cost 27/7/-.
Our Price 39/6
English 150 amp A.C.
D.C. meters, 3 1/2" dia.
Ideal for generators
57/6.

**IDEAL FOR
HOME LIGHT-
ING PLANTS**




**RAAF
BATTERY
CHARGING
GENERATORS**
24 volt 1500 watt £13/15/-
Brand New English Lucas, 12
volt 500 watt £10/15/-

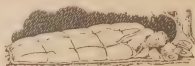Just what you have been waiting for
**GUARANTEED WATERPROOF
SLEEPING BAGS**
Why buy a tent for your holidays?
Ideal for campers. Carry one in
your car for emergency. . . £4/15/-



**AT LAST! British Army Issue
DOUBLE SCALE VOLTMETER
0-15 0-250 VOLTS**

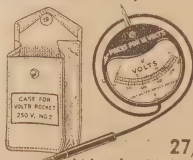**IDEAL
FOR
BATTERY
SET
USERS
AND
DEAF
AID
USERS
OR HOBBYISTS**



27/6
Worth £3/15/-


**Brand New
American
Vacuum
or Air Pump**

Builds up air
pressure to
30lbs. at 1000
R.P.M.
Develops up to
120lbs. per sq. in. of hydraulic
pressure, will pump 7 1/2 gals. S.A.E.
oil or other liquids per minute.
Useful for spraying, milking,
presses, oil burners, hydraulic
systems £3/15/-



**BRAND NEW ENGLISH VERNIER
CALIPERS**

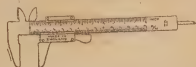Will measure inside and outside.
Can also be used as Depth Gauge.



22/6

Ideal for all types of engineering
work. Measures in ins. and m/m.
Can be carried in the pocket.

BRAND NEW AIR COMPRESSOR
2.2 cubic feet, will pump up to 75lb.

Never before
at this price.



£9/10

Ideal for spray-
ing.

**WATCHMAKERS AND
INSTRUMENT MAKERS**



English Tweezers 5/6
English Pin Vices 6/6
Single Drivers, 5 sizes, 2/6 to 3/6
Eyeglasses 6/6 & 8/6
Extra strong double lens eye-
glass 15/-

**AT LAST:
DALTON
COMPUTERS.
IDEAL FOR
AERO CLUBS
A.T.C., ETC.**



Only
Limited
Stocks
Available.
Be
Early.
35/-

**Brand New American Weston
Voltsmeters 0-50V, £2/2/-.**


0-50 volts, 0-100
amps, combined.
£3/10/-

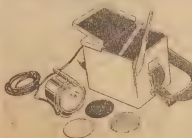0-10 Weston Amp-
meters 50/-



Also Metro-Vickers 0-15 volts,
0-600 volts, full scale, 0-500 Micro-
amps, Brand New 25/-
A.C.-D.C. 0-20 Milliammeters,
2 1/2 in. dial 23/6

**LUCKY PURCHASE BRAND NEW
ENGLISH ARMY SPOTLIGHTS**



Ideal for
Shooting,
Fishing, etc.
Fit One
To Your Car

29/6

Complete in Carrying Case with Red
Amber & Green Discs.

Telephone FJ5904


**INCLUDE STATE IN ADDRESS
and Efficiently Despatched**

Just arrived Brand
New R.A.F. Flying
Suits, guaranteed
waterproof, £5/19/6.
Genuine English
R.A.F. Flying
Coggles, MK.7,
37/6 pair.

RED  LINE

Matched Transformer Kits

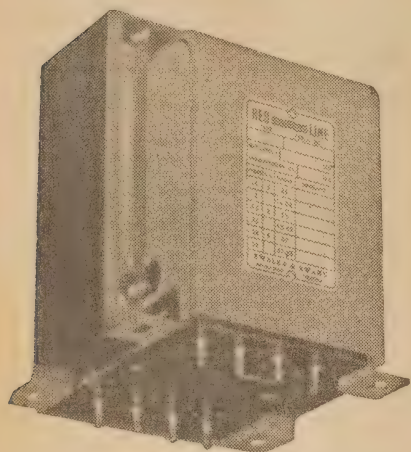for the Williamson Negative Feedback Amplifier



*As originally designed by
Mr. D. T. N. Williamson in "Wireless World,"
April and May, 1947.*

Output Transformer

Primary Impedance 10,000 Ohms 807 (T) P.P.
Secondary Impedance as required—see panel.*

FREQUENCY RESPONSE: Linear within 0.2 db.
20 cps. to 30,000 cps.

PRIMARY INDUCTANCE (at 5v AC) not less than 100
Henries.

LEAKAGE INDUCTANCE (at 5v AC, 1000 cps.) 17
Millihenries.

INSERTION LOSS: 0.4 Decibels.

AF Series Output Transformers*

10,000 ohms p.p. plus 34 db primary.

500 & 125 ohms	secondary	AF 10
8 & 2 ohms	secondary	AF 8
12 & 3 ohms	secondary	AF 3
15 & 3½ ohms	secondary	AF 15

Condenser Input Power Supply

	Type No.	Price
Output Trans	AF*	127/9
1 P/Trans	20453	93/2
1 Choke	201515	36/2
1 Choke	50825	30/3

RED LINE EQUIPMENT PTY. LTD.

TRANSFORMER ENGINEERS

City Office:
157 Elizabeth St., Melbourne. MU6895

Workshop:
2 Coates Lane, Melb. Central 4773



Distributors:
S.A.—Gerard & Goodman Ltd.
N.S.W.—United Radio Distributors Pty. Ltd.
Q'ld.—A. E. Harold, B. Martin Pty, Ltd,
Vic.—All Leading Wholesalers.

A GUARANTEE OF DEPENDABILITY

tive enough to be used as a field strength meter when transmitting and to pre-tune the receiver. Just to show that someone has really tried to simplify this radio control business, figure 38, depicts a receiver using a germanium crystal, a relay and not much else. However, it took 100 watts of transmitter power to operate the relay at $\frac{1}{2}$ mile!

The boys who fly indoor model aeroplanes get the weight of their models down to fractions of an ounce and even here successful radio control has been applied.

Using a 100 watt transmitter again; this time a receiver containing a bi-metal strip was apparently made to operate a rudder with power from the transmitter, only over a matter of a few feet of course; but very interesting nevertheless.


Before any control of model aircraft, or, for that matter, of any other type of model, can be undertaken, special permission must be obtained from the PMG Department through the Wireless Branch in any particular State. Two frequency bands have been set aside for model control and are subject to the following conditions:—

The input power to the plate circuit of the transmitter valve feeding the aerial must not exceed 2 watts.

The frequency band will not be used for any service except model control. Transmissions shall not cause any interference with broadcast listeners, or with any other radio service.

Licensed amateur transmitters

Fig. 38 The circuit of a crystal receiver useful for extremely short distances.

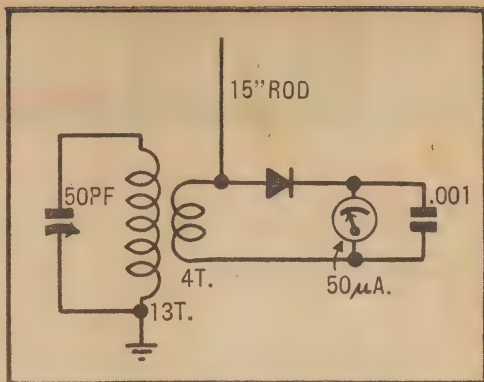

may operate radio controlled models on any of the amateur bands above and including the 144 mc. band, but can only use the two special control bands after obtaining permission to do so.

The frequency bands for which permits will be considered are 26.957—27.282 mc. and 40.66 and 40.7 mc. The transmissions must lie wholly within these limits.

The PMG will require full details of the experiments to be carried

out, together with a description and circuit diagrams of the equipment, both receivers and transmitters, it is proposed to use. The locality of the experiments must also be stated.

Permits if granted are valid for six months from the date of issue. Applicants between the ages of 16-21 years must supply written statement from their parents accepting responsibility for any breaches of regulations which might occur during operation.

RADIO IN THE AFRICAN JUNGLE

(Continued from Page 21)

realignments and these are being corrected as production continues. The result should be a very simple but effective battery set, ideal for use by the native population. In fact, many of the sets are being sold as portables and "second sets" to the white population and this fact lends them immediate prestige.

The Government is concentrating on a publicity campaign through the Press and mobile cinemas and is also preparing to sponsor a listeners club, complete with membership badges and listeners' magazine. Additional markets are being opened up in Southern Rhodesia, Nyasaland and other neighboring provinces.

TYPICAL LETTERS

Letters from the native population, though phrased in primitive fashion, speak eloquently of the impact of the Saucepan Special and the programme which it makes available. Typical letters read:—

"I have the honor to write this letter in order to thank you for your kindnesses which the Government of N. Rhodesia has done to we Africans the greatest gift to let we Africans buy the wirles. Indeed we are very much pleased to hear things which was done in every part of N.R. and all over the countries, it is the first gift which we received we Africans of Northern Rhodesia to have the wirles to understand all the words which comes to every contries that is why I write this letter to give my

thanks is I have got a wirles in my house.

Stephen Moffat Chepela.

"I did not know that from Lusaka there can come words as if the one speaking is just with me in my house and when they are singing as if they were with me in my house. My wife an I are praising the Governor for having sent the District Commissioner walking for 8 miles to come and bring me a wireless set."

Chief Chief Chimbombo.

"Oh how very happy we are, I and my wife Lucy. How very pleased we are when our wireless starts to speak at 5 o'clock.

Diamon Simukwai.

"If you have bad thoughts in you or are fond of fighting others when you get your own set and listen in you can forget and stop all your bad ways. . . . Nowadays I will be enjoying a lot if I don't die quickly. . . . I wish to tell you that I do enjoy very much listening to my set, although I don't get satisfied as I do when eating 'Nsima' (porridge). If you spend your £6/5/0 in buying a cheap wireless set then you know that it will always keep you happy."

I. Webster Kmombo.

"At 444 miles away on the Great North Road always people come around me to listen in and are very pleased. Number of them is about 25 to 40 people. So, sir, we are all


very happy indeed. I carry my set with me on the mail lorry."

E. M. Stephenson (Mail Driver).

"With much pleasure to inform you that I have already bought one of the wireless sets which of course make me to be pleased when it is in operation. I bought it as soon as it reached the Booth's store before the Christmas. . . . In addition to this many people are also interested to come and listen to my wireless. Schoolboys and girls are very much glad to hear from this machine. We therefore thank the Government of N. Rhodesia for introducing this wonderful machine for the use of the Africans in this Territory."

H. A. Chelu (Headmaster).

New Invention Crystal Detector

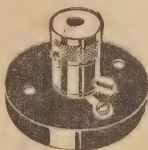

The "Red Spot" highly sensitive semi-fixed permanent crystal detector is now available from Tenatone Manufacturing Co., Pacific House, 296 Pitt Street, Sydney, for 9/6, 10/- posted. The "Red Spot" will take the place of the old type crystal and catwhisker and give much better and more constant results. When necessary, it is easily adjusted by means of the knurled cap as illustrated.

Pocket Book

The STORYTELLER MAGAZINE 6D

SHORT-WAVE NOTES BY RAY SIMPSON

RADIO SAIGON WITH A NEW NAME

For many years now listeners have been hearing the Indo-China station in Saigon which was formerly known as "Radio Saigon." In recent months its title has been changed to "Radio France Asie" and one of its frequencies changed from 11.78mc to 11.83mc and also 11.84mc.

QUITE some time ago now it was announced by the station that they would be carrying out tests on a new channel, 9.524mc. However, despite a careful watch, no sign of this new outlet was heard. It now transpires that they have actually begun to use the 31 metre band but not on 9.524mc, but instead, 9.495mc.

About three weeks ago the writer heard a very powerful French speaking station on this latter frequency which came on the air around 8.15 pm and after playing native type music until 8.30 pm, changed over to Western type music till leaving the air a few minutes before 9.0 pm. The only announcement heard was "Ici Radio France Libre" together with the frequency. However, according to Radio Australia's two Southern listeners have identified this newcomer as "Radio France Asie" and heard them testing when they announced they were operating on 9.524mc.

Despite this announcement, they are not on this frequency but as we said before, 9.495mc. On opening and closing they have a distinctive piano interval signal which is easily identified once it has been remembered. We still have a slight doubt that it is actually the same station as Radio France Libre, but agree it is possibly in Saigon.

RADIO MALAYA

IN a recent letter to one of Radio Australia's DX-ers Calling Session, they said that they had been carrying out considerable testing and that during this period it was quite possible that reception of some of their harmonics had confused listeners.

Considerable expansion of this station is planned both in regard to technical facilities and also programme material and operating times.

Their present operating schedule is as follows but readers will notice that no mention is made of 7.2mc though this channel is still in use, usually in parallel with 7.25mc.

Red Network
6.135mc 2.30 pm to 3.15 pm Indian.
3.15 pm to 4.30 pm Chinese.
4.78mc 7.30 pm to 9.30 pm Indian.
9.30 pm to 11.30 pm Malay.
11.30 pm to 1.30 am Chinese.

Blue Network
7.25mc 2.30 pm to 3.30 pm English.
3.30 pm to 4.30 pm English.
7.30 pm to 8.30 pm Burmese.
8.30 pm to 1.30 am English
Sat. 4.30 pm to 7.25 pm English.
7.25 pm to 9.30 pm English.
Sun. 11.30 am to 2.30 pm English.
4.30 pm to 7.25 pm English.
7.25 pm to 2.00 am English.

Kuala Lumpur, on 6.025mc rebroadcasts the Blue Network of Radio Malaya in addition to local programmes.

U.S.A. STATIONS CHANGE FREQUENCIES

JUST as we go to press we notice that both the Voice of America stations and the Armed Forces Radio Service stations have made some alterations in frequency.

Voice of America programmes can now be heard from 7.0 pm over KRCA operating on 6.08mc, 9.515mc and 9.6mc while KCBR is also carrying these programmes on 6.185mc.

The Armed Forces Radio Service have also opened up a channel in the 49 metre band at the same time and can be heard from KCBR using 6.04mc.

STATION ADDRESSES

STUTTGART: Sueddeutscher Rundfunk, Radio Stuttgart, 14, Neckarstrasse, Stuttgart, Germany.

HAMBURG: Nordwestdeutscher Rundfunk, Rothenbaumchausse 132-134, Hamburg 13, Germany.

LEIPZIG: Sender Leipzig, Springerstrasse 24, Leipzig N.22, Germany.

JANNINA: 8th Merarchia, Radio Jannina, 492, Taghma Dhiavivaseon, Jannina, Greece.

CRKRH: Radio Clube de Huiala, Sa da Bendeira, Lubango, Angola.

OQZRC: Radio Congolia, P.O. Box 63, Leopoldville, Belgian Congo.

RABAT: Radio Maroc, Immeuble des P.T.T., Rabat, French Morocco.

EAAAH: Radio Tetuan, Calle O'Donnell 11, Tetuan, Spanish Morocco.

FZKE: Radio Dakar, Pose Federal de Radio Dakar, Dakar, Senegal.

YDL: Radio Indonesia, Studio Padang, Sawahan 51, Padang, Indonesia.

YDK: Radio Indonesia, Studio Palembang, Talang Djawa 7, Palembang, Indonesia.

CFPCX: Canadian Marconi Company, 1231 St. Catherine Street, West Montreal, Quebec, Canada.

CJCK: Eastern Broadcasters Ltd., Radio Building, 308 Charlotte St., Sydney, N.S., Canada.

COBL: Radio Cadena Suaritos, 25 Num 1113, Habana, Cuba.

SHORT-WAVE Notes for the December issue are due on November 4. For the January issue they are due on December 9. Please send them direct to Mr. Ray Simpson, 80 Wilga Street, Concord West, NSW.

THIS MONTH'S VERIFICATIONS

VERIFICATIONS this month have been few and far between and this seems to have been the case with both the writer and other correspondents who have written. Admittedly there have been a few but all we received were of similar type to those that have already been covered in these pages.

We often think what a wealth of information there would be if all the stations we have written to were to suddenly decide to verify our reports. This can be appreciated when we consider that at the present time the writer has reports away to over 180 stations that so far have not replied, and we know that many other listeners have just as many and maybe more whom they are waiting to hear from.

The only two verifications we will mention this month are Johannesburg on 3.356mc and ZEA Salisbury on 6.018mc. We were particularly pleased to receive the former as we tried for a very long time before we were able to log this low frequency station as this rather high wavelength African is particularly difficult to hear except when conditions are favorable.

The second station, ZEA in Salisbury was heard at reasonably good strength and it was therefore gratifying to receive a nice letter of verification from the Radio Office confirming reception on 15th July last and advising that the frequency in use was actually 6.018mc rather than 6.02mc as we had reported.

Have You Heard

These?

PHILIPPINES: Some months ago now, we reported reception of the Manila station DZHB on 6.03 mc, and later DZHT on 9.73 mc. When the stations sent along their verification, they stated that they would later take into use DZHB on 11.855 mc and DZHT on the 19-metre band. No sign of these stations was heard until quite recently, when DZHB opened up on 15.3 mc instead of 11.855 mc, as previously advised.

This new one can be heard nightly, but suffers from severe interference from Singapore on the same channel. These stations are all operated by the Far East Broadcasting Co., and the broadcast call is DZAS.

POLAND: For some time now we have been hearing a station on 7.205 mc jammed in between GWZ and GWL, around 6.30 am. At first we thought it to be in Yugoslavia, as frequent mention was made of that country, but we have now confirmed that it is Warsaw in Poland. From 6 am till 6.30 am it carries the same programme as Warsaw on 6.215 mc, but from then onward till fadeout, around 7.15 am, it carries a different programme, which seems to be either a news commentary or straight news.

From 6 am, the programme is in French, with both lady and gent announcers, so listeners should have no difficulty in hearing it, provided you can separate from the two London stations.

MALTA: The Forces Broadcasting Station in Malta seems to be having great difficulty in finding a suitable outlet for its programmes, as it has recently opened on still another frequency, this time 6.02 mc, which can be heard every morning till station closes at 7 am. This channel is being used in place of the one on 4.965 mc, and carries the same programme as on 7.22 mc.

The latter is much the louder, but the new one on 6.02 mc is quite good, however, except for slight interference from Rome on 6.01 mc. As the programme is all in English, it is quite easy to find and closes with the usual announcement, "This is your Forces Broadcasting Station, Middle East."

ITALY: After a few weeks of staying put, so to speak, Rome has again begun experimenting on new frequencies. The latest new one is on 5.98 mc, which is now heard daily from around 6 am. Just prior to opening at the above hour, it has a continuous 15 second interval signal, followed by announcement in Italian, "Radio Italiana."

All the programmes we have heard have been in Italian, and are different to the other programmes, being heard on the near constant 6.01 mc. The new one is not particularly loud, and do not mistake HVJ on 5.97 mc for Rome, as the Vatican City transmitter is very strong at the same time, and tends to blot out the 5.98 mc station.

TANGIER: In last month's issue, we reported receiving a verification from the Tangier station, EAAAA, which up till that time had been operating on 7.06 mc. Since these notes were written, EAAAA has changed its frequency to 7.12 mc, where it is heard, at much better strength. This one can be recognised by its slogan, "Radio Africa," which is given quite often by both lady and gent announcers.

There is another Tangier station on 15.05 mc operated by Par-American Radio and which is supposed to be on the air from 10 pm to 10.30 pm daily testing out their antennas. We have heard a strange station at the above times, but at time of writing are not certain that it is actually Tangier.

FLASHES FROM EVERYWHERE

CAMEROONS: In the September issue we published a paragraph giving details of Radio Douala's transmissions on 9.15 mc and we now have some further information regarding this station, which we gleaned from Seden Calling DX-ers. According to a letter recently received from the station, in addition to their transmission on 9.15 mc from 3.30 am to 6.30 am, which is with a power of 600 watts, they have a 1 kw transmitter in service operating on 7.287 mc and on the air at the same time.

It is their intention to discontinue use of the 600 watt transmitter in the very near future, but whether they will eventually use 9.15 mc or 7.287 mc is not clear.

GUATEMALA: For this Central American country we have word of two new stations, the first one being TGNA, which is located in the capital, Guatemala City, and is said to be operating on 6.04 mc, their address being PO Box 801, Guatemala City. Exact operating times are not known, but it is said to close at 1.15 pm. The second one is TGBA, located in Mazatenango and using a frequency of 8.1 mc between the hours of 11 am and 1 pm; 11 pm and 1 am; and 3 am and 5 am.

It is suggested that the best time to try for this one would be from 11 pm onward, but up to the present we have been unable to find a trace of it.

DENMARK: Now that the 19-metre band is improving so much at night, we have been able to hear the Danish station OZ1 at very good strength on 15.165 mc. It is on the air on Tuesdays, Thursdays and Saturdays from 8 pm to 9 pm. On Tuesdays, they have a mailbag session and a DX programme. This frequency is also in use on the same days from 10 am till 11 am, but so far we have not been able to log it at this time.

Copenhagen also is on the air daily from noon till 1 pm in the 31-metre band on 9.52 mc with a programme in Danish. There is also an English programme daily except Monday, from 1 pm to 1.30 pm, so there is ample scope here for everyone to log at least one of these Danish transmissions.

KENYA: It is a long time now since we have had any word regarding the Forces Broadcasting Station at Maccinnon Road in Kenya. In fact, the last word was when we received our verification for their 7.175 and 7.22 mc transmissions when they said they were no longer using a short-wave outlet, but were only transmitting in the broadcast band.

We have now heard through the DX session from Radio Australia that this station is again on the short-wave bands, using 6.115 mc at the following times:—Monday to Saturday, 1 pm to 3 pm; 7.30 pm to 9.30 pm; Tuesday to Saturday, 12.01 am to 5 am; Sunday 12.01 am to 6 am, and 3 pm to 5 am Monday. This will be a rather difficult transmission to log, but careful listening may enable you to hear them.

HUNGARY: There has been a remarkable improvement in the broadcasts from Radio Budapest, and at the time of writing this station can be heard at really excellent strength from around 6 am. Although they are supposed to be using 11.91

RADIO AUSTRALIA'S BROADCASTS

While many listeners are well aware of the excellent English programmes given from our own Radio Australia, we think there are quite a number who do not know of the wide nature of this stations transmissions. This station, which was formerly under the control of the Department of Information, has now been taken over by the Australian Broadcasting Commission.

At first it was thought that this may have meant a curtailment of some of the broadcasts, but judging by the latest schedule just received, it is still providing for listeners in many parts of the world. Some of our less experienced listeners will no doubt have heard Radio Australia in some of their foreign language programmes, but owing to their lack of experience in foreign tongues may not know that they are actually listening to Shepparton or Lyndhurst stations.

So that these readers can look out for these stations we are printing the full current schedule showing call letters, frequency, times on the air and target area. With the help of this list, we think you will be able to follow these stations without any difficulty, and if you care to write to them they will be pleased to send you a verification card.

Call	Freq. m	Mon-Fri.	Sat.	Sun.	Target Area
VLA8	11.76	0600-0900	0600-0900	0600-0915	British Isles and Europe
VLC	15.20	0600-0906	0600-0900	0600-0915	British Isles and Europe
VLB11	15.16	0629-0900	0629-0900	0659-0915	Japan, N. Pacific Is.
VLC	15.20	0900-1050	0900-1200	0915-1200	S-E Asia (Malaya)
VLA10	17.84	0915-1050	0915-1200	0928-1200	S-E Asia, S-E Asia (India, Pakistan, Malaya)
VLG11	15.21	1050-1330	—	—	S-E Asia, N-E Australia.
VLB5	21.54	1245-1415	1200-1245	1200-1415	Japan, N. Pacific Is.
VLC	15.20	1445-1415	1200-1415	1200-1415	S-E Asia (Malaya).
VLA10	17.84	1245-1430	1200-1430	1200-1430	S & S-E Asia (India, Pakistan, Malaya).
VLB5	21.54	—	1245-1730	—	Japan, N. Pacific Is.
VLA10	17.84	1430-1545	1430-1545	1430-1545	S & S-E Asia.
VLB5	21.54	1430-1545	—	—	Africa.
VLA10	17.84	1430-1545	1430-1545	1430-1545	N. America (West Coast)
VLA10	17.84	1545-1655	1545-1655	1545-1655	S & S-E Asia.
VLG11	15.21	1600-1640	1600-1640	1600-1640	Tahiti.
VLC	12.20	—	—	—	French Indo-China.
VLA10	17.84	1655-1815	1655-1815	1655-1815	British Is., Europe and S. Asia.
VLC	15.20	1655-1815	1655-1815	1655-1815	British Is., Europe and New Zealand.
VLB3	17.76	1655-1815	1655-1815	1655-1815	British Is., Europe and New Zealand.
VLG11	15.21	1700-1730	(Fri. Only)	—	Thailand.
VLG11	15.21	1745-1845	1745-1845	1745-1845	New Caledonia.
VLA6	15.20	1828-2130	1828-2130	1828-2130	Japan, N. Pacific Is.
VLB4	11.85	1828-1950	1828-1950	1828-1950	N. Asia, Japan.
VLG11	15.21	2000-2130	2000-2130	2000-2130	S and S-E Asia.
VLC	15.32	2030-2100	2030-2100	2030-2100	S-E Asia.
VLA6	15.32	2100-2130	2100-2130	2100-2130	Indonesia.
VLA5	15.20	2130-2355	2130-2355	2130-2355	S and S-E Asia.
VLB4	11.85	2130-0000	2130-0000	2130-0000	Japan, N. Pacific Is.
VLC	15.32	2200-0000	2200-0000	2200-0000	S, and S-E Asia.
VLA6	15.20	0000-0100	0000-0100	0000-0100	N. America (East Coast).
VLB4	11.85	0000-0100	0000-0100	0000-0100	British Isles, Europe.
VLC	15.32	0000-0100	0000-0100	0000-0100	S, and S-E Asia.
VLA6	15.20	0000-0100	0000-0100	0000-0100	N. America (Central).
VLC	15.32	0100-0215	0100-0215	0100-0215	S, and S-E Asia.
VLB4	11.85	0100-0215	0100-0215	0100-0215	N. America (West Coast).
VLA4	11.77	0115-0215	0115-0215	0115-0215	Africa.
VLG11	15.21	1650-1830	—	—	S-E Asia, N-W Australia.
VLG11	15.21	1050-1845	—	—	New Guinea.
VLG11	15.21	1600-1640	1600-1640	1600-1640	Tahiti.
VLG11	15.21	1700-1730	(Fri. Only)	—	Thailand.
VLG11	15.21	1745-1845	1745-1845	1745-1845	New Caledonia.
VLG10	11.76	1859-2330	1859-2330	1859-2330	New Guinea.

mc, they are only being heard on 6.247 mc and 9.83 mc. This latter outlet is the better of the two, and when they give the news in English, at 7 am, it can be followed word-perfect.

The 6.247 mc transmission is also good, and only slightly less so than 9.83 mc. During the news in English, they ask listeners to send reports of reception giving their comments on the programme and strength of signal, addressed simply "Radio Budapest," Hungary.

GERMANY: In a recent issue of Sweden Calling DX-ers, they publish a paragraph concerning "Radio Free Europe," which we think may be the same station as we reported recently as heard on 6.13 mc. According to the paragraph we mentioned, Radio Free Europe is operated by "The National Committee for a Free Europe." Programmes are prepared at studios in the Empire State Building, New York, and transmitted by a relay station somewhere in Central Europe.

Transmissions are said to be beamed to all countries under Communist control. Six other transmitters are planned, including some medium-wave outlets. According to another source, the 6.13 mc station is listed as "Radio Europa Libera."

IRAN: We hear from Art Cushen that he has verified an Iranian station, EPP, which operated on 4.04 mc, his report being the first received by the station. EPP is now supposed to be operating on 3.94 mc with a power of 2 kw. Other listeners report hearing a station on 6.845 mc with the same programme as EPB on 15.1 mc, audible around 6 am, but when reported to the Iranian authorities, they made no mention of the 6.845 mc outlet.

According to our lists, the following are listed for this country: "Persian Forces," 7 mc in Chelman, 7.95 mc in Shiraz, and 6.845 mc in Teheran. In addition, Teheran is assigned to EQD 4.78 mc, EQC 9.66 mc, EQB 6.155 mc, EPF 8.11 mc, and EPB 15.1 mc. There is also an outlet with no call letters on 4.03 mc.

NEW STATION LOGGINGS

Call	Kc	Metres	Location.	Times Heard.
ROME	5980	50.17	Rome, Italy.	6.30 am.
F.B.S.	6020	49.83	Malta.	6.30 am.
KCBR	6040	49.67	Delano, Cal. U.S.A.	7.00 pm.
TGNA	6040	49.67	Guatemala City, Guatemala.	1.00 pm.
KRCA2	6060	49.50	Dixon, Cal. U.S.A.	7.0 pm.
F.B.S.	6115	49.06	Mackinnon Road, Kenya.	5.00 am.
KCBR	6185	48.50	Delano, Cal. U.S.A.	7.00 pm.
EA9AA	7120	42.13	Tangiers, Tangier.	7.00 am.
SP41	7205	41.63	Warsaw, Poland.	6.00 am.
HRXW	8982	33.40	Tegucigalpa, Honduras.	8.00 am.
DZ12	9550	31.41	Manila, Philippines.	9.00 pm.
KRCA	9600	31.25	Dixon, Cal. U.S.A.	7.00 pm.
KHANIA	10050	29.86	Khania, Crete.	6.00 am.
DZH8	15300	19.61	Manila, Philippines.	8.00 pm.

ELECTRONIC
A & R
EQUIPMENT

A & R Transformers and Reactors

ELECTRONIC
A & R
EQUIPMENT

This advertisement is designed primarily to introduce our products to the readers of "Radio and Hobbies."

Since the inception of this Company, five years ago, we have developed over 800 types of Transformers and Chokes. We conservatively estimate that in those five years our factory has produced 30,000 items.

Our range of work is wide, reaching from Output Transformers for Hearing Aids, to 5 K.V.A. Power Transformers.

Each month, in this publication, items selected from our catalogue will be featured.

Transformers for Radio, Audio Sound Film Projection and Industrial requirements.

All A & R products are fully guaranteed against faulty workmanship and materials for a period of twelve months from the date of purchase. Each and every item is fully checked at the rated load with rigid tests to guard against insulation failure.

Due to the conservative rating of our products, the values indicated on the terminal panel are for continual operation—there is no need for the consumer to add a margin for safety—our engineers take care of that.

REMEMBER . . . GOOD TRANSFORMERS MAKE GOOD EQUIPMENT

A. & R. Electronic Equipment Co. Pty. Ltd.


378 ST. KILDA ROAD, MELBOURNE, S.C.1

Phones: MX1159, MX1150

Tape Recorders now available!

TELETAPE

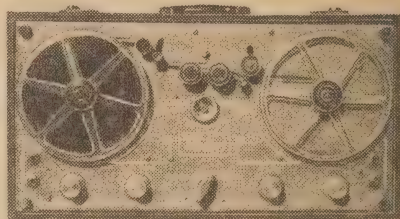The new Teletape recorder incorporating all the following exclusive features is now available in limited quantities for delivery to Interstate and country mail order clients.



With these exclusive features

- High fidelity reproduction to $7\frac{1}{2}$ KC.
- 30 or 15 minutes per reel of tape.
- Two inputs, microphone and pick-up.
- Two outputs. Phones and external speaker.
- Built-in speaker.
- Weight only 39lbs.
- A fast forward wind.
- Automatic QUICKLIFT rewind mechanism that permits rewind without unthreading.
- TWO HEAVY DUTY MOTORS.
- Blank and library tapes available. Library (tapes may be purchased outright) includes dance music by world famous orchestras, comedy and party numbers, organ, religious and symphony music.

Write Now For Illustrated Brochure to —

H.N. CHAPMAN COMPANY

10th FLOOR, KYLE HOUSE, MACQUARIE PLACE, SYDNEY.

BARRACLOUGH B. MOORE

Since the war radio amateurs have been gradually extending the range of their transmissions on the UHF bands. A greater knowledge of propagation on these frequencies gained by recent experience has assisted, as have improvements in antenna design and increased power.

DISTANCES now covered are greatly in excess of anything anticipated a few years ago. Distance records on the 144mc band were shattered during late September and the record now stands at 1300 miles. 2BAV was responsible for the good work and he worked two W5's at that stance, as well as a W0 at 1175 miles. The latter was using only 12 watts input, but W2BAV uses a 48 element beam that would help. Incidentally he runs 40 watts input on 144mc. It was thought at the signals were reflected and that ionospheric bending was not responsible for the conditions.

HIGH POWER

The general trend in the US is towards high power on 144 mc/s and many amateurs are running a full KW on this band. W4AO of Virginia increased power to 1KW from 100 watts and trebled his round wave coverage. He has no trouble working consistently over 100 miles even under bad conditions. He has worked considerable number of stations between 700 and 900 miles during aurora disturbances.

During the beam north during the aurora, signals are reflected back to many portions of the States. W4AO uses a 32 element beam horizontally polarised, plus a 10 element reversible array.

During September, NSW amateurs established a new 50mc band record on the State VK2ABH, 2WJ, 2VW and 2WY operating from Blackheath in the Blue Mountains established contact with VK2AKC station of the Kingsford Radio Club in Sydney. The distance covered was 55 miles.

The portable transmitter consisted of a 955 super regenerative detector and audio stage. The antenna a 24 element array.

It looks as if 50mc will soon provide some of the anticipated seasonal DX. In early October during the day a number of carriers have been heard fading badly and coming from the North East. They were possibly KH6's or W's.

MAKE USE OF WWV

AMATEURS use the standard frequency transmissions of the U.S. Bureau of Standards so often that the following information on WWV may be of interest.

The station is located at Maryland, 20 miles north of Washington DC and the frequency of the transmission is held constant by one of three vacuum mounted quartz crystals which run continuously on 100kc/s.

These crystals are located in a concrete vault 30 feet in the ground and each is encased in an insulated temperature controlled box.

The vault is seldom opened, as the heat from a human body is sufficient to effect a noticeable change in temperature and frequency of the crystals. The crystal which is holding its frequency most accurately, is used to control the standard frequency transmissions at any given time.

The transmissions from WWV are accurate to the Broadcast Band to one part in 50 million or point 000,002 per cent. The maximum deviation allowed by the F.C.C. from allocated frequency in that band is 20 cycles or point 02 per cent.

As the frequency is multiplied, the margin of error increases but even at 35,000kc/s accuracy is still better than a cycle. As well as controlling the frequency of the transmissions from 2.5 to 35 mcgacycles, the original 100kc signal is divided to control the 440 and 1000

cycle tones and even runs a 50 cycle clock.

The second "beeps" that can be heard imposed on the transmissions is a 1000 cycle tone that lasts for 5/1000 of a second. The standard 440 cycle tone is also transmitted for given periods.

OVERSEAS COMMENT

THE Clapp Oscillator is in the news again, not with reference to its virtues as a VFO, but in regard to its origin.

You will remember that information on the Clapp appeared in QST in 1948 (originally in the I.R.E. proceedings). Later the Technical Editor, George Grammer, WIDF, pointed out in reality the circuit appeared in QST back in 1941.

A new claimant as the originator is B.B.C. Engineer G. G. Gouriet. He states that he first used the circuit in 1941 and it has been used practically exclusively in B.B.C. equipment since that date. We are mainly interested in its efficient operation and whoever did invent it, is to be congratulated.

The RSGB celebrated this year the 25th Anniversary of the publication of their official journal the R.S.G.B. Bulletin. From a circulation of 1000 in 1925 it has now increased to 14,000. Since the war the society has had great difficulty in obtaining sufficient paper to keep the journal at a reasonable size. The position has improved slightly and the Bulletin now runs to 40 pages per month.

The magazine is available to members free of charge and membership costs 12/6 sterling. Special attention is paid in its pages to TVI-free equipment and one can keep abreast of technical development in amateur affairs in Great Britain by perusing its pages.

The G's are certainly in some difficulty over the erection of their towers and beams in many areas. Both G8QW and G2AK have been refused permission to erect towers for supporting their rotary arrays.

Both these amateurs first struck trouble when their respective local councils would not grant an authority for the building of towers. Appeals were then made to the final authority, the Ministry of Town and Country Planning, and these were also rejected.

The Ministry gave as its reason, that this proposed development, would be inconsistent with the proper planning of the area.

Representatives of the RSGB were in attendance at both appeals and further investigations are being made in the hope of overcoming the position as it now stands.

BLIND AMATEURS

Radio Technical Education of the blind is receiving much more attention in recent years and Bill Zech VK2ACP of Katoomba is obtaining from the USA copies of a Radio and Electronics Guide published monthly in Braille. This magazine is edited by W2TIO. In England considerable use is made of the Talking Book scheme, where quite a number of technical books have been recorded. The RSGB has proposed that a talking book version of the Amateur Radio Handbook be produced, and that they would be glad to contribute to the cost of such work.

Sir Ian Fraser, well-known authority on matters pertaining to the education of the blind, offers the suggestion that radio amateurs could assist greatly if they would give information on the operation of the Talking Book Machines to blinded persons.

Quite a number of these machines are returned to the National Institute for

the Blind as unserviceable, when a small adjustment would make them work again.

Sir Ian, a past president of the RSGB, who is blind himself, considers that radio amateurs could assist greatly if they would keep an eye on Talking Book Machines in their locality, and assure that machines are only returned to the Institute when they are in need of a major overhaul.

Recently in England, the call sign G3GYL was issued to Miss Nina Barrett who has the misfortune to be blind. In a short twelve months Miss Barrett mastered the Morse code and took orally the same technical examination as did other candidates for the amateur licence. G3GYL only operates on 3.5mc CW at the moment.

Considerable investigations is going on at all times to improve the usefulness and accuracy of the service. In the latter case efforts are being made to better the standards in the UHF spectrum.

With the ever increasing number of television stations in the U.S. it has been necessary to operate stations on the same frequency. If station frequencies can be controlled extremely accurately simultaneous transmissions can be made from stations in close proximity. At the moment this is impossible due to the lack of standards in the spectrum.

CERTIFICATE DESIGNS

THE Federal Executive of the WIA has invited new designs for the Australian DXCC certificates, and it is hoped that the amateurs who were not happy about the old one will submit their own design.

The NSW WIA combined Newcastle and Sydney Field Day will be held at Woy Woy on November 26th. Assembly will be at 11 am at the usual point, the Masonic Hall, and a full programme has been arranged. The hidden transmitter search will be run on 144mc (horizontally polarised) and 3.5mc. No special arrangements have been made for meals but light refreshments will be available.

Cec Hardman, VK2KR of Woy Woy, will be pleased to hear from anyone who can attend and the local gang at Gosford and Woy Woy have been meeting on 50mc to discuss details for the Field Day.

Reports on the special amateur band predictions and charts presented monthly in the WIA magazine Amateur Radio are earnestly required. These charts without a doubt are being used extensively and it is desired to learn how they work out in practice.

Comments on the usefulness of these charts should be forwarded to the WIA.

The NSW Division's UHF section opened the UHF summer season with 144mc contest run between October 13th and 28th. Support during the opening days was excellent.

Dr. Allison VK1RA at the September meeting of the NSW Division presented three films of Life on Heard and Macquarie islands and the Antarctic. The doctor explained many phases of life down under and the evening was very entertaining, attracting the largest crowd at a monthly meeting for many months.

THE VK/ZL CONTEST

The VK/ZL DX Contest started off under very bad conditions and by 0100 hours on the first evening many amateurs who would normally operate throughout the night, had retired. The contest received good support but amateurs everywhere complained of the poor conditions.

Bill Leonard W5KSL reviewing the contest over the Voice of America claimed that 'Australian signals were rather poor but the 7mc provided the best possibilities for consistent working. Quite a number of contacts were made

FERRIS Electric TRAINS


ACCURATELY ENGINEERED JUST LIKE THE
REAL ONES



*So realistic in every way . . . a joy
to the hobbyist and to every man
and his boy*

No corners have been cut, no detail has been spared in the accurate engineering of these model trains. THE POWER car has one of the sweetest running little motors ever designed. It incorporates automatic stop, start and reverse and headlights. Ferris TRANSFORMERS are skillfully manufactured to ensure trouble-free performance. Look at that Ferris Model transposed on the Sydney Harbor Bridge—doesn't it look the real thing? That's typical of all this equipment as you can see once again from the PARCEL VAN illustrated below.

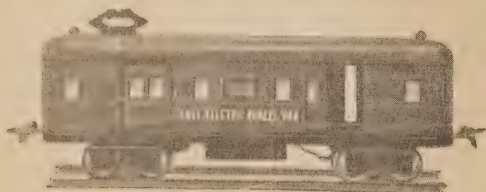Here's an opportunity to add some really good equipment to your model railway. These trains are designed to run on standard "O" gauge tracks. Further literature and price lists are available. Write in now and they will be forwarded by return mail.



COUPON

TO FERRIS BROS. PTY. LTD., DOWLING ST., EAST SYDNEY.

Please send me by return mail full details and price list of your Model Electric Trains.

NAME

ADDRESS

R & H 11/50

with American stations on 3.5mc/s. Scoring well in NSW in the CW section were VK2GW, 2E2C, 2GG, 2ZC and 2AHA.

Following the original experiments on influence of the ionosphere conducted by Professor Bailey of the Division of Physics Sydney University further tests were made between 0100 and 0200 hrs on October 4th and 11th. Amateurs in the Blue Mountains and the Goulburn area forwarded reports. National Station 4QR on 580kc/s was again used and the pulse transmission was made from the New England College of the University. Reports forwarded by amateurs on the original experiments according to Professor Bailey were valuable and greatly appreciated.

The NSW division has decided to run a hamfest in conjunction with the National Field Day to be held in January. At the meeting to organise the day were past presidents Frank Goyen VK2UX, Wal Ryan VK2TI, Morrie Meyers VK2VN, and a full and comprehensive programme is to be arranged. Tentative details are as follows—the hamfest will open on the Friday evening when a special monthly meeting will be held. Saturday afternoon will see competitions and lectures presented, and in the evening a dinner will be held. On Sunday, special prizes will be presented to parties operating in the National Field Day and it is anticipated that many stations will be in the field.

DX AND PERSONAL

DX of the month was perhaps FB8ZZ operating from Isle Nouvelle Amsterdam in Antarctica. On 14040kc/s he appeared around 2100 hrs E.A.S.T.

VK5BY managed to contact him but within 10 minutes of his appearance he was receiving the attention of the usual group of W stations. It was a typical September evening on 14mc—hardly a DX station breaking through, certainly no W stations.

The FB certainly brought W3BES, 3CPV and 2AUQ plus a hundreds out of hiding. Even VPJNM, rare as he may be, was unable to compete with the S's. Americans. If they are only using a KW then some of their beams must have a gain of 40 DB., considering the fact they can produce an S9 signal on a "dead" band.

Jack Young VK2OY of Goulburn must really be putting a good signal into the US. He received special mention in a Voice of America Broadcast as being the loudest Australian on the East Coast—"like a local" was the exact term used.

FKS is the prefix used by French troops in Austria, while most of the Italians have made a change and are now signing IT instead of the old I prefix. An odd Frenchman can be heard signing stroke FC and is located in Corsica.

VQ8CB in the Chagos Islands is on again, and appears between 2100 and 2200 hours E.A.S.T. on 14030. He is rather weak as he is only using low power, but can be contacted.

Just to state that the lower frequency bands are still good. Hugh VK2WH contacted a W6 and W7 on 3.5mc telephony at 2330 hours E.A.S.T.

South Africans are again coming through in the late evenings. ZS5U has been heard as early as 2030 hours which is about a record for 14mc working.

Two old-timers joined the ranks of "Silent Keys" during September—KZ5PA and Bill Hall ZL2BH.

KZ5PA, active from the Canal Zone for many years, is best remembered as WY2AB in the thirties, while Bill was active on all bands throughout the years. Many Australians remember ZL2BH for pleasant 80 metre yarns in the last few years.

PK5AA 14060kc/s is active most evenings, and is rather popular as Dutch Borneo is still a rare country. HC2IS caused some excitement on 7mc/s as South Americans are pretty scarce on that band. Quite a number of Australians took the opportunity of making a WAC.

YOUR OPPORTUNITY

to join the world-wide ranks of amateur transmitters! The Wireless Institute of Australia holds regular classes in Sydney to assist Sydney and suburban enthusiasts to obtain their Amateur Operator Certificates of Proficiency.

Write for particulars to the Class Manager, W.I.A., Box 1734, G.P.O., Sydney.

Why do things happen?

(Continued from Page 15).

per downward? No, the paper came

So likewise does it happen to an airplane wing. It was discovered that the upward curve of an airplane wing forced the air caused by the downward motion of the plane to travel at a higher speed over the top of the wing than on the comparatively flat surface underneath. This caused a reduced pressure on the top because of an increase of velocity and accounts for three-quarters of the lift. This reduced pressure may not account for much per square inch, being it is perhaps only a couple of inches lower per square inch than underneath. But multiply this by the thousands of square inches of a plane's wing surface and the result is a lift amounting to some tons.

AIR PRESSURE

While we are on the effects of air pressure, it is well to finalise this discussion by dealing a little with air pressure.

Air pressure is responsible for the suction which we commonly call sucking.

When we refer to sucking liquids up a tube we really mean that we reduce the air pressure at the top of the tube and the higher atmospheric pressure on the surface of the liquid forces the liquid up the tube.

Those familiar suckers used for attaching sun visors to windscreens or glass table tops to counters, &c., rely on this pressure for their action. When you press one of these suckers on a smooth surface you force all the air from between the sucker and the smooth surface. The atmosphere pressing on the outside surface of the sucker at 15 pounds per square inch makes it difficult to pull the sucker off.

Finally, you can easily demonstrate why streamlining of cars, aeroplanes and ships is necessary and how it works. Light a candle and hold a flat piece of cardboard between the flame and your mouth. Blow on the cardboard. The flames comes toward you.

Now bend a piece of cardboard about four inches wide and a foot long into the shape of a blunt-nosed boat, with the rear end tapering off to a point. Place this between the candle flame and your mouth and blow on the blunt end. The candle flame goes away from you.

"DRAG"

There is a popular idea afoot that the resistance of air or water to a car, plane or boat is caused by the water or air that hits the front end. This is not right. It is caused by the air or water being torn from the latter end.

The above cardboard and candle demonstration proves this. In the case of the flat cardboard the air can't flow smoothly past the cardboard, but rushes around and past the edges and creates a partial vacuum at the back. The flame is therefore sucked or, more correctly, pushed toward the cardboard by the air behind it coming in to fill the partial vacuum.

A COURSE IN TELEVISION

(Continued from Page 59)

the cathode circuit and produced by the pulses of plate current.

When the signal is first applied to the valve, the plate current builds up a voltage in the cathode circuit which is "averaged out" and held constant by the long time constant of R and C. Thereafter, plate current flows only during the high amplitude synchronising pulses, which are sufficient to overcome the standing cathode bias.

Once again, great care is necessary in selecting the values for R and C and also a high Gm. tube which generates high plate current pulses for moderate input signals.

The diode versions of these two circuits are shown in figures 3c and 3d.

In figure 3c, the components R and C are given a time constant long enough to hold the diode plate substantially negative and therefore prevent plate current flow except on the positive peaks of signal. On these positive peaks, however, a voltage appears across the cathode load resistor RL, while the corresponding current through "R" helps to maintain the charge across "C" at a figure approximating the black or blanking level.

In figure 3d both loads are in the cathode circuit. Here R and C combine to hold the cathode initially positive, the synchronising pulses appearing across RL.

DIODE SEPARATORS

Diode separators are less sensitive than triodes or pentodes, for obvious reasons, but there are cases where they may be more convenient. The pulses produced by the diode arrangement of figures 3c and 3d are positive-going, while those from the plate of an amplifier valve, as in 3a and 3b are negative-going.

The matter of pulse polarity is important, in that most pulse generators are triggered by positive-going pulses. Therefore, the sense of the synchronising separator and the number of possible synchronising amplifiers must be arranged to maintain a positive-going signal to trigger the oscillators.

Thus far, synchronising separation has been considered as a function quite separate from detection and d-c restoration—subjects which have already been covered in these columns.

In practice, however, the functions

of synchronising separation and d-c restoration are frequently combined, operating in conjunction with the final video amplifier. While it is not possible to examine all likely combinations, one simple circuit will serve to illustrate the idea.

In figure 4, V1 is the final compensated video amplifier, delivering its signal to the picture tube through the coupling condenser Cc. From the connection of the diode, the signal is obviously so phased that the synchronising pulses will be negative-going.

The action of the diode tends to line up these negative peaks, thereby having the desired d-c restoration effect on the signal applied to the picture tube grid. The signal pulses representing white are then positive going with respect to this reference, which is according to requirements.

At the same time, the negative pulses applied to the cathode produce a burst of current through the diode, allowing the synchronising signals to appear across the resistor in the plate load.

LIMITATIONS

Circuits of this nature, although manifestly simple, suffer from various limitations. Not the least serious is the effect of normal variations in line voltage, which change both the gain of the stages feeding the separator and the marginal voltages which govern its operation. The separation of synchronising and picture signals is therefore likely to be erratic, while the shape of the pulse may depart substantially from the desired rectangular form.

The tendency is for pulse requirements to become more stringent as the frequency increases so that circuitry which is adequate for medium definition systems is a virtual failure for high definition. As a result, it is not unusual to find voltage stabilising and wave shaping circuits to improve the contours and the consistency of the pulses.

It will be recalled that a composite signal contains timing pulses for both the vertical and horizontal sweep oscillators, the difference being in their spacing and duration. A problem which yet remains is to separate the pulse trains so that the resultant voltages can be applied to the respective oscillators.

GERMANIUM INFRARED LENSES

A TECHNIQUE of purifying germanium, the chemical from which lenses for spectacularly improved infrared equipment can be made, was announced in Oak Ridge, Tenn.

Lenses made from germanium transmit invisible heat radiation. The germanium lenses will do this even though they are an inch thick and do not allow ordinary light to pass.

OFF THE RECORD — NEWS & REVIEWS

The history of reproduced sound and how to get it has been an interesting one, none the less because of the prevailing "fashions" which from time to time have come and gone in the attempt to pin-point the most important factor in getting results. The importance of power output, transient response, and frequency response, have all been focal points of discussion in their day, each being the subject of much measurement and experiment.

By JOHN MOYLE

At the moment, the emphasis seems to be on intermodulation distortion, that rather elusive thing which is perhaps the hardest of them all to isolate and evaluate.

The word fashion isn't really a good one, because it might be considered to imply that none of the things are really important, but are simply fads which sound engineers fasten on from time to time.

The fact is they are all extremely important in their own way, as most of us have found from time to time. But the answer is really that they all bear on the same thing, and in

some cases, are merely different ways of attacking a problem of clean reproduction which is vitally affected by them all.

This intermodulation distortion can be explained quite simply as it concerns its simple forms. If for instance we play two different frequencies through an amplifying system, but insert in the output a filter which removes one of them, we should hear only the unfiltered note through the speaker. If intermodu-

lation distortion is present, however, we will hear the untouched frequency all right, but super-imposed upon it we will hear more or less of the second frequency which "rides in" on the first.

I think it will be fairly obvious that, if this effect can be noticed in such a simple case, it indicates that although an amplifying system may be fine when tested on single notes, it will be subject to more or less severe distortion when reproducing music which demands a waveform often exceedingly complex.

TECHNICIAN'S PARADISE

The subject is something of a technician's paradise, and it is not my idea here to blind you with science by treating it as such. Its effect on the listener is to make clear separation of musical instruments for instance, almost impossible, because they are always distorted by an admixture of other frequencies which originate in other instruments. It is one reason why orchestral records, for instance, sound confused and muddy on one speaker, but much cleaner on another.

The prime cause of intermodulation distortion in any amplifying system in non-linearity. This term may be explained by saying that a linear device is one in which the ratio between the magnitude of the input and the output is constant. It could be represented graphically as a straight line, and often it is. If this line shows any curvature over that portion which is used when the amplifier is operating, then it indicates non-linearity in that particular stage or device.

NON-LINEARITY

Now the opportunities for non-linearity in an amplifier are many, and, of course, must include the pick-up and the loudspeaker as well. This means that both electrical and mechanical non-linearity are concerned, for record reproduction involves the translation of mechanical energy into electrical energy, and back again to mechanical energy, a process which has already taken place at the record factory before the record ever reaches your turntable!

At the factory, however, there is generally an adequate supply of high grade equipment and facilities for checking linearity which are denied to most amplifier builders. So we can be fairly sure that what intermodulation troubles do exist in good modern records, they are quite




OLD TIME DANCE RECORDS

Harry Davidson
AND HIS ORCHESTRA
(OLD TIME DANCE SERIES)

- No. 57—Old Time Excuse Me Dances (Parts 1 and 2) DX.1474
- No. 58—Old Time Excuse Me Dances (Parts 3 and 4) DX.1480
- No. 59—The Jazz Twinkle (Franklin)
- No. 60—On Leave Foxtrot (Poor John) (Leigh-Pether) DX.1487
- No. 61—The Latchford Schottische (Harris-Bayford)
- No. 62—The Choristers Waltz (Phelps) DX.1498
- No. 63—Donella Tango (Oh! Donna Clara)
- No. 64—The Merry Widow Waltz (Lehar) DX.1505
- No. 65—Moonlight Saunter (Moonlight on the Nile) (Thurban)
- No. 66—Savoy Tango (Where the Cafe Lights are Gleaming) (Goehr) DX.1515

From all leading music stores.

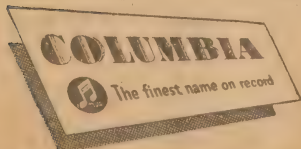

Columbia Graphophone
(Aust.) Pty. Ltd.
HOMEBUSH, N.S.W.

CH. 75.18

in value as compared with what it might produce at our end.

Coming now to the things we can do to reduce intermodulation the first is the selection of a good pickup. It's rather hard to say more than this, because intermodulation figures are rarely quoted for pickups, and in any case are likely to vary from one sample to another according to accuracy in manufacture.

Possibly the most important thing in the pick-up is that the armature should move in a constant magnetic field. This means a not too narrow gap, accurately placed armature, and one which moves over a small arc. In other words, if we consider the pick-up as a small electric generator, its electrical output must vary in direct and linear ratio with the movement of the armature, within its limits of amplitude.

AMPLITUDE

This last qualification is quite important, because it appears all along the line of reproduction. It is fairly easy to preserve linearity at low amplitudes or volumes, but when extremely high amplitudes are involved, and the armature of necessity approaches closer to the pole pieces, it operates in a much more intense magnetic field, and its output at that instance increases. In other words, we no longer have a linear relationship between armature movement and electrical output.

To a certain extent, this explains why some pickups will play loud, musically complex passages more cleanly than will others, while both are able to do a good job in quieter passages where the movement of the armature is not so great. In fact, it is probably true that the non-linear chain commences with the intimacy of the stylus tip contact with the record. This, of course, should be constant at all amplitudes, but I fear that only the best of the new light-weights, with their high compliances, approach this ideal.

Leaving the pickup, we come to the amplifier itself. Here our main consideration will be the valves. They are the actual amplifiers, and, today are used almost exclusively with wide-range resistance coupled stages.

THE VALVES

Now, non-linearity, even though it is in small doses, is a natural enemy of the valve. Most valves in gramophone amplifiers operate as voltage amplifiers, that is, they are fed with certain voltages in the grid circuit, and produce amplified versions of these voltages in the plate circuits. And here's the catch — these input and output voltages must be in direct or linear ratio if intermodulation is to be beaten.

The valves used are adjusted in such a way that they operate as class A amplifiers. The grid bias is so adjusted that the valve will accept a certain grid voltage and amplify it with good linearity. As soon as the input voltage exceeds a permissible figure, however, this linearity deteriorates very rapidly.

The obvious precaution, therefore, is to see that there is always a good margin of safety in the voltage handling capacity of the valves used in all stages. In practice, this should be something like 50 per cent. It is one reason why it is good practice to use high powered output valves, which are never pushed near their output limits.

The intermodulation distortion of an amplifier at half power may quite well be very low — only a few per cent — rising to a completely unacceptable level when approaching the limit of its rating.

LOUDSPEAKER

The same general story is true of a loudspeaker. Here, we have an electric motor which must produce output in direct ratio to input. As in the case of the pickup, we have a magnetic field with a moving component — this time, the voice coil. This coil must operate in a constant magnetic field for linearity. If it is energised to such an extent that the coil itself, moves to the weaker sections of the magnetic field round the gap, non-linearity is inevitable.

Speakers, therefore, should have a deep magnetic gap and a big magnet to hold up the lines of force if the voice coil is to sustain movement of large amplitude and stay in a constant magnetic field.

The alternative, of course, is to operate a speaker at well below its maximum level. Irrespective of design, this is a really good practice, and one of the most effective in avoiding intermodulation.

Operation well within limits also makes the task easier for the actual loudspeaker cone. Unless this is completely rigid, it is bound to break up in some way when asked to handle complex oscillations at high amplitude.

SUMMARY

When we realise the almost endless chain of electrical and mechanical operations which interpose between the original performer and the reproduced sound, we might well marvel that the finished product sounds half so good. But it will sound better without intermodulation distortion, and, if you can't do much about the design of your pickup or your loudspeaker, at least you can see that your amplifier is designed to handle the volume you require without overload, and, in fact, to operate well within its maximum capability.

There I'll have to leave this subject for the time being, although there are many other aspects I'd like to discuss. Some of them are rather hard to handle in a general way without getting off the track, but they have a big bearing on our approach to good sound.

Incidentally, quite a few relevant points on distortion have come up in the "Buy An Argument" series of articles. Amplifiers are under discussion right now, and you might get some interesting angles from reading our readers' letters and the technical editor's replies.

"The YORK"

4 VALVE BROADCAST MANTEL KIT SET

"The York" features:

Attractive Bakelite Cabinet (as illustrated); size 10½" x 6½" x 6½". Also available in cream.

Rola 5 inch speaker.
R.C.S. Intermediates.

Valves, 6J8G, 6G8G,
6V6GT, 6X5GT.

Full vision Dial.

A proved circuit with full instructions, easy to follow.



Complete to the last nut and bolt, including valves.

Price
£15/19/-
retail

Attractive Discounts to the Trade.

Build your own Radio Set and save pounds.



BLOCH & GERBER LTD.

WITH WHICH IS ASSOCIATED

THE WELDON ELECTRIC SUPPLY CO

40-42 YORK STREET, SYDNEY

TELEGRAMS: 'LESKO' SYDNEY

BX4221-T10 LINES

Also supplied as a Foundation Kit Set—a boon to the small manufacturer. Prices on Application.

ffrr—Full Frequency Range Re~production



Plessey

RECORD PLAYER

- The only Record Player featuring the patented automatic push-button start.
- The only Record Player which gives a choice of Decca ffrr, Acos Crystal or Magnetic pickup.
- The only Record Player which will increase your turnover and give years of trouble free service.

Distributed by:



UNITED RADIO DISTRIBUTORS PTY. LTD.

RADIO-ELECTRIC WHOLESALERS

Showrooms: 175 Phillip Street, Sydney. Offices: 183 Pitt Street, Sydney.

TELEGRAMS & CABLES: URD, SYDNEY

TELEPHONES: MA 9251, MA 1563

A SIMPLIFIED DUAL WAVE SET

(Continued from Page 35)

coils for the benefit of those who happen to have such a kit.

We will assume that you do not have a modulated oscillator. In any case, constructors with such an instrument will, no doubt, be familiar with the procedure. Quite a good amount of alignment can be done on broadcast stations if due care is taken.

Remember that the receiver is equipped with AVC and if you attempt to do the alignment on strong local stations the effect of any adjustment will be masked to some extent.

However, the AVC circuit is arranged so that it has a slight voltage delay characteristic and does not come into operation until a definite signal level is reached. Therefore, we suggest that you carry out the alignment procedure, or, rather, the final touching-up, on weak but steady signals such as can be expected from distant stations during daylight hours.

TUNING UP

After allowing the set to warm up for five minutes or so, tune in a station toward the high-frequency end of the band and adjust the aerial trimmer for maximum output.

Next, tune to a station at the low-frequency end of the band and adjust the padder until you receive it at maximum volume. Adjustment of the padder will affect the position of the station on the dial, so that it will be necessary to retune each time. With the chassis standing on its end, you should be able to juggle the padder and dial until you obtain the strongest signal.

Having obtained a satisfactory adjustment of the padder, loosen the rubscrew holding the dial drum to the condenser shaft and turn the drum as necessary to make the stations near the low-frequency end of the band correspond with the dial calibrations.

Then tune to a station near the high-frequency end of the band and adjust the oscillator trimmer until the dial calibration is correct. Peak the signal, or preferably a weak signal nearby, with the aerial trimmer. The alignment of the front-end circuits of the receiver is then complete, but if you are fussy you could repeat the whole procedure.

I.F. COILS

Up to date, the variable slugs in the IF transformers should not have been touched. They are set to the correct frequency during the normal testing procedure at the factory, but circuit capacities will change the settings somewhat, and it is necessary that they be readjusted.

Tune to a weak but steady station anywhere on the dial, and carefully adjust the slugs one by one for maximum output. However, it is a good idea to carefully note the original settings in case you have to return to them for some reason. This completes the broadcast alignment.

If your coil unit is fitted with

TRANSMITTER FOR 50 MC

(Continued from Page 45)

be mounted with connecting leads as short as possible, and preferably with the coil actually mounted on the condenser itself.

Assuming about 5 mills or more drive for the 807's, the last problem is that of instability in the final stage.

In the grid circuits, we have used a couple of parasitic chokes, just on principle, but in fact they were quite unnecessary.

It is almost impossible to avoid some regeneration in this stage, because the 807 internal capacitances and lead inductances are not low enough to avoid it at 50 mc. They should not be enough to cause oscillation of the stage, however, unless we add to their effect by not reducing external, unwanted capacitances and inductances coupling to a minimum.

STABILITY

In keeping the stage stable, therefore, there are two important points to be watched.

The first is that both cathodes should be well and truly earthed, and the second is that the screens should be individually bypassed right at their sockets.

The effect of the screen circuit on stability is a subject on its own, too large to analyse here. However, by a process of progressive experiment, the aim of which was to obtain the least possible grid current variation as the plate circuit was tuned to resonance, we found that cathodes individually earthed to the metal shield, and mica bypasses at each screen, not only produced this state of affairs, but prevented any tendency of the output stage to oscillate with or without load, and with or

without drive. Some regeneration exists, but not enough to seriously prejudice operation or adjustment.

In fact, by individual cathode bypassing, we were able to include a 200 ohm cathode resistor for use when tuning up to avoid excessive plate and screen currents, but which is switched out when the transmitter is in use. This is a convenience, but a rather useful one if the voltage is more than about 400.

Better than mica condensers would be the special ceramic types now available, which are small, allow short leads and virtually eliminate condenser inductance—quite important at 50 mc, and which limits the value of even mica condensers as bypasses.

There is nothing much more in the transmitter, which is not shown in the circuit and pictures. Although the meter is switched to read the plate current of the 6V6's, it is the grid current of the 807's which is really the most valuable check on their operation.

Do not operate the 807's for more than a few seconds at a time without a load, as the screen current may rise to a dangerous figure if you do. When testing, use a 60-watt lamp as a dummy load.

We used two power supplies—one to give about 350 volts for the 6V6's, and another to give 600 volts for the final.

One supply could be used, however, selecting dropping resistor values to give the right voltage distribution.

A standard 807 class AB2 modulator will be ideal to modulate this transmitter. With 600 volts available, it will produce plenty of output when loaded to about 160 mills plate current.

variable iron dust cores the procedure is slightly different. Begin by adjusting the aerial trimmer at the high-frequency end of the band but at the low-frequency end of the band adjust the aerial coil slug for maximum output. Note that there is no necessity to rock the dial backwards and forwards to make this adjustment. The oscillator coil core is set at the factory and should not be interfered with.

Loosen the dial drum screws to make the stations correspond with the dial, retune to the high-frequency end of the band and correct the calibration with the oscillator trimmer.

S.W. BAND

It now remains to check the alignment in the shortwave position. Do not be disappointed if when you first switch in the shortwave coils you hear only a few weak signals. Conditions on the shortwave bands are subject to great change, according to the time of day and time of year. Ray Simpson's shortwave notes in recent issues will act as a guide as to the best stations, frequencies and transmission times.

If you dual-wave unit has air-cored coils there will normally be only two adjustments to worry about on the shortwave band. The padder capacitance value is not as critical as on the broadcast band and an adjustable padder is not required.

Start with both trimmers about halfway in, and tune in a station toward the high-frequency end of the band. Then peak the aerial trimmer. You may find that the aerial trimmer has a very slight effect on the dial-setting, so it is a good idea to retune after each adjustment.

The dial calibration can be adjusted with the oscillator trimmer, but remember to readjust the aerial trimmer after each change in calibration. Actually you may have to do a certain amount of listening before you can identify a station positively and obtain its exact frequency.

With iron-cored shortwave coils, adjust the aerial slug for maximum output at the low-frequency end of the band and return to the high-frequency end and recheck the aerial trimmer at the high-frequency end. Calibration can be connected with the oscillator trimmer, in which case the aerial trimmer must be readjusted.

Are you looking for
a market
for that invention?

*That's our business — marketing inventions
of all types, sizes, value or application*

We have a complete, Australian-wide manufacturing and marketing organisation equipped to:

1. Produce your invention in quantity.
2. Distribute the product through marketing companies.
3. Promote the sale through merchandising and advertising.
4. Compensate the Patentee by pre-determined Royalties.

We have extensive manufacturing facilities in two States.

We have affiliations in America, England and other countries, so that if your invention is approved you may be assured of a world market.

Our activities include Gadget-of-the-Month Club and Consumers' Testing League. Please note that you should obtain at least provisional protection for your invention before submitting.

*If you consider your invention
has merchandising possibilities, contact . . .*

AMERICAN GADGETS PTY. LTD.

408 Crown St., Sydney
402 Post Office Place, Melbourne

Fiction By The
WORLD'S BEST AUTHORS

Pocket Book
STORYTELLER

On Sale Now — Price **6d**

A PRACTICAL BOOK ON AMPLIFIERS

We have read many textbooks on amplifiers—probably as much has been written about sound reproduction as any other aspect of radio. And because there is always the unknown quantity of personal likes and dislikes involved, there is always room for argument.

IT was therefore with much relief and not a little amusement that we looked through a copy of **HIGH FIDELITY TECHNIQUES**, written by James R. Langham, and published in USA by Hugo Gernsback for one dollar.

Inside the space of 100 pages pretty well the whole business of getting good sound is covered from A to Z, commencing with a general discussion about distortion, running through speakers and baffles, continuing via amplifier circuit design to conclude with much useful and practical comment on records and pickups.

What we liked about this book was its free and easy approach—it appreciation of the fundamental and many finer points, and its expression of them in understandable terms.

Witness this extract from the foreword, which is typically titled "About This Book." "There is no such thing as an audio engineer. The trouble is that its all subjective. It's not cut and dried . . . Nobody has the right to dictate what you should like. If you happen to want a lot of bass — why fine — nothing in the world wrong with listening to it. Major Armstrong builds a gorgeous hunk of set that your neighbor likes; you are perfectly within your rights if you think it stinks. High fidelity audio is a nebulous thing and unpredictable beyond a certain point.

Now don't get the idea that the book can be dismissed because it's written that way. The point is that although it is packed with practical facts, it makes at the same time really entertaining reading. So much so that, once having got started, we began reading from cover to cover with no great urge to put it down while we digested a set of curves and equations. There are plenty of useful curves and circuits, but very few equations, and no superfluities.

The author is obviously a well-informed man who has done plenty of building. He has told his story as he would tell it to a couple of interested friends over the lunch table with illustrations scrawled on the menu. Maybe that's why most people will be able to understand it.

Whether we would agree with all the ideas expressed isn't as important as the fact that they all represent a point of view with plenty of legitimate thought behind it.

We suggest you keep your eyes open for this little book. Whether it is talking about "boom boxes" (vented enclosures to you) or "R's, Gm and Stuff," it will be well worth the price.

A. We will reserve comment on the circuit until we are able to give it the appropriate space in the columns. Meantime, it has been filed along with other letters in similar strain.

Transients

I consider that Mr. Williams let one of your October correspondents down too lightly. I refer to the reply to a letter signed by Mr. P. Stevens.

Mr. Stevens says: "Although one or two watts output is ample for the average home, his creation has to have 12 watts or more."

It is quite obvious that the gentleman knows little about the subject. He apparently has never heard of transients, he naturally, has never heard them on his 1 to 2 watt outfit. If he attempted to play that excellent recording referred to in "Off the Record"—the Schumann Concerto, which I presume is the Lipatti one, and which starts off with some tremendous chords for the piano, his one watt pet would, in the forte passages, produce something akin, in musical tone, to a couple of sticks being banged together.

On the other hand if he brought the same record along to one of those foolish "enthusiasts" with a despised 15 watt Williamson fed by a modern high compliance lightweight pick-up, adequate bass compensation and working into a 15 watt speaker such as a Goodmans mounted in a vented enclosure, even the prejudiced Mr. Stevens would have to admit there was quite a difference. Those heavy piano passages, which on his one watt just blurred and rattled, without any semblance of tone, now come out clean and melodious, no rattle, no blur, just satisfying genuine piano tone, no matter how vigorous the pianist.

That, Mr. Stevens, is because, although you apparently don't know it, the sudden burst of energy which arises instantly when a percussion instrument is struck may reach to eight, ten or twelve watts even when the normal operation of the outfit is set to your favorite 2 watts. These transients are of very comfortable aural satisfaction, and call for that reserve of power which is the reason for the 12 to 15 watt amplifier and speaker.

Actually, if the 15 watt outfit were taken into a public hall and tuned up to work at its full rating, then it, too, would fall down on rendition of transients because, like Mr. Stevens' one watt, there would be no reserve to handle these essential components. (If 15 watts were needed to fill a large hall adequately, then nothing less than a 50 watt amplifier would properly do the job.) (C. W. Warlow).

* * *

Overseas reader

Howard D. Thompson (Salem, Oregon, USA) writes: "I have a very good friend who lives in

Brisbane. He sent me the January and February issues of your very wonderful radio magazine. I do a lot of radio experimenting and have done so for over 25 years and get a lot of enjoyment out of it. I was really thrilled when I saw the article on page 36 of the February issue, telling about the 4-watt amplifier. I was looking for a diagram of a small amplifier to build, and so as soon as I read the article in Radio and Hobbies, I started building it. Now I have it completed and it works wonderfully. I have it hooked up with my tape recorder. I also noticed the simple receiver for 288 Mc. and I have made that up also and it works well.

"I read the article on page 48 about Enlarging Your FM Tuner and have made that, too. When anyone comes and sees these sets, I tell them that they were built from plans in a radio magazine from Australia. I like the article 'For the Junior Experimenter.' I read with delight the department, 'A Reader Built It.'

"It is very interesting to read through a magazine from some other country and see how they do things. I find that your magazine is published and set up just as well as any of our radio magazines.

"I like the article 'Short Wave Notes,' by Ray Simpson. I am very much interested in short-wave listening and have a lot of cards from stations all over the world. I have six verification cards from stations in Australia, and they are only a few of what I hope to get from time to time. "Best of luck."

* * *

A bouquet

Just a few lines in acknowledgement and appreciation of the help Radio and Hobbies has been to me. I have been interested in radio ever since it began to operate, and whenever I have been in need of a circuit to use I have looked up the old Wireless Weekly, and now Radio and Hobbies is my stand-by.

The Little General in its various forms has been a success, also the several Advance sets. I also built a couple of amplifiers, the one valve Gramophone was one of them, and also "PA5 High Gain." I used this job for a deaf aid system in a church, connecting a suitable line transformer to it for the phones. It can also be used with the gramophone pick-up as well as for public address and a splendid job it is, too. Wishing you all the best, I am yours respectfully (P. M. Beck).

ANSWERS TO CORRESPONDENTS

Unsigned, of Post Office, Tuena, NSW, sends in 1/- with a request for a 1-valve receiver using the 1K5-G.

A. We regret that you omitted to sign your name. If you will drop us another line, we shall be glad to forward you the circuit.

R. Toreaux (Queensland) writes complaining of the scarcity of SWG wire gauges specified by R. & H. and suggests that B. & S. gauges would be more suitable. We also ask some questions about a R. & H. circuit and submits two of his own for comment.

A. As sure as we specify B. & S. gauge R.T., we will have a flock of requests to use SWG. Actually the two gauges were converted quite readily from wire tables, and the resulting discrepancy is then negligible. Many thanks for your report on the "Reader Built It" set, and glad to know you have had such good results. The BFO coil for the double conversion superhet could be an IF transformer of whatever inductance the IF used. As mentioned in the handbook this IF can be anything from 455 KC to 50 KC. The 7 Mc crystal would necessitate changes to the coils. Its harmonics would, however, provide a marker point in the amateur bands. The two circuits submitted should function but with much reduced efficiency, and battery drain is likely to be excessive. The tone control circuit is correct. In the case of the TRF set the screen dropping resistor to the first valve could be omitted and we would not recommend the 6S17 in this position. The back bias resistor of 1000 ohms is not required in this circuit and the 300 ohm bias resistor in the detector stage is also not required. Care should be taken to see that the current through the phones is not excessive. Some form of shunt feed system may be preferred here.

M.M. (Hawthorn, Vic.) advises of his new address and at the same time makes some general remarks with regard to our magazine.

A. Our subscription department has been notified about the change of address as requested. We are very pleased to hear that your version of the "Jeep" performed so well and trust that you will find as much of interest in future issues of Radio and Hobbies as in the past.

B.W.B. (Kew, Vic.) wishes to construct an 80-meter beam from 3-8in diam. rod. A. The idea is not impossible but most people would find it quite impractical. Each element of the beam would need to be 30 odd feet long so that to support the elements the rotating mechanism would have to be built along the lines of a locomotive turntable. We suggest that you check through the chapters on aerials in the standard amateur handbooks as the subject is much too lengthy to be discussed here. You will also be interested in the article on aerials in the 1950 edition of the Australian Shortwave Handbook, which is available from most booksellers at a cost of 2/-.

J.T. (Beecroft, NSW) sends in the circuit of a small battery-operated receiver for comment.

A. Although, as far as we can judge from a quick check, your circuit would work, it would be possible to obtain much better performance by including regeneration in the detector stage. The circuit would then be very similar to that of the "Duplex Single" which, incidentally, we can send to you through the shilling query service. The value you have indicated for the volume control of your set is quite in order and it is not necessary to include a condenser between the microphone transformer and the volume control. The microphone circuit you have indicated should work well although we would imagine that the available gain would be much greater than normally required. The tone control circuit also is quite in order. The size of the "A" battery you employ is a matter that can only be decided with a knowledge of the particular circumstances. A single torch cell will give a few hours of life while a large heavy duty "A" battery could be expected to last much longer. Any audio transformer with a ratio between about 1½ and 3½ to 1 would be well suited to your circuit.

BRANDED RADIOS

RADIOLA, S.T.C., PHILIPS, ASTOR, M.V. Every set carries 90 days conditional GUARANTEE.

A.C. MODELS

Asma 4 valve, list price £18/18/-. Our price £12/10/-. Asma 5 valve, list price £21. Our price £16/10/-. T.C. Bantam, list price £17/17/-. Our price £13/10/-. Philips 4 valve, list price £18/18/-. Our price £14/10/-. Riesler Dual Wave, list price £18/18/-. Our price £13/10/-. Philips 5 valve dual wave, list price £17/10/-. Our price £22. M.V. Model 46, list price £21. Our price £14/10/-.

PORTABLE 1.4 VOLT BATTERY MODELS

Tecnico 5 valve, very powerful, list £31. Only £22. Astor 5 valve, very powerful, list £31. Only £20. Meteor Pan, 5 valve, very powerful, list £31. Only £23. Tele Verta 4 valve, bargain price to clear, £13/10/-. These prices include batteries.

VIBRATOR BATTERY MODELS

Kriesler dual wave £19/10/- Tele Verta dual wave . . . £22/10/- Airzone B/cast, portable case £19/10/- Radiola B/cast, 4 volt . . . £16/10/-

COUNTRY ORDERS

Sets packed in cartons and sent by air freight where possible. Otherwise by passenger train, freight forward.

RADIO MART

439 PITT STREET
SYDNEY. Tel. MA2351

LUMINOUS PAINT

Powder, 3/-. Hydroponic, soil-less gardening salts, with instructions, 5/-. Silverplating Compound for brass and copper, 4/-. Fish Lure oil, 4/6. Silver, metal polish cloths, impregnated, 1/9.

ANDES DISTRIBUTORS.

Box 33, P.O., Fairfield, NSW.

MAKE MONEY AT HOME

Cast bowls, book-ends, lampstands, statuettes, gifts, novelties, etc. Learn new, easy Moulding Arts. Start Home Business. Send stamp for details.

Dept. B, Le Bon College (regd.), Box 279 Haymarket P.O., Sydney.

Let's Buy an Argument

(Continued from Page 69)

requires a wide-band system, or one with a very short rise-time or one with a minimum of phase delay in the upper register. Essentially the three expressions mean the same thing.

But don't forget that, if the record the pickup, the tuner, the speaker or anything else slows up the vital harmonics, the final sound still has to be rounded off, no matter how good the amplifier is. What's more, if compensation is employed in the amplifier to offset the deficiency in terms of frequency, it will probably compensate matters correctly also in terms of phase. This was part of my original justification for using compensation and tone control of the right kind.

AESTHETICS

Finally, there has been little time, as I write, for arguments to develop about the aesthetics of reproduction but here are a few random thoughts contributed by Mr. Browne, of Coogee:

"Individual engineers may set their microphones in quite different positions, even for the same orchestra. Allowing also for monitoring, there would be variations in the finished record equalling an unknown number of db in the amplifier."

(No comment required.)

"Nearly all the so-called lightweight pickups have some form of counterbalance. The record, in displaying inevitable eccentricity, &c. must move the total mass of head, the arm and the counterweight."

(What do you think of this one?)

"With regard to 78 and long playing records, one method pickup manufacturers are using is to change the stylus. Imagine trying to fit a stylus back into its original position each time."

(The idea is that the stylus shall not be fitted back into the original position. It is contended that the constant changing will never allow a "flat" to develop on any one face.)

"The frequency response of an amplifier varies, particularly in the treble, with the setting of the volume control. It would seem that the only way would be to vary the amplification of the audio tubes."

(There are too many difficulties about this; and gain control using negative feedback is seldom convenient. The problem affects the treble only and the simplest corrective is to bridge the "hot" end of the potentiometer with a selected small value of condenser.)

INSTRUMENT CASES

We specialise in All Classes of Covered Cabinets—Instrument, Portable and Mantel Radio Cabinets in either Leather or Leatherette.

GIBBONS & DENHAM

122 DARLING ST., BALMAIN
Phone: WB2772, Sydney
For trade only

RADIO DESPATCH SERVICE November Specials

Clearance of genuine Jaffe Toasters. Each 15/-
Stamper 4 1/2 volt 6 Batts. Each . . . 10d
0-1 M/A 2 1/2 meters. Each . . . 30/-
Universal Sewing Machine Motors.
Hotpoint Radio Receivers. Phillips and Radiotron Valves, complete range.
All other Radio and Electrical Accessories stocked. Trade supplied.

Phone: MA1876 or call.

Wembley House, 841 George St., Railway Square, Sydney.



The CAPTAIN AERIAL UNIT equals a 50ft. high aerial, gives tone, volume, sensitivity, more stations, freedom from lightning. Reduces static, fits inside your set. Does away with poles and guy wires. Broadcast or short-wave reception. Installed in a minute—nothing to get out of order. PRICE ONLY 6/9. Registered Post Free. No C.O.D. Money Refunded if Not Satisfied.

REG COOKE,

P.O. Box 9 (H), Gerringong, N.S.W.

LEARN
AT HOME
for
2/6
WEEKLY



It's "Quicker"—easier under MONEY-BACK GUARANTEE with a Sampson Home-Study course for
★ Hill-billy Guitar
★ Steel Guitar
★ Banjo Mando
★ Piano Accorcion
★ Saxophone
★ Clarinet ★ Ukulele
★ Mouth Organ
★ Button Accordion
★ Violin ★ Piano
5000 have succeeded—why not YOU?

It takes 3 Lessons to play first piece—10 Lessons a variety and 20 Lessons any piece. It doesn't matter where you live.

INSTRUMENTS. Exclusive models available on small payments to any part of Australia—Freight paid.

FREE. Illustrated catalogue and descriptive booklet FREE. Write for yours. (MENTION INSTRUMENT FAVORED)

SAMPSON'S, Dept. 14, 481 Kent St., Box 4184X, G.P.O., Sydney

POCKET BOOK STORYTELLER PRICE SIXPENCE

PAGE ONE HUNDRED AND THREE

STEREO-TELEVISION FOR ATOM LABORATORY

TELEVISION in three dimensions has been developed by engineers at the Argonne National Laboratory near Chicago. Used along with electronic remote-control devices, it enables atomic scientists to conduct experiments at a safe distance from readily radioactive materials. When operating a mechanical hand three-dimensional views are almost essential in grasping beakers and performing infinite precision tasks behind the lead shields. Dr. H. L.

Hull, director of Argonne's remote-control engineering division, has devised two types of stereo-television. Both use the double-lens camera. One receiver presents two nearly identical pictures on the television screen which must be viewed through prismatic glasses to get one three-dimension picture. The other projector superimposes one image on top of the other and looks out of focus until viewed through polarised spectacles.

HERE'S VALUE

that makes a wonderful

XMAS PRESENT

The Federal 35/120" Enlarger Kit,
mailed to your door for only

£9/19/6

Fit your own lens or we supply single
meniscus lens f.11 2 1/2" or 4" at 17/6
each mounted ready for use.

- Positive screw focusing.
- No bellows to wear out.
- Solid upright, vibration free.
- Complete with globe.
- Proper light diffusion with flashed
opal screen.

All enquiries promptly attended to. Make sure of quick delivery by writing
now, enclosing stamped, addressed envelope.

FEDERAL PHOTOGRAPHICS

..... DIVISION OF
BEAUMARIS HARDWARE CO.

22 DALGETY RD., BEAUMARIS, VICTORIA, AUSTRALIA. Tele.: CHELT. 1511.



WANTED TO BUY, SELL OR EXCHANGE

EXCHANGE OR SELL: New 32-watt
Amplifier unit with Garrard PU unit
4v tuner, 3v mixer in case, 12" Rola
cables, for late model car radio. 88/
Sutton St., Echuca, Vic.

FOR SALE: Amateur radio ticket
Personal correspondence course by
radio amateurs. Details Amateur Radio
League, Box 1047N, GPO, Brisbane.

FOR SALE: Garrard Automatic Record
changers. Model RC65. In brown
leatherette carrying case, £18. Leyland
31 Glen St., Milson's Point, Sydney.

FOR SALE: American Webster 3-speed
automatic record-changer and pickup
complete with adaptor and 240-110 volt
transformer. New condition. £50 or offer.
Apply No. 5468, Radio & Hobbies.

FOR SALE: One each 4 and 5 valve
Battery Chassis, complete and wired,
less valves, 30/-. One each Power Trans-
former, power valve and rectifier as
new, lot 30/-. Fred Doessel, Preston, Qld.

SALE: AVO AC-DC Test Meter, £15.
8m/A m/c Meter, 15/-, 2-1R5, 1N5,
1H5, midget 2-gang, 10/- each. Loop ant.
5/- Port record case, £1. Arrl. H/book,
12/6. Pop. Science Radio Man, 7/6. USA
Geographics '46-'49, 2/6 ea. Leitz enlarg-
er, £25. Want pr. good binoculars. Ward,
35 Clarke St., West Ryde, NSW.

FOR SALE: 3 valve AC mantel receiver
(Minnivox) £7/10/-. B. A. Williams,
103 Bathurst Rd., Orange, N.S.W.

SELL: Set parts to build R&H 5 BPM
C.R.O., with chassis and case, power
supply, all tubes and components. All
New, assembled, part wired, £20 or offer.
F. Smith, 32 William St., Forbes, N.S.W.

SELL: 15-watt AC/6VDC Amplifier.
3 valve D/W AC/6VDC Receiver, two
8" Speakers with Transformers. Garrard
Motor and PU. All units as new in at-
tractive portable cabinets. Crystal mic,
universal test loud speaker. Best offer.
64 Lake View St., Boolaroo.

SELL: ALL R. & H. from May, '44, to
Dec., '49. Best offer. S. L. Mann,
PO Box 43, Sth. Grafton, NSW.

SELL: Eddystone 640 Receiver, as brand
new, £50. E. H. Zahnel, Box 15,
Finch Hatton, Qld.

SELL: ICS Service in Radio Engineering,
price £33. Will sell for £20. Ring
McGill, FA3974, Sydney.

SELL, or exchange for any useful article
85 loose and bound copies of R. & H.
from 1939 issue to present, all different
what offers? D. Dennis, Dutton St.,
Coolangatta, Qld.

SELL: British Jonrad "Globe King" 1
valve short wave receiver with new
batteries (two 45 volt, one 3 volt), good
earphones (equivalent to Brown's type D)
and instructions to operate. Set works
perfectly. Bargain £5/5/-. A. Glassey, 24
Geoffrey St., Toowoomba, Qld.

WANTED: Mf Shf dials and dial move-
ments for ARS receivers. Quote
price and condition of dials to J. P. Troy,
PB Kerang, Vic.

WANTED: 1946 July R. & Hobbies. Will
pay 3/-. Egan, Tolmie, Mansfield, Vic.

MODELS: Blue Prints of Old
time Sailing Ships.
Send 2/- for latest Catalogue. O. B.
Bolton, 70 King St., Sydney.

Printed and published by Associated
Newspapers Ltd., at the registered office
of the Company, 60-70 Elizabeth Street,
Sydney, NSW.

RADIO AND HOBBIES FOR NOVEMBER, 1950

AIRCRAFT Dashboard CLOCKS (U.S. & U.K. Air Forces)

These clocks are suitable for HOME, CAR, MOTOR BIKE, BOAT, AIRCRAFT,
PIGEON RACING, and IDEAL for DARK-ROOM precision timing or any place
where a reliable timepiece is required. All clocks listed have jewel lever move-
ment.

AMERICAN ELGIN WATCHES



AMERICAN ELGIN
8-day, with sweep centre, sec-
ond hand, luminous dial.
Reconditioned as new.

£5/5/-



These WORLD
F A M O U S
P O C K E T
(ex - Army)
WATCHES (as
i l l u s t r a t e d),
with all lumin-
ous dials, jew-
elled m o v e -
ments with sec-
ond hand, are
worth £8/10/-.
R e c o n d i t i o n e d
as new. A
necessity to the
man on the
land or in the
tropics. **65/-**

Screw front and
back.

ENGLISH



1-day, luminous
dial with sweep
centre and
dummy time
of flight hands.

BRAND NEW

£2/17/6

SMITH'S 8-day non-
luminous dial with
dummy time of flight
hands.

BRAND NEW

£4/12/-



All orders promptly attended to. Please send Cheque, Money Order or Postal Notes
SORRY, No C.O.D.

M. GOODMAN

422 PITT STREET,
SYDNEY, N.S.W.

Australia's Best Magazine of Fiction
Pocket Book Weekly
OUT EVERY MONDAY—PRICE 6d